

## APPLICATION NOTE

### ANP024 | The USB Interface from EMC Point of View



Dr.-Ing. (Doctor of Engineering) Heinz Zenkner

#### 1. TECHNOLOGIES AND KEY FIGURES

The USB (Universal Serial Bus) specification defines the mechanical and electrical characteristics, as well as the protocol layer of the interface. The cable and connector are precisely defined. USB defines two types of hardware, hubs and functions, as well as terminal devices. In theory, up to 127 devices can be linked together in a star bus topology in which the only limitation is the 7-bit address. Connections are possible between the hub and function or terminal device or between hub and hub, whereby direct connections between terminal devices are not possible.

USB is a differential, bidirectional, serial cable bus. The differential NRZI (Non-Return-to-Zero-Invert) signal is transmitted asynchronously between the ports. The maximum cable length is 4 meters, the cable contains four wires, two for the twisted data pair and two for the supply voltage of the terminal devices and ground.

The data rate is between 10 kb / s and 480 MB / s in one of the three possible modes.

- 10 - 100 kbps for slow data transmission (mouse, keyboard). The signal voltage is between 0 V and 0.3 V.
- 0.5 - 10 Mbps for medium data transmission rates. The signal voltage here is 0.3 V (low) up to 2.8 V (high).
- 25 - 480 Mbps for high data transmission rates, defined as USB 2.0 with a maximum possible rate of 480 Mbps. The signal voltage here is 0 V ± 10 mV (low) up to 400 mV ± 10% (high).

At high data transmission rates it is necessary to terminate each of the symmetrical conductor pairs to ground with

a 45 Ω terminal resistor. Here the cable impedance must be 90 Ω +/-15% (symmetrical / differential).

Originally, USB was intended to supersede the serial and parallel interfaces in IT, meanwhile USB has become established not only in the IT domain, but has become indispensable in many other fields of application, e.g.

- home audio, video – for digital photos and music
- automotive – for MP3 music
- mobile IT, such as hand scanners – uploading data to a PC
- industry controllers – software upgrade, data download and upload
- medical devices – software upgrade, data download and upload

USB is a network with a star-shaped topology. All other USB terminal devices branch out from the host controller. A USB terminal device represents the bus connection, whereas a USB hub can branch to another hub or to terminal devices. Every other USB hub can represent a branching point until the maximum number of addressable devices is attained. This illustrates what a complex network structure can be built up with a USB and this also clearly shows that this structure has to be paid special attention with regard to EMC. It is now apparent that even USB devices as standalone devices, i.e. without hub, without further branches, can display EMC weaknesses and "only just" meet the demands placed on them, and in a more complex structure can no longer meet their requirements. This then manifests itself in write/read errors with drives, dropouts with cameras, writing delays with keyboards, etc. But more on that later.

# APPLICATION NOTE

### 2. HARDWARE AND COMPONENTS

Receptacles and plugs can have different sizes with USB, depending on their use in cameras, video devices or IT. The USB hub and terminal device connector can also differ in their form. The pin assignment is always the same, as shown in Figure 1 and Table 1.



Figure 1: Pin assignment of the USB interface, type A receptacle and plug.

Pin	Signal name	Color
1	VBUS	red
2	D-	white
3	D+	green
4	GND	black
Package	Shielding	Ground

Table 1: Pin assignment and cable assembly for USB.

The USB cable should be structured as shown in Figure 2.

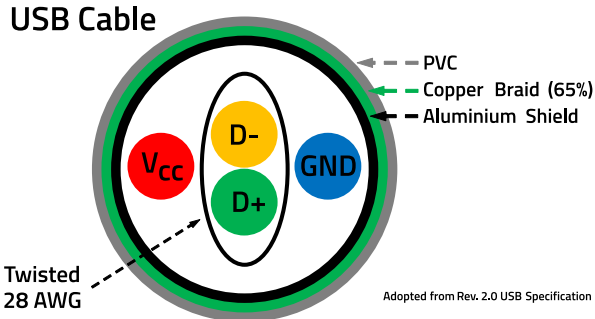


Figure 2: USB cable layout.

The cable has four wires, which are precisely defined—the data wires are 28 AWG (American Wire Gauge) and the supply wires are 20 to 28 AWG. This defines the diameter and copper resistance, the HF conductor parameters result from the further structure.

The two supply wires are untwisted, the data wires are twisted around one another, this results in the differential mode impedance of 45  $\Omega$  or 90  $\Omega$  (+/- 15%) against ground. The cable shielding should have a shielding braid with an area coverage of at least 65% and also an aluminum shield, i.e. double shielding is intended to guarantee high shield attenuation and consistent wave impedance for the cable. I can confirm from practice that there are many "black sheep" on the market, some of which only have an aluminum shield and even this consists of a foil that is only metalized on one side. Structured like this, the "shield" leaves a gap over the entire length of the cable and so the shield attenuation hardly attains values over 15 dB rather than the common > 50 dB - but it is cheap.

The cable length must not exceed 5 meters. If longer lengths are needed, hubs have to be connected in-between.

Due to the high flexibility in the application and the high data transmission rate, special requirements arise for the circuit design and the interface construction - also depending on the application area.

Chip manufacturers know the problem of high data rates and the EMC requirements that still apply in terms of interference emission and immunity, and develop their USB controllers to be as good as possible in this regard. Nonetheless, not only the chip design, but also the complete circuitry concept has to be developed with a view to EMC. For this reason, the

- circuit concept
- layout
- filter concept
- construction (housing, connectors)

have to be coordinated. This certainly takes more effort in the development phase, but pays off in higher quality and also in lower production costs. Good engineering does not make products more expensive, but, given the same quality, makes them cheaper.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### 3. EMC CRITERIA

So what does EMC have to do with the USB interface? Before taking a closer look at this, I would like to define an equation:

$$\text{EMC} = \text{assured functionality} \quad (1)$$

EMC is not "nice to have" to meet legal requirements for the declaration of conformity. EMC in our example of the USB means:

- Low interference radiation: A well matched symmetrical interface with optimized filters does not radiate. Through matching, the useful signal has the required quality factor Q, so we also achieve the required signal-to-noise ratio and high interference immunity.
- High interference immunity: By symmetrizing the useful signal and using additional filters with overvoltage protection as well as interface jacks offering high levels of shielding attenuation with the relevant high design quality (not expensive) housing design, the interference immunity is considerably increased against transients and other inductively and capacitively coupled interference signals and therefore the functionality is ensured.

Before we examine the circuitry and design measures, here is a brief excursion into EMC basics. What is EMC?

Electromagnetic Compatibility is the capability of an electrical system or device to work properly in its electromagnetic environment without being disturbed in its proper operation by neighboring systems or devices and without disturbing other systems or devices in their proper operation. This is a long and complicated sentence, but contains just what we previously described somewhat more technically with the question "What does EMC mean in case of the USB interface".

What EMC phenomena do we have to consider in the development of a product with USB and what are the most critical phenomena? These are:

- interference emission (interference field strength)
- interference immunity against electrostatic discharge (ESD)
- interference immunity against fast transients (burst)

As mentioned, there are now numerous application areas for USB. Every application area has other standard EMC requirements, but let us consider our equation (1).

Functionality must always be ensured and experience shows: If functionality works, then EMC also works, regardless of the application area.

In the following we will examine USB circuit design step-by-step and present the design points to be considered.

### 4. EMC CIRCUITRY CONCEPTS

The USB interface is a bidirectional, symmetric interface, as presented in Figure 3.

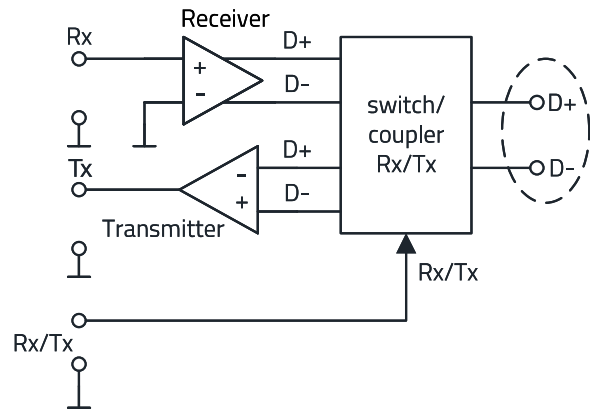


Figure 3: The USB interface is symmetrical and bidirectional.

Symmetrical transmission techniques have numerous advantages in terms of signal integrity, which are apparent in lower interference emission and higher interference immunity. Figure 4 provides a more detailed explanation.

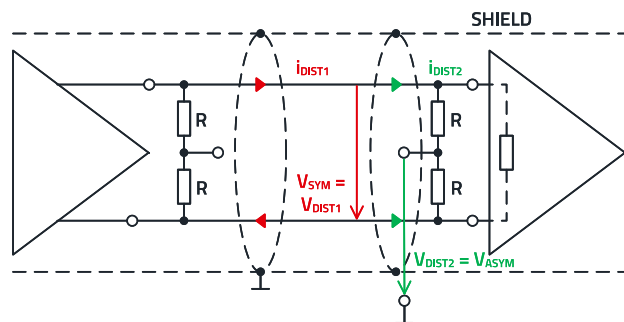


Figure 4: The symmetrical interface with its measurable interference voltages.

The following are measurable:

- $U_{\text{sym}}$ : interference voltage between the signal wires
- $U_{\text{Asym}}$ : interference voltage between the voltage midpoint and the reference voltage (ground) and the cable shielding.

This means that the USB transmission path can be affected by both differential mode, as well as common mode interference voltages.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

This can be both interference voltages from the interface itself, in this case described as interference radiation or interference emission or an electromagnetic effect from the outside in the form of inductive, capacitive or wave coupling - in this case described as interference coupling, which assumes a certain interference immunity of the interface in order to maintain continued function.

### 4.1 Interference emission

In the case of USB transmission, differential mode interference is mainly generated by non-linear signal harmonics due to mismatching and inadequate circuit design. Given asymmetry of the transmission path, i.e. transmitter, circuit board and conductor tracks, possibly filters, cables through to the receiver, this interference can lead to interference radiation and impairment of signal quality.

Common mode interference arises from parasitic coupling in the circuit environment of the USB controller, which can usually be found from capacitive coupling on the USB signal with rising interference frequency and increasingly in amplitude. However, these interference types are found on both USB wires in phase and at the same amplitude and therefore do not impair the useful signal. Asymmetries in the cable or at the receiver often convert the originally common mode into a differential mode interference signal, however, which can then contribute to signal impairment. High quality circuit design is called for here too. Figure 5 illustrates the case.

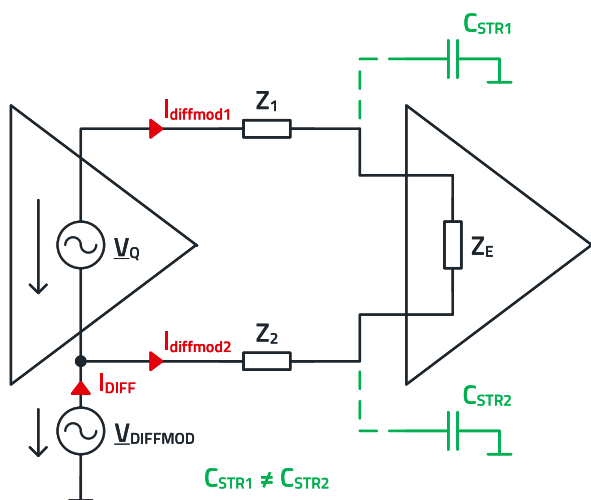


Figure 5: Conversion of differential mode to common mode interference due to parasitic coupling capacitaries.

### 4.2 Interference immunity

Differential mode data transmission offers a significant advantage over the simple coaxial cable when it comes to the effect of interference on the USB. Figure 6 presents the effect of interference on a coaxial cable.

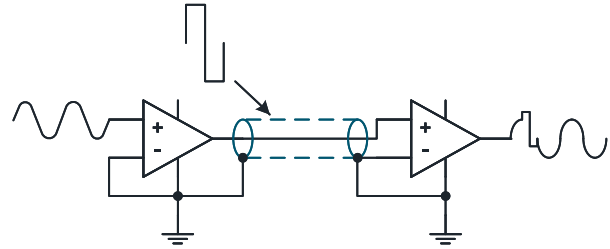


Figure 6: Effect of interference on a coaxial data transmission path.

Depending on the shielding effectiveness of the coaxial cable, a burst (electric field), for example radiated from a mains cable in parallel with the USB cable, couples into the data line and interferes with the data signal. This leads to data or communication errors, which depend on the interference signal length and amplitude.

Figure 7 represents the case of differential mode data transmission, in this case with only a twisted pair of wires.

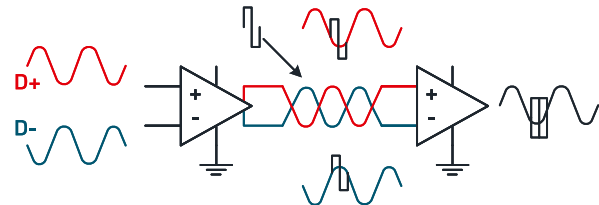


Figure 7: Compensation of electrical interference coupling of the differential mode signal input and twisted wire pairs.

The polarity of the useful signal is shifted from one wire to the other by 180°, the signal difference is evaluated at the input of the receiver. But the interference signal affects both wires in the same phase, so this cannot have an effect as an interference signal at the receiver.

Furthermore, in the case of the inductive interference effect (magnetic field), the twisting of the wires achieves compensation of the interference effect. As a result of the symmetrization of the partial inductances of the respective twisted wire, the interference influences compensate each other.

## APPLICATION NOTE

### ANP024 | The USB Interface from EMC Point of View

#### 4.3 Possibilities of reducing emission and increasing interference immunity

It is apparent in practice that interference emissions cannot be prevented and also interference immunity also has its – sometimes stringent requirements. The reason lies in many details, of which these are the most important:

- The inputs/outputs of the USB controller are insufficiently symmetrical, the USB signal displays common mode interference.
- The layout is not HF/EMC compatible, parasitic capacitances and the lack of wave impedance matching generates common mode interference.
- The circuit design (USB filter) is inadequate, the filters affect the signal quality and/or the insertion loss is too low.
- The interface design (receptacle, housing) is inadequate, poor ground reduces the shield attenuation of the cable, filters have poor ground reference.
- The USB cable is asymmetrical, poorly shielded, has inadequate ground connection. The cable deteriorates the signal quality, radiates signal harmonics and has insufficient shield attenuation towards external interference sources.

Some points cannot be influenced, these include the technical realization of the USB controller and the use of "cheap" USB cable. This demonstrates that preventive measures have to be met. Measures to

- protect the interface from the effects of external interference, which can lead to the destruction of the USB controller.
- limit interference radiation of signals via the cable.

## 5. REALIZATION OF THE USB FILTER

### 5.1 Circuit technology

Both points can be fulfilled using additional filters and the USB interfaces. Figure 8 shows the basic circuit of a symmetrical USB signal filter.

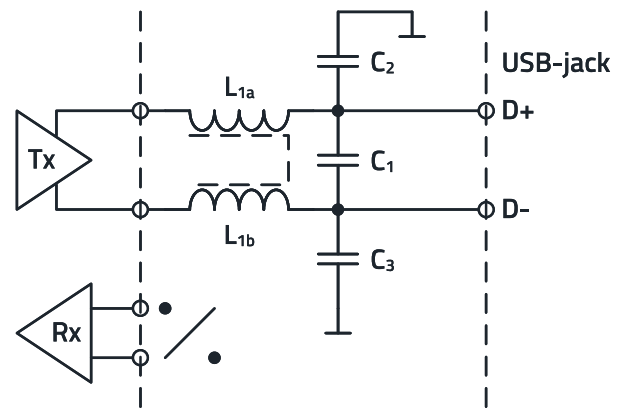


Figure 8: Basic circuit of a symmetrical signal filter.

Capacitances of up to approx. 3 pF between the data line and ground are tolerable with USB 2.0, beyond this the signal is impaired too much so that non-linear distortions occur that cause phase shift and attenuation in the harmonic component of the useful signal. The capacitors  $C_2$  and  $C_3$ , together with the current-compensated choke, reduce the symmetrical interference components. The capacitances  $C_2 / 2$  and  $C_3 / 2$  affect the signal. It goes without saying that  $C_2 = C_3$ .  $C_1$  reduces the symmetrical interference components and thus also affects the useful signal, its capacitance should be less than 4 pF. The values depend strongly on the properties of the current-compensated choke. The choke must have a high degree of symmetry and low stray capacitance between  $L_{1a}$  and  $L_{1b}$ .

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

Furthermore, the real component of the ferrite permeability - that is the inductive component - must be low and within the useful frequency range. In contrast, the resistive component of the permeability - that is the complex component - must be high and within the frequency range to be filtered. Figure 9 illustrates the relationships. The ferrite material has its transition range at around 200 MHz.

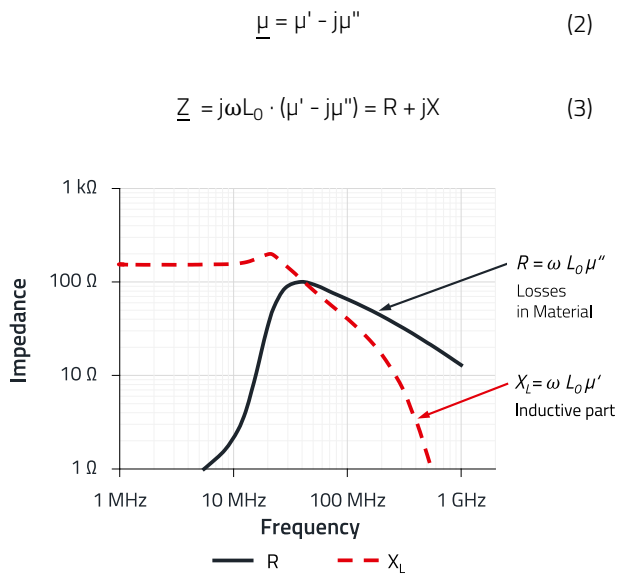


Figure 9: Example for the curves for the complex and real permeability components of a HF ferrite material.

Transient interference signals, such as ESD and bursts, can generally be limited with varistors. Especially SMT multilayer varistors which are particularly fast and withstand a high level of energy. What they all have in common is their high capacity, which is why they are not suitable for limiting transients at the USB. Transient limitation with diodes is shown in Figure 10.

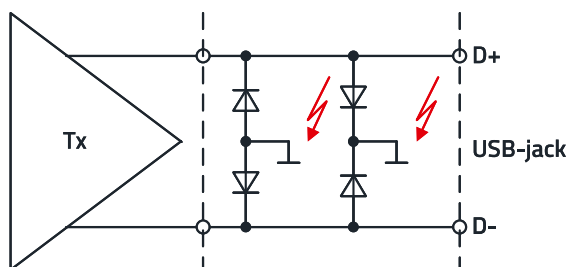


Figure 10: Diode limiter to reduce coupled transients (burst, ESD) on the USB interface.

Transients are limited against ground, both on D+ as well as on D- up to the forward voltage  $V_F$  of the diodes. This voltage is around 0.7 V for silicon diodes.

A problem appears very quickly here, which is why the diode pair on the right has two red flashes. The signal voltage of the "mid-speed" signal is up to 2.8 V (D+ to D-), i.e. 1.4 V to ground. The positive branch must therefore be provided with an "offset" in order to avoid impairing higher signal voltages.

Figure 11 shows the solution.

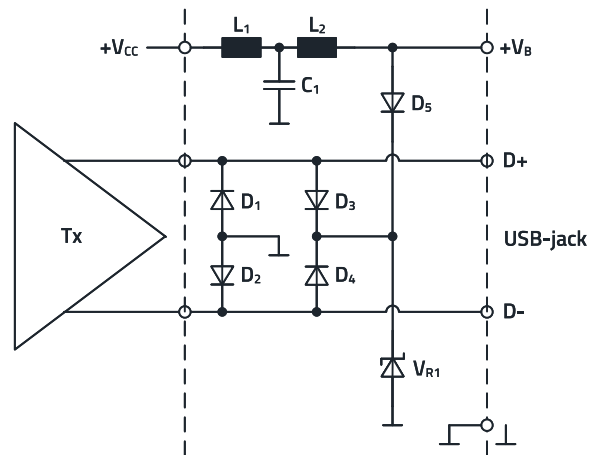


Figure 11: Diode limiter to reduce coupled transients (burst, ESD) on the USB interface with "offset" for higher signal levels.

An additional TVS diode with a limitation voltage of 6 V sets the threshold value to approx. 6.7 V. That is sufficient for protection; TVS diodes with lower limitation voltages are too slow to limit ESD. The voltage levels are illustrated in Figure 12.

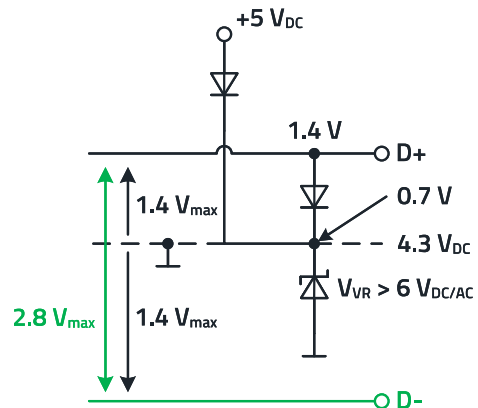


Figure 12: Voltage level of the positive diode path.

Transient limitation at the connection of the supply voltage can be achieved at the same time using the additional diode  $D_5$  in Figure 10. Although the capacitance of the TVS diode is low at 5 pF, it would be too high for USB. As  $V_{R1}$  is in series with  $D_3$  and  $D_4$ , however, the capacitance of  $V_{R1}$  reduces the overall capacitance that affects the signal here - so it is uncritical, as  $D_3$  and  $D_4$  have capacitances of approx. 2 pF.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

As in Figure 8, the capacitors are in series with  $D_3$  and  $D_4$  with reference to the signal, there is an overall signal-to-signal capacitive load of 2 pF and signal against ground of around 3 pF.

In the supply voltage branch there is a T-filter with two SMT ferrites and a ceramic capacitor. The lossy component of the permeability should rise sharply at around 30 MHz, the inductive component is uncritical, as no signals are affected. The current carrying capacity is an important parameter, which is specified in the datasheets at 20 °C. It should, of course, be selected to be adequate for the respective application.

### 5.2 Practical example

Figure 13 shows the complete circuit diagram. The associated technical data of the components are specified as follows.

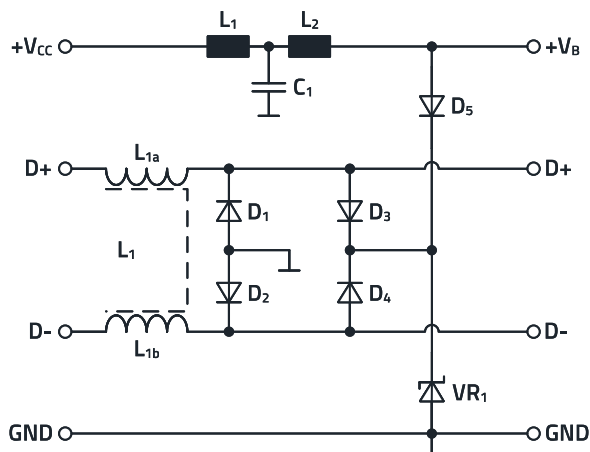


Figure 13: Complete circuit diagram of the USB 2.0 filter.

### Filter for DC supply

The SMT ferrite already has an impedance of 300  $\Omega$  at 30 MHz, of which 200  $\Omega$  is resistive – i.e. the "ohmic" component. The ferrite has its maximum impedance in the range from approx. 80 MHz to 500 MHz in which the highest level of interference is to be anticipated in USB data transmission, above 200 MHz it is practically only lossy. Above 200 MHz the ferrite acts like an ohmic resistance without reactive components. Table 2 shows an overview of the most important parameters, the impedance curve is presented in Figure 14.

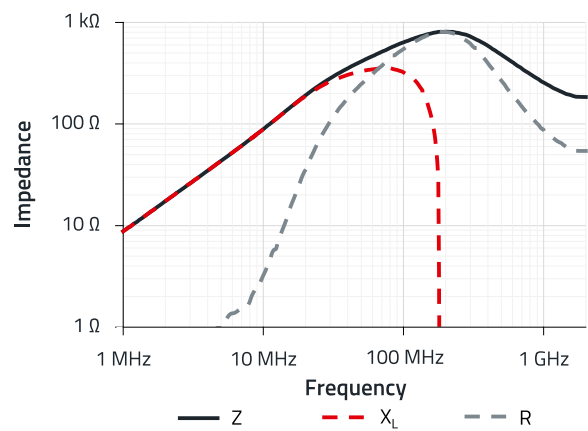


Figure 14: Impedance curve of the SMT ferrite [742792651](#).

The capacitor WCAP-CSGP X7R0603684K016DFCT10000 used here (Part. No [885012206051](#)) has the following characteristics:

- Max. voltage 16 V
- Capacity: 680 nF
- Tolerance: 10%
- Ceramic: X7R

Properties	Test conditions		Value	Unit	Tol.
Impedance @ 100 MHz	100 MHz	Z	600	$\Omega$	$\pm 25\%$
Maximum impedance	200 MHz	Z	800	$\Omega$	typ.
Rated current	$\Delta T = 40 \text{ K}$	$I_R$	1000	mA	max.
DC resistance		$R_{DC}$	0.20	$\Omega$	max.

Table 2: Electrical characteristics of SMT ferrite [742792651](#).

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

The capacitor should have its series resonant frequency above 500 MHz, which depends on the dielectric and the package. Small packages like 0603 or smaller with lossy dielectric such as X7R or Y5V are well suited. Lossy dielectrics exhibit less pronounced resonances, which is desirable for filters in the supply voltage area. The resonance is a series resonance, which, as a result of the parasitic components above the resonance frequency of the filter, make the capacitor unfit for use, i.e. in advance: The ground connection of the capacitor also has to be low-inductance (layout) in order to keep the total impedance as low as possible. Figure 15 illustrates the relationship.


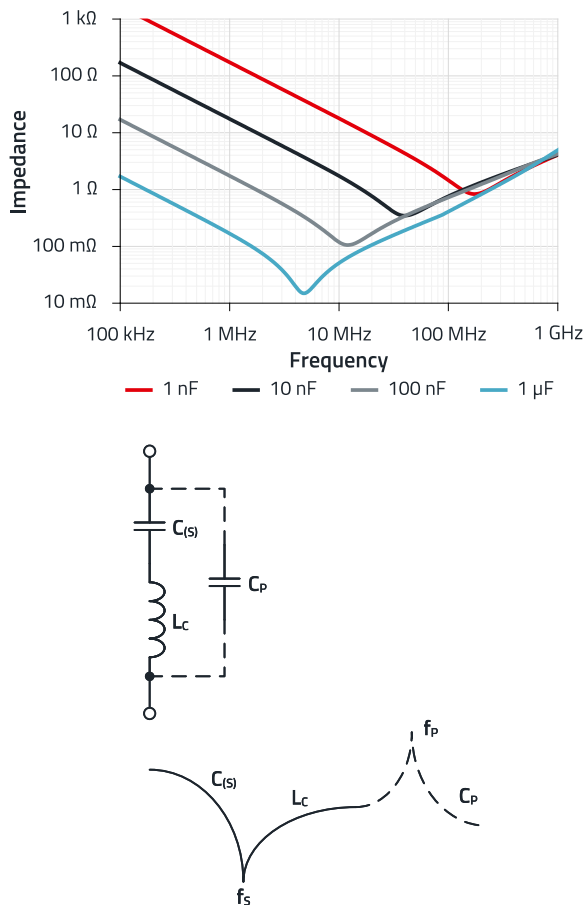


Figure 15: The capacitor with its parasitic properties (simplified).

Depending on the package and dielectric, the capacitor has a series resonance that can already occur at a few MHz. Furthermore, the capacitor has a second resonance, whose frequency is significantly higher, however. Typical SMT 0805 package capacitors with X5R ceramic of 100 nF have their series resonance at approx. 500 MHz and their parallel resonance at 1.5 GHz.

The T-filter constructed this way for the supply voltage has a high insertion loss. The T-circuit was therefore chosen, because it has to be assumed that both the source, as well as the sink, in the power supply area are of low impedance. This gives rise to an optimal mismatch and therefore maximum suppression.

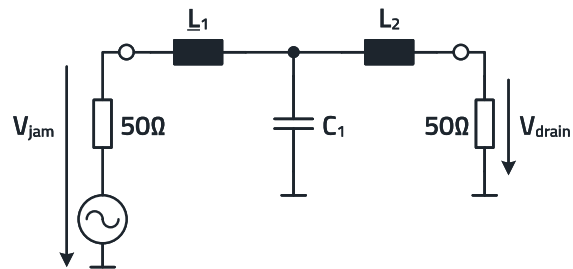In Figure 16 the theoretically possible insertion loss is calculated for the example of a 50 Ω system. There is a maximum attenuation of 70 dB at 100 MHz. This should be sufficient even for the toughest of situations. Figure 16 and equation (4) - equation (7) show the calculation of the insertion loss of the T-filter in the supply voltage.




Assumption: source, drain = 50 Ω

L<sub>1</sub>, L<sub>2</sub>: 600 Ω @ 100 MHz

$$C_1: 680 \text{ nF} = \frac{1}{2\pi f \cdot 680 \cdot 10^{-12} \text{ } \Omega} \quad (4)$$

@ 100 MHz → 2.3 Ω

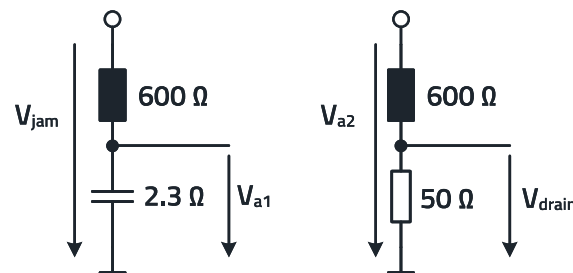

$$a_1 = 20 \cdot \log\left(\frac{2.3}{600 + 2.3}\right) = 48 \text{ dB} \quad (5)$$

$$a_2 = 20 \cdot \log\left(\frac{50}{600 + 50}\right) = 22 \text{ dB} \quad (6)$$

$$a_{\text{ges}} = 48 \text{ dB} + 22 \text{ dB} = 70 \text{ dB} \quad (7)$$

Figure 16: Calculation of the insertion loss of the T-filter in the supply voltage.



# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### Data line filter

The current-compensated choke [744232090](#) is the heart of the data line filter. On account of its winding technology and the few windings, the choke has a high degree of symmetry and low parasitic capacitances. A high insertion loss can be attained as a result of the high permeability of the ferrite material. The structure is shown in Figure 17, the most important parameters are given in Table 3.

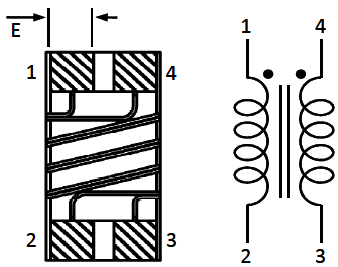


Figure 17: Current-compensated choke [744232090](#) for the data line filter.

The impedance curve of the choke in common and differential mode is presented in Figure 18.

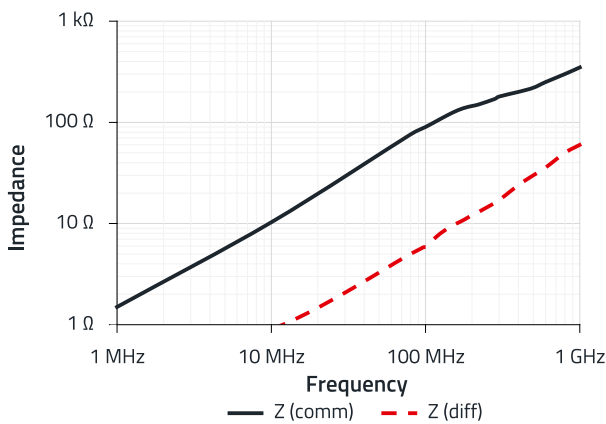


Figure 18: Impedance curve of current-compensated choke [744232090](#).

It is its common mode or asymmetrical suppression that takes effect if the same interference components are on D+ and D- with respect to ground.

This is always the case for capacitive or inductive coupling on the circuit or its conductor tracks. So this impedance component must be as high as possible. At 100 MHz the choke has around 90 Ω. The differential mode impedance is the impedance compensated by the winding structure. "In one branch the current goes in - in the other out again", which is how current compensation should arise and the useful signal sees this impedance. This impedance must be as small as possible. All components of this impedance arise from asymmetries in the set-up and due to losses in the material from eddy currents and the skin effect. At 100 MHz this choke has a differential mode impedance of 6 Ω (both windings together).

Now to the filter capacitors that form a low-pass 2nd order filter in the output of the filter. A diode array is used here instead of capacitors. The integrated diodes also have a capacitance, a parasitic capacitance, which we make use of here. In addition, the parasitic inductance of the TVS diodes in the array is very low. This has to be the case, as otherwise a short response time to the overvoltage transients cannot be attained. So we combine an almost ideal capacitor with effective transient protection.

Properties	Test cond.		Value	Unit	Tol.
Impedance	100 MHz	Z	90	Ω	± 25%
Rated voltage		U <sub>R</sub>	50	V	max.
Rated current	ΔT = 40 K	I <sub>R</sub>	370	mA	max.
R <sub>DC</sub>	@ 20 °C	R <sub>DC</sub>	0.30	Ω	max.

Table 3: Electrical characteristics of current-compensated choke [744232090](#).

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

The most important electrical characteristics and the structure of the array are presented in Figure 19 and Table 4.

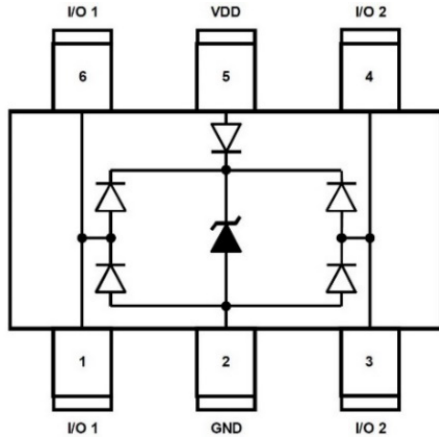


Figure 19: The structure of the diode array WE-TVS [82400102](#).

The interference signal attenuation can also be calculated for this filter; assuming that the interference occurs at both signal wires in the same amplitude and phase angle, the calculation in Figure 20 and equation (8) - equation (10) applies.

$$C_x = 6.6 \text{ pF} \quad (8)$$

$$X_C = \frac{1}{j\omega C} = 240 \Omega @ 100 \text{ MHz} \quad (9)$$

$$a = 20 \cdot \log\left(\frac{100}{240 + 100}\right) = 10.6 \text{ dB} \quad (10)$$

Here the attenuation is 10 dB at 100 MHz. Even this is sufficient, as the interference components can be assumed to be lower than on the power supply connection and the useful signal should not be affected. Every capacitance to ground acts as a signal load of half capacitance.

Properties	Test conditions	Value typ.	Value max.	Unit
$C_{IO}$	$V_{Pin5} = 5 \text{ V}, V_{Pin2} = 0 \text{ V}, V_{IO} = 2.5 \text{ V}, f = 100 \text{ MHz}, I/O \text{ to GND}$	2.0	2.5	pF
$C_x$	$V_{Pin5} = 5 \text{ V}, V_{Pin2} = 0 \text{ V}, V_{IO} = 2.5 \text{ V}, f = 100 \text{ MHz}, I/O \text{ to GND}$	0.4	0.6	pF

Table 4: Electrical characteristics of the diode array WE-TVS [82400102](#).

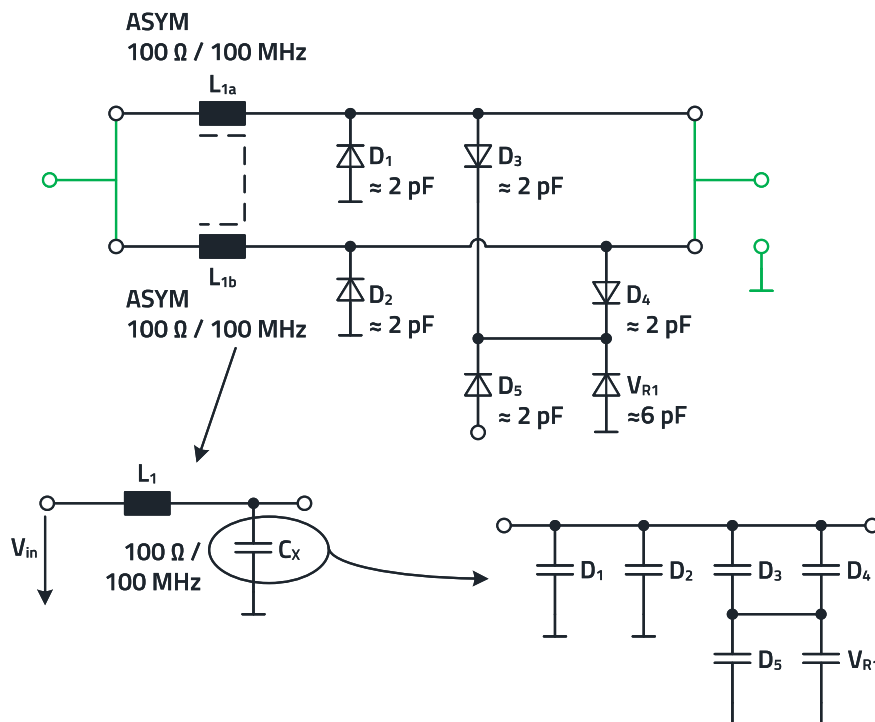


Figure 20: The insertion loss of the USB data line filter.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### Layout

The circuit board with its conductor tracks is an arrangement of components with capacitances and inductances. The layout therefore has to be developed according to the circuit requirements. A simple LC low-pass filter can be significantly impaired in its effectiveness by an unfavorable layout.

Figure 21:

What is wrong with the layout in Figure 20?

- The ground connection to the capacitor is too long. 1 cm of track corresponds to 6 - 10 nH.
- The ground connection should pass directly to the housing, as the ground reference of the cable shielding and the ground reference of the filter must lie on the same HF potential.
- A stub line to the capacitor passes between the inductor and capacitor. This stub line is an additional inductance in series with the capacitor and, as a result of the higher reactance of the inductance with increasing frequency, renders the capacitor ineffective.
- The filter input and filter output couple inductively with each other. The filter is short-circuited with increasing frequencies.

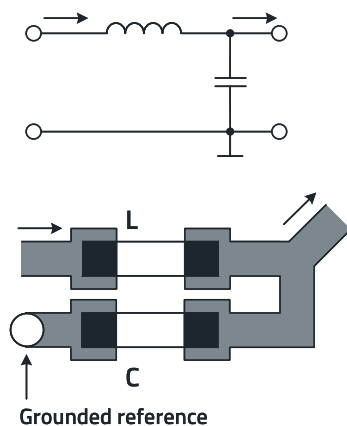


Figure 21: Example of a low-pass filter for high frequencies with an unfavorable layout.

- The components couple capacitively as they are located parallel to one another. Here too, the coupling is greater with increasing frequency.
- The corrected layout with the associated HF-compatible arrangement is shown in Figure 22.


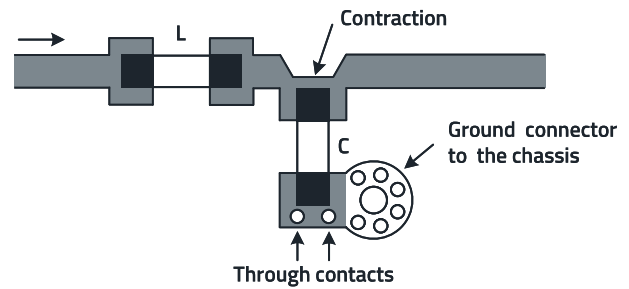


Figure 22: HF-optimized layout of an LC filter.

What is right with the layout in Figure 22?

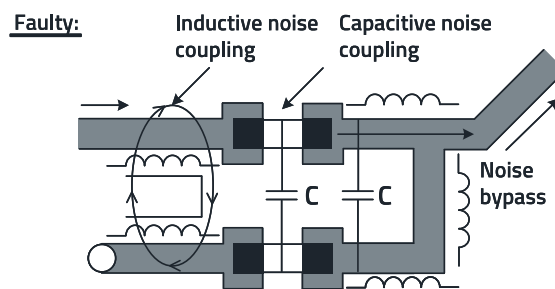- The contraction prevents that interference current is bypassed at the capacitor. The capacitor "lies" in the signal path.
- The rectangular arrangement of the components prevents mutual coupling.
- The short ground connection at the capacitor, which is of low impedance as a result of two through-contacts, offers an ideally HF-passivated reference point for the capacitor.



# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### 5.3 The Würth Elektronik eiSos USB 2.0 EMC Application Board

All the points discussed so far have been considered in the USB Application Board.

The data lines are routed symmetrically, all ground connections have the shortest connection to the chassis and the circuit board also has a ground plane. The empty space, also around the components, has been filled with compound in order to reduce coupling between the tracks and between the components. All ground connections are provided with at least two through-contacts. The layout and both sides of the circuit board are presented in Figure 23. Figure 24 shows the resulting USB dongle; the circuit diagram corresponds to that in Figure 13, the layout to that in Figure 23.


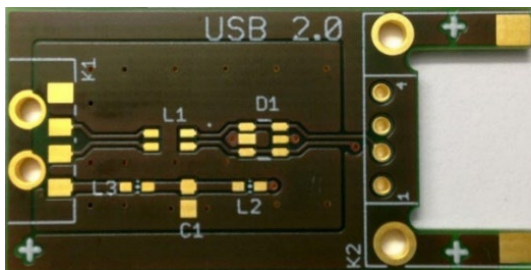


Figure 23: Layout and component side of the EMC Application Board for USB.

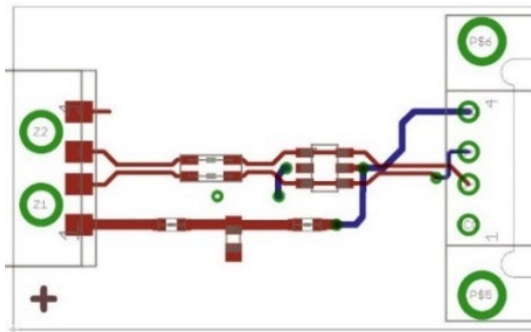

Figure 24: USB Dongle, closed and opened, layout according to Figure 23, circuit diagram according to Figure 13.

The optimal connection of the reference and chassis ground is clearly identifiable from the USB receptacles. It is obvious that this ground reference is only ensured if the USB receptacles of the device (PC) are of low impedance, connected directly to the chassis and the USB cable is also shielded, as described previously.

The following curves in Figure 25, Figure 26, Figure 27 show (from top to bottom) the insertion loss of the power supply filter, the common mode and differential mode impedance of the data line filter and the transient limitation of the data line filter.

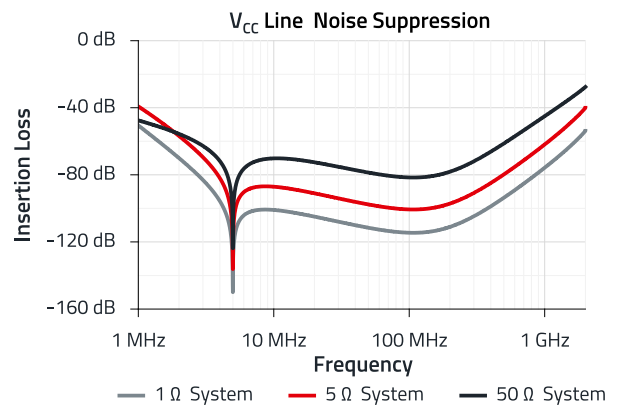


Figure 25: Insertion loss of the power supply filter.

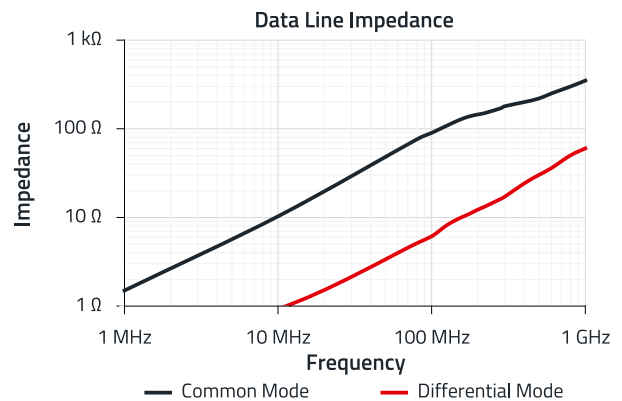


Figure 26: Impedance of the data line filter, common and differential mode.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

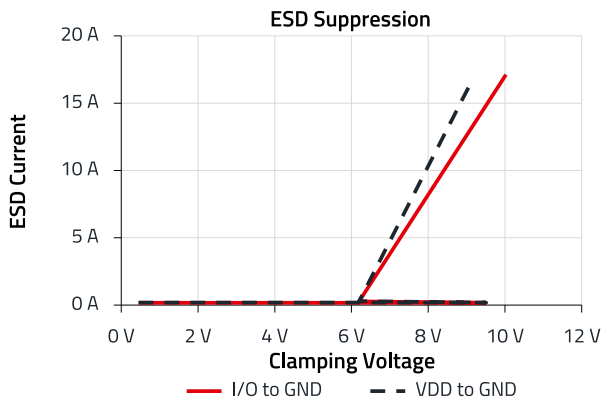


Figure 27: Voltage limitation of the data line filter against transient interference, such as bursts and ESD.

The filter is usually integrated on the controller board within the device. Würth developed the EMC Application Dongle in order to facilitate the engineer's circuit development and to be in a position to evaluate effectiveness. Despite an optimal layout and ground connection to the USB receptacles, the dongle requires an HF-compatible ground connection from the USB receptacles to the PC on the one hand, and to the cable on the other. The reason is that the  $V_{CC}$  filter capacitor (Figure 13) and the overvoltage diodes have to dissipate their HF interference currents and possibly transient interference currents; this only works against ground or the chassis. Figure 28 shows the set-up.

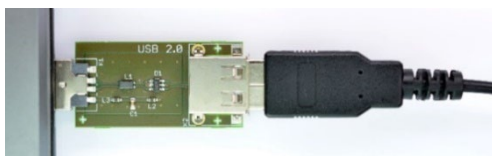


Figure 28: Use of the EMC USB dongle.

Used in this way, as a signal source for a PC and as a peripheral device, a USB hard drive emits an interference emission spectrum as in Figure 29.

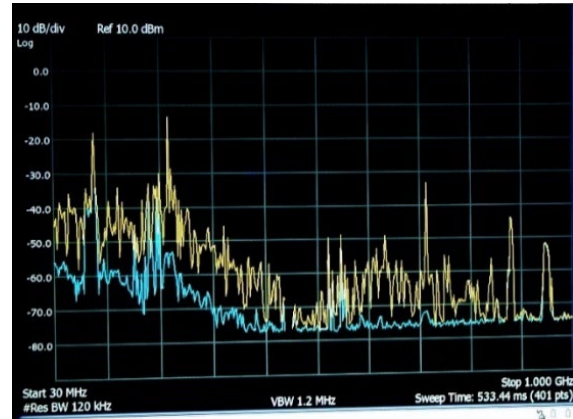


Figure 29: Interference emission spectrum on D+ before and after the data line filter.

The yellow curve shows the interference spectrum on D+ in front of the filter, the blue curve behind it. The interference is reduced by up to 35 dB. The magnitude of suppression is strongly dependent on the impedance of the interference source, which depends of the type of coupling, i.e. capacitive, inductive or radiated. The higher the impedance of the interference source, the more effectively the filter works. Interference sources that are on the ground system of the device cannot be reduced by a filter, of course, as there is no corresponding reference or grounding point.

Figure 30 shows the interference spectrum before and after the power supply filter.

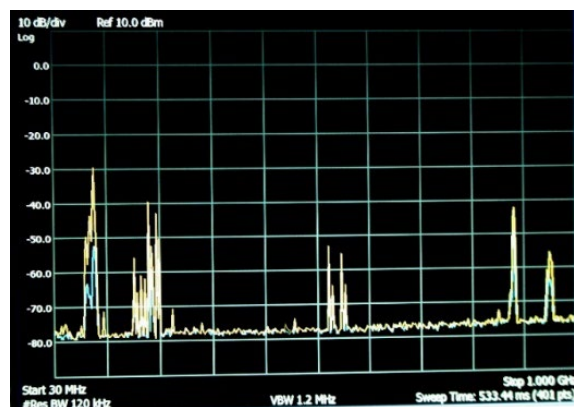


Figure 30: Interference emission spectrum on the power supply line before and after the data line filter.

A reduction in interference of around 20 dB is apparent here too.

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### 5.4 The USB 2.0 EPLE jack with integrated filter

Filter design has its pitfalls, as shown from numerous practical examples. All these pitfalls are controllable, but framework conditions, such as space requirements, the mechanical concept and many others, often do not permit "good" filter design. Retrofitting a filter, e.g. following EMC approval measurements, also frequently turns out to be costly and time-consuming.

That is why Würth Elektronik offers a USB jack with integrated USB filter (see Figure 31).

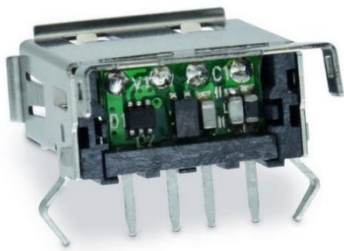


Figure 31: USB receptacle with integrated EMC filter.

The most important technical data:

- ESD and overvoltage protection to < 10 V for 15 kV discharge voltage
- Common mode data line attenuation to 90 Ω at 100 MHz of > 10 dB (dependent on the source and sink impedance)

- Attenuation at the voltage supply at 100 MHz: > 40 dB (dependent on the source and sink impedance), the filter attenuates reliably up to over 1 GHz

The filter is therefore outstandingly shielded and has an optimal ground reference. In addition, the extremely small package strongly reduces coupling between the components and conductor tracks in the useful frequency range up to 1 GHz. By simply replacing existing unfiltered receptacles with these makes the application extremely convenient and shows immediate effect.

### 6. SUMMARY

EMC without filters is no longer possible in today's circuit technology. Electronics in tight spaces, useful frequencies up into the GHz range and also consideration of the EMC standards necessitate their use. EMC is not "nice to have" or to satisfy the regulations and standards, but is a quality feature for which the user of the product has a right. Nevertheless, EMC is often an engineering challenge and a balancing act between performance and time. Würth Elektronik would like to present you with the necessary components, as well as the necessary expertise to support you in optimally designing the USB interface. We hope to have done this with the products introduced and this brief technical article and wish you every success with your next design.

### 7. BILL OF MATERIALS

Description	Package	Electrical specification	Order code
WE-CBF EMI ferrite bead	EIA 0603	$Z = 600 \Omega$ ; $I_R = 1 \text{ A}$ ; $R_{DC} = 0.2 \Omega$	<a href="#">742792651</a>
WE-CNSW CM choke	1206	$Z = 90 \Omega$ ; $I_R = 370 \text{ mA}$ ; $R_{DC} = 0.3 \Omega$	<a href="#">744232090</a>
WE-TVS High Speed	SOT23-6L	$V_{RWM} = 5 \text{ V}$ ; 4+1 channel; $C_{Ch} = 2 \text{ pF}$	<a href="#">82400102</a>
WCAP-CSGP	0603	X7R; 680 nF $\pm 10\%$ ; 16 V	<a href="#">885012206051</a>
EMC USB adapter	USB A-A	USB 2.0, 90 $\Omega_{Diff}$ ; 1 A; ESD+EMI protected	<a href="#">8299995TICK</a>
WE-USBH EPLE connector	USB A	USB 2.0, 90 $\Omega_{Diff}$ ; 1 A; ESD+EMI protected	<a href="#">8492121</a>

# APPLICATION NOTE

## ANP024 | The USB Interface from EMC Point of View

### IMPORTANT NOTICE

The Application Note is based on our knowledge and experience of typical requirements concerning these areas. It serves as general guidance and should not be construed as a commitment for the suitability for customer applications by Würth Elektronik eiSos GmbH & Co. KG. The information in the Application Note is subject to change without notice. This document and parts thereof must not be reproduced or copied without written permission, and contents thereof must not be imparted to a third party nor be used for any unauthorized purpose.

Würth Elektronik eiSos GmbH & Co. KG and its subsidiaries and affiliates (WE) are not liable for application assistance of any kind. Customers may use WE's assistance and product recommendations for their applications and design. The responsibility for the applicability and use of WE Products in a particular customer design is always solely within the authority of the customer. Due to this fact it is up to the customer to evaluate and investigate, where appropriate, and decide whether the device with the specific product characteristics described in the product specification is valid and suitable for the respective customer application or not.

The technical specifications are stated in the current data sheet of the products. Therefore the customers shall use the data sheets and are cautioned to verify that data sheets are current. The current data sheets can be downloaded at [www.we-online.com](http://www.we-online.com). Customers shall strictly observe any product-specific notes, cautions and warnings. WE reserves the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services.

WE DOES NOT WARRANT OR REPRESENT THAT ANY LICENSE,

EITHER EXPRESS OR IMPLIED, IS GRANTED UNDER ANY PATENT RIGHT, COPYRIGHT, MASK WORK RIGHT, OR OTHER INTELLECTUAL PROPERTY RIGHT RELATING TO ANY COMBINATION, MACHINE, OR PROCESS IN WHICH WE PRODUCTS OR SERVICES ARE USED. INFORMATION PUBLISHED BY WE REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE A LICENSE FROM WE TO USE SUCH PRODUCTS OR SERVICES OR A WARRANTY OR ENDORSEMENT THEREOF.

WE products are not authorized for use in safety-critical applications, or where a failure of the product is reasonably expected to cause severe personal injury or death. Moreover, WE products are neither designed nor intended for use in areas such as military, aerospace, aviation, nuclear control, submarine, transportation (automotive control, train control, ship control), transportation signal, disaster prevention, medical, public information network etc. Customers shall inform WE about the intent of such usage before design-in stage. In certain customer applications requiring a very high level of safety and in which the malfunction or failure of an electronic component could endanger human life or health, customers must ensure that they have all necessary expertise in the safety and regulatory ramifications of their applications. Customers acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of WE products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by WE.

CUSTOMERS SHALL INDEMNIFY WE AGAINST ANY DAMAGES ARISING OUT OF THE USE OF WE PRODUCTS IN SUCH SAFETY-CRITICAL APPLICATION.

### USEFUL LINKS



Application Notes  
[www.we-online.com/appnotes](http://www.we-online.com/appnotes)



**REDEXPERT** Design Platform  
[www.we-online.com/redexpert](http://www.we-online.com/redexpert)



Toolbox  
[www.we-online.com/toolbox](http://www.we-online.com/toolbox)



Product Catalog  
[www.we-online.com/products](http://www.we-online.com/products)

### CONTACT INFORMATION



[appnotes@we-online.com](mailto:appnotes@we-online.com)  
Tel. +49 7942 945 - 0



Würth Elektronik eiSos GmbH & Co. KG  
Max-Eyth-Str. 1 74638 Waldenburg Germany  
[www.we-online.com](http://www.we-online.com)