

ANOTHER CONDUCTED EMISSIONS DEMO?

Farid Jamialahmadi
Technical Academy – Applications Engineer

AGENDA

- Fundamentals of conducted emissions
- Test Setup (Flyback board, load, LISN, ground plane, test receiver)
- CMC Selection
 - Comparison of different core materials
- X Capacitors
- Y Capacitors
- Will the filter design pass?



Electromagnetic Compatibility

Emission



Immunity

Conducted

Radiated


Conducted

Radiated

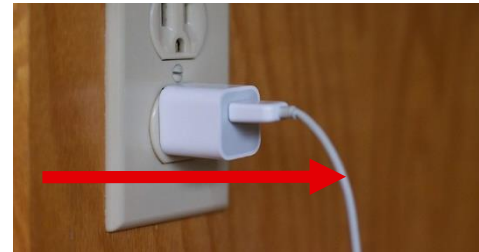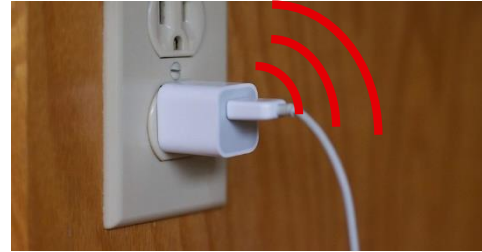


CONDUCTED EMISSIONS LIMITS

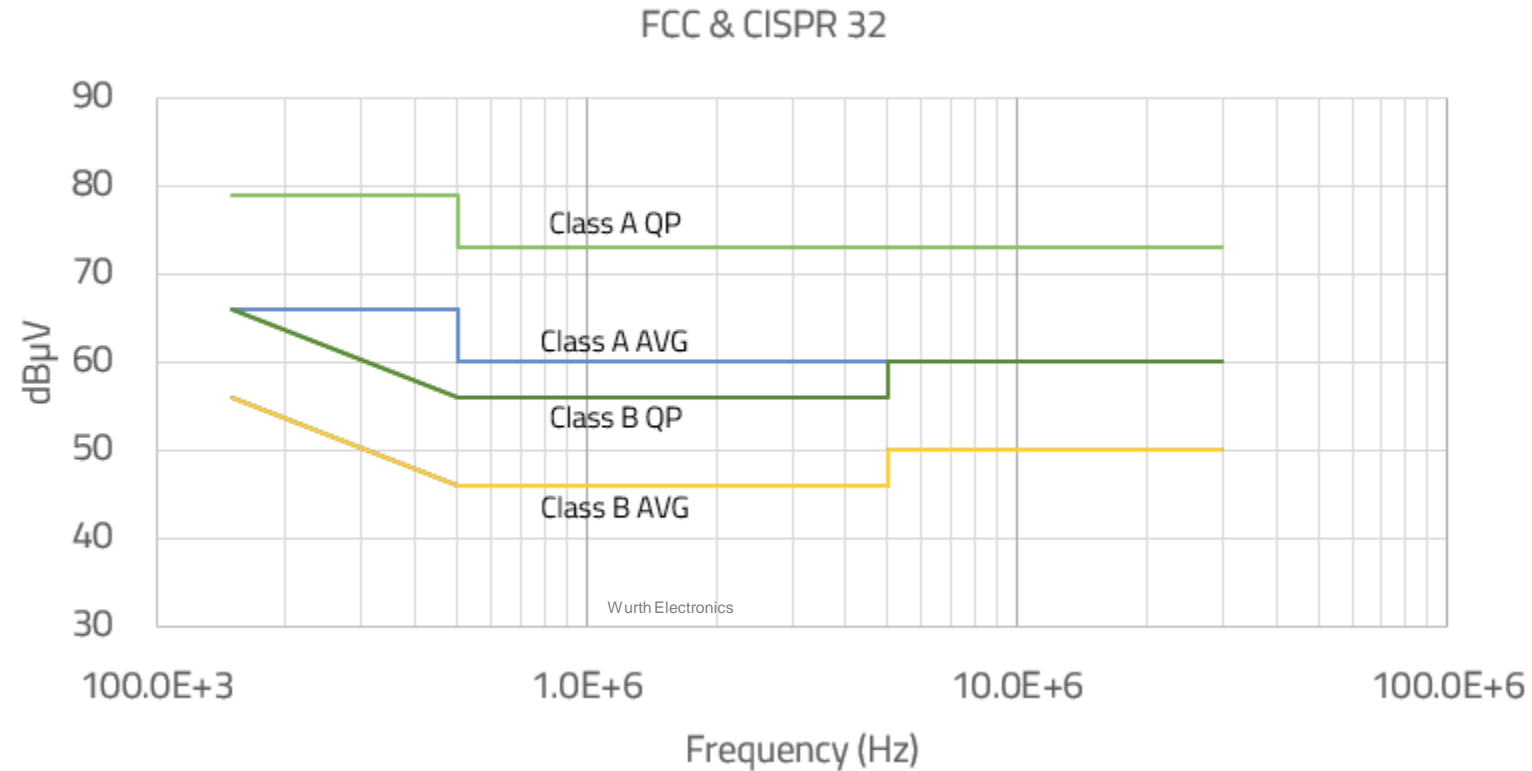- Limit lines shown for Quasipeak and average.
- Why Care?
 - If you want to sell your product, you will need to comply with these limits otherwise you could face large financial penalties. Ignorance is not a defense!




TEST SETUP

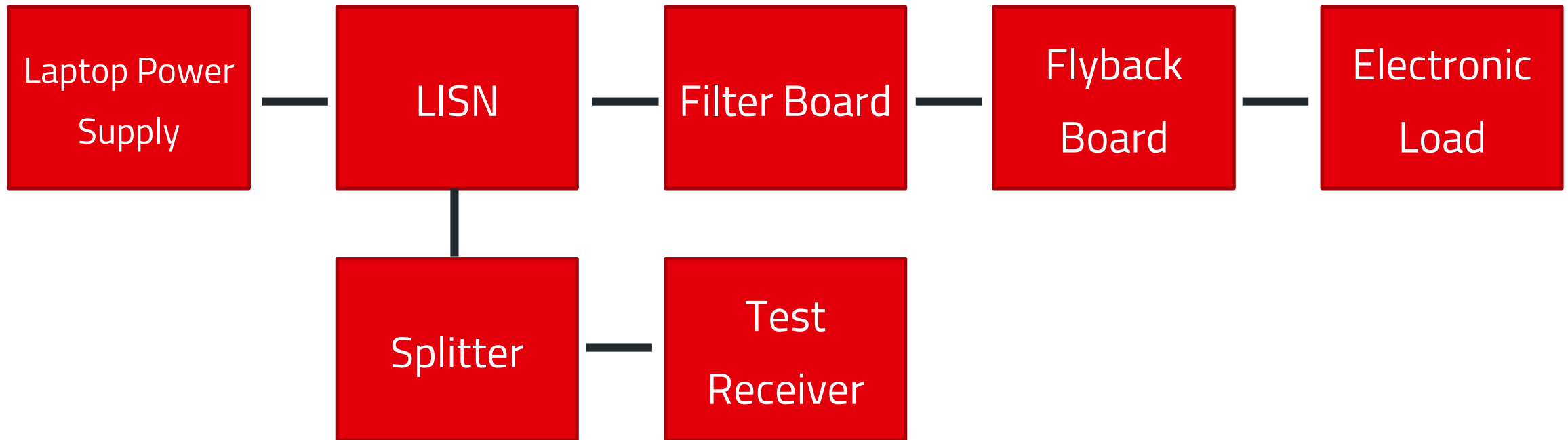

Picture Caption

FLYBACK BOARD

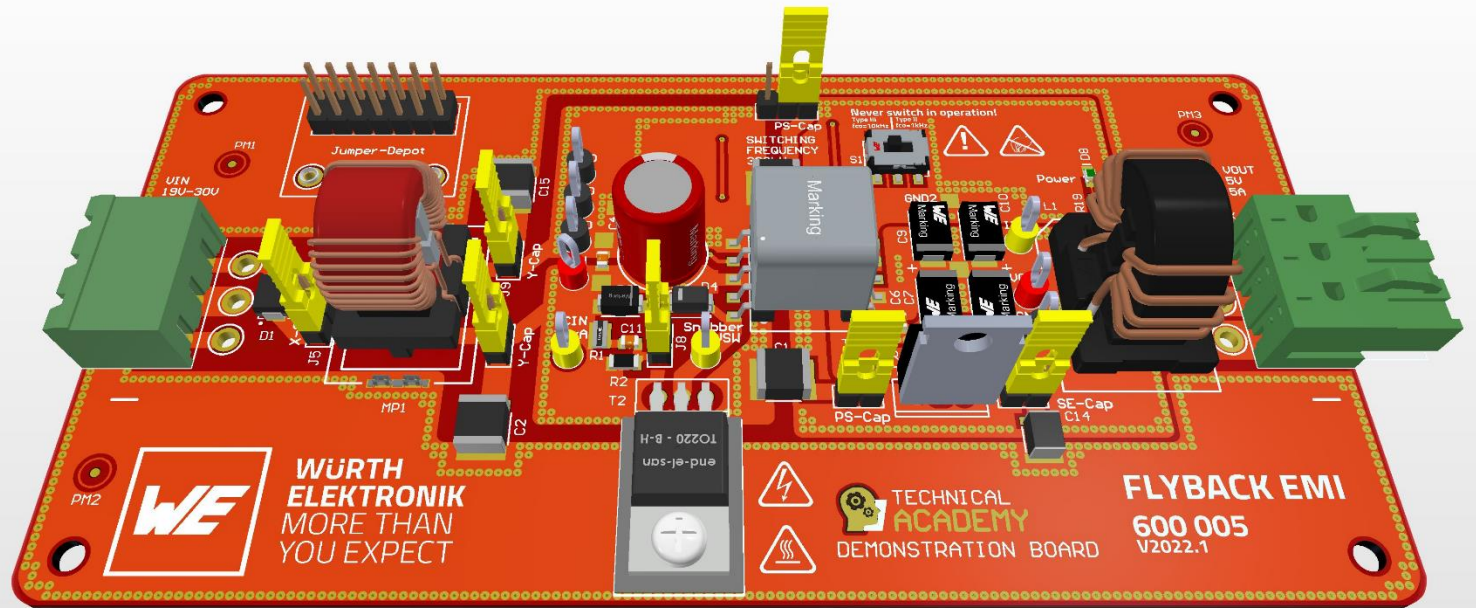
- DC/DC Flyback-Converter CCM (Continuous Conduction Mode)
 - $U_{in} = 19V (19-30V)$
 - $U_{out} = 5V$
 - $I_{out,max} = 4A (20W)$
 - $f_{sw} \approx 300kHz$
 - Efficiency $\approx 90\%$
- IC: ADP1071-2 (Analog Devices)
 - with synchronous rectifier
- Transformer: 749119550
- MOSFETs in TO220-package



Würth Electronics


BASIC CONCEPTS

- Differential Mode
- Common Mode

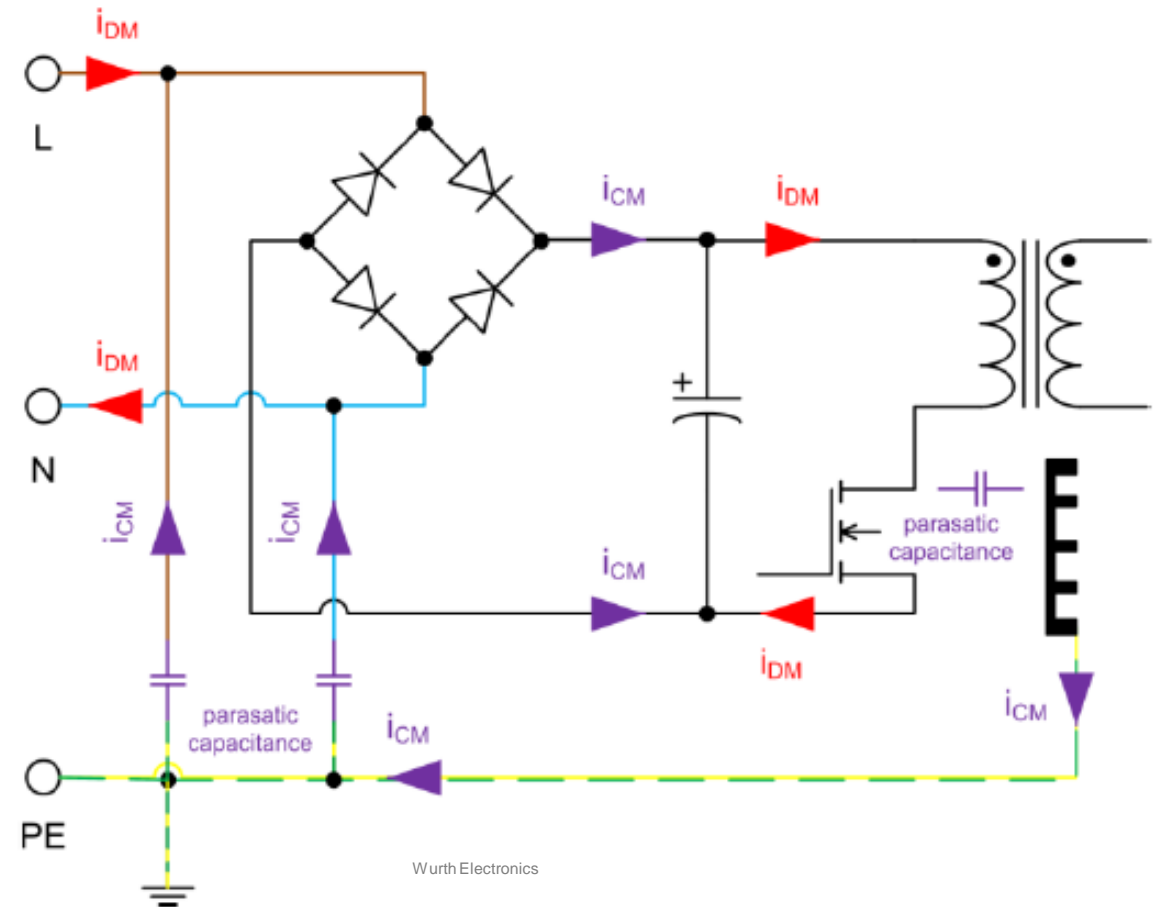


BASELINE TEST

BLUE IS CM AND RED IS DM

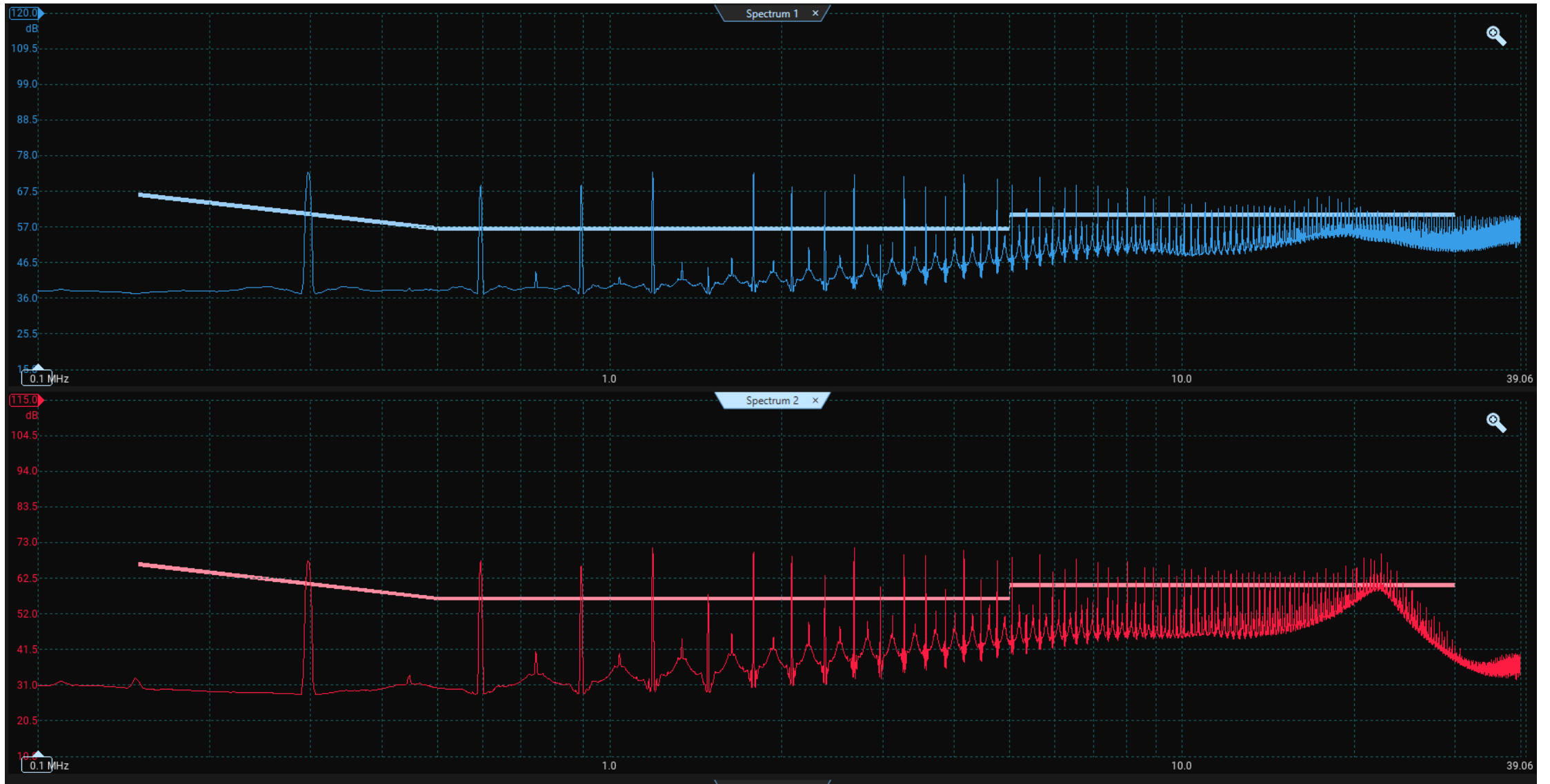

BASIC LINE FILTER

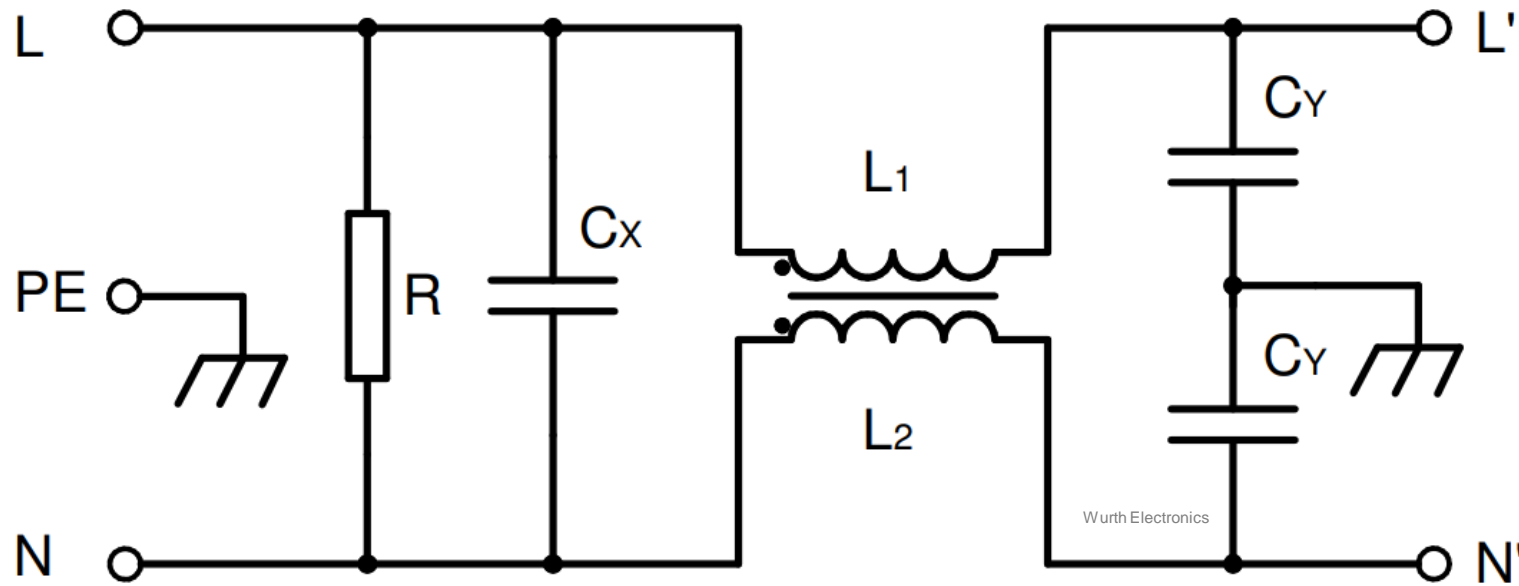

Add varistor between Line and Neutral for overvoltage protection!


CMC SELECTION



WHAT IS A COMMON MODE CHOKE?

- It is a Bi-directional filter
 - From device to outside environment
 - From outside environment to inside device
- Intended Signal - **Differential mode**
- Interference Signal (noise) – **Common Mode**

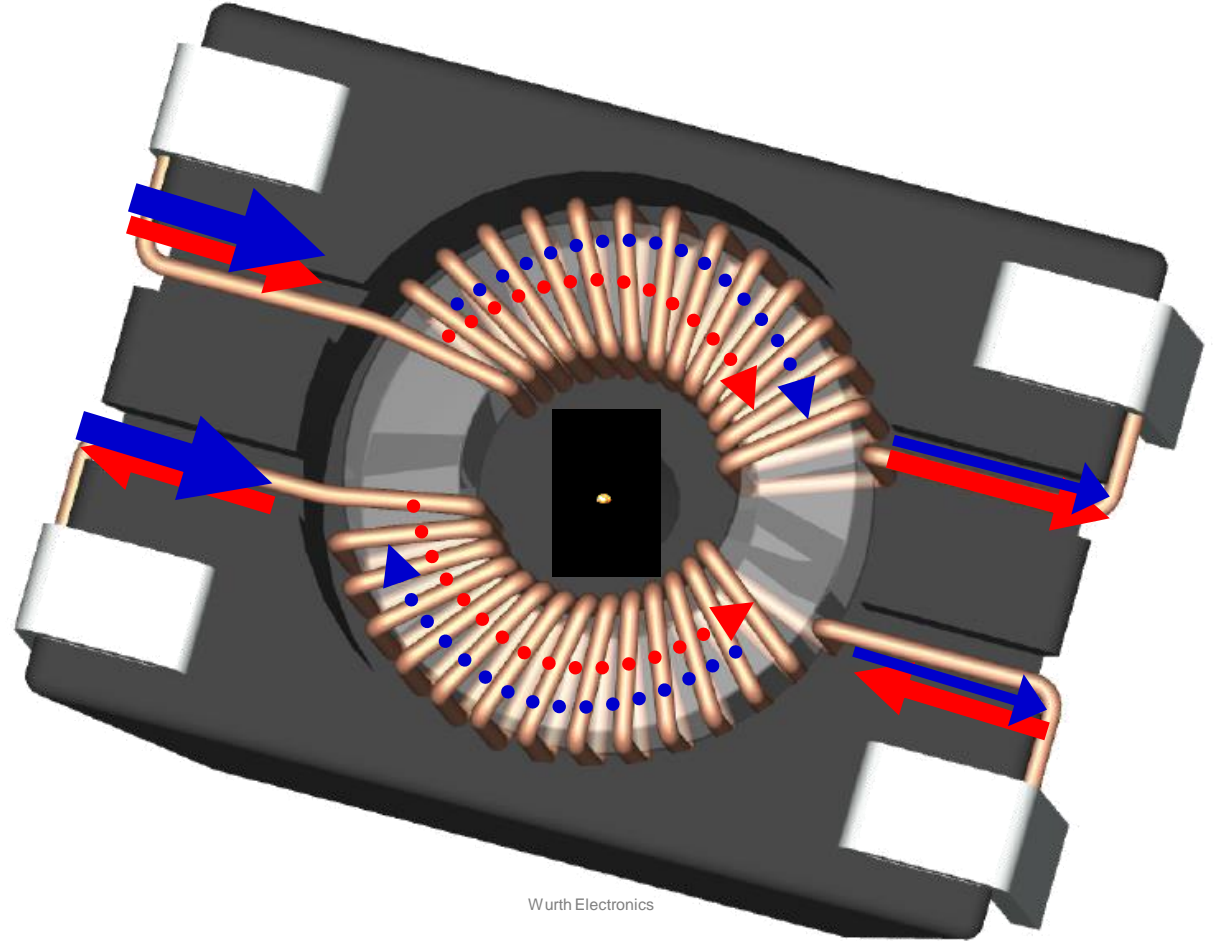- Conclusion:
- “almost” no affect the signal - **Differential mode**
- high attenuation to the interference signal (noise) – **Common Mode**




CHOOSING A CMC






Würth Electronics

bifilar

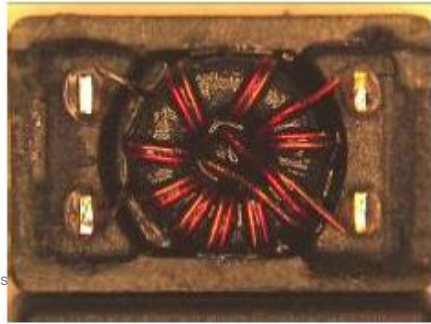


Würth Electronics

sectional

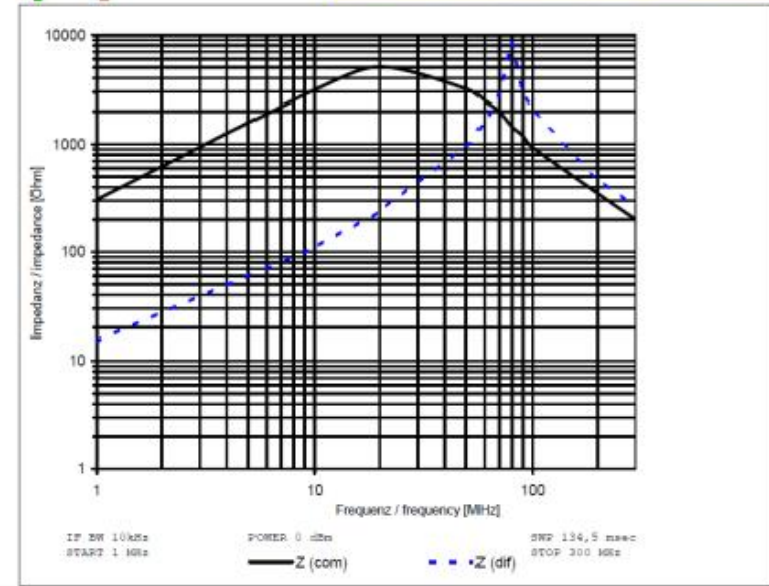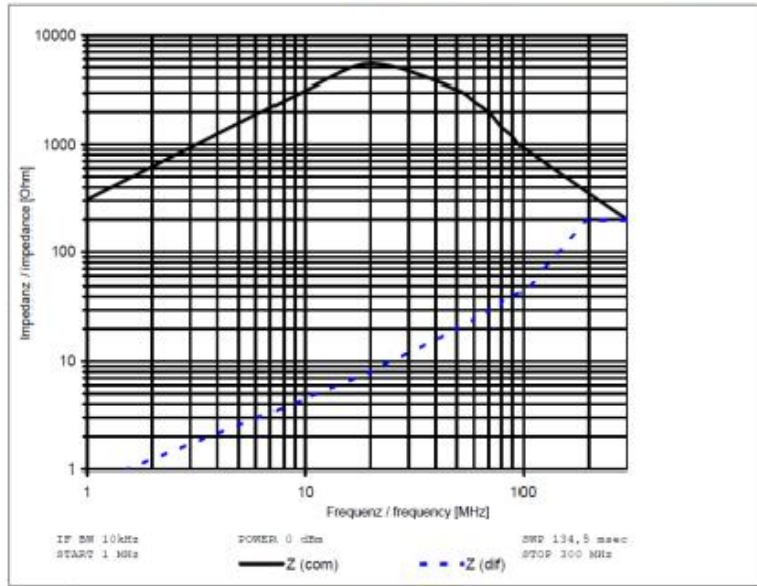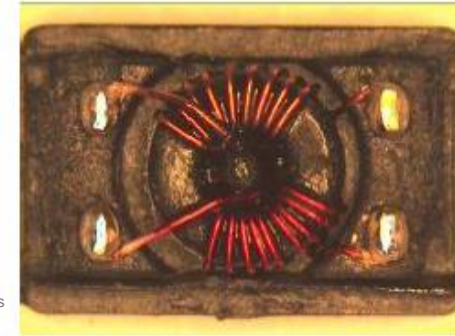


CHOOSING A CMC - CORE MATERIAL

Inductive Part of Impedance


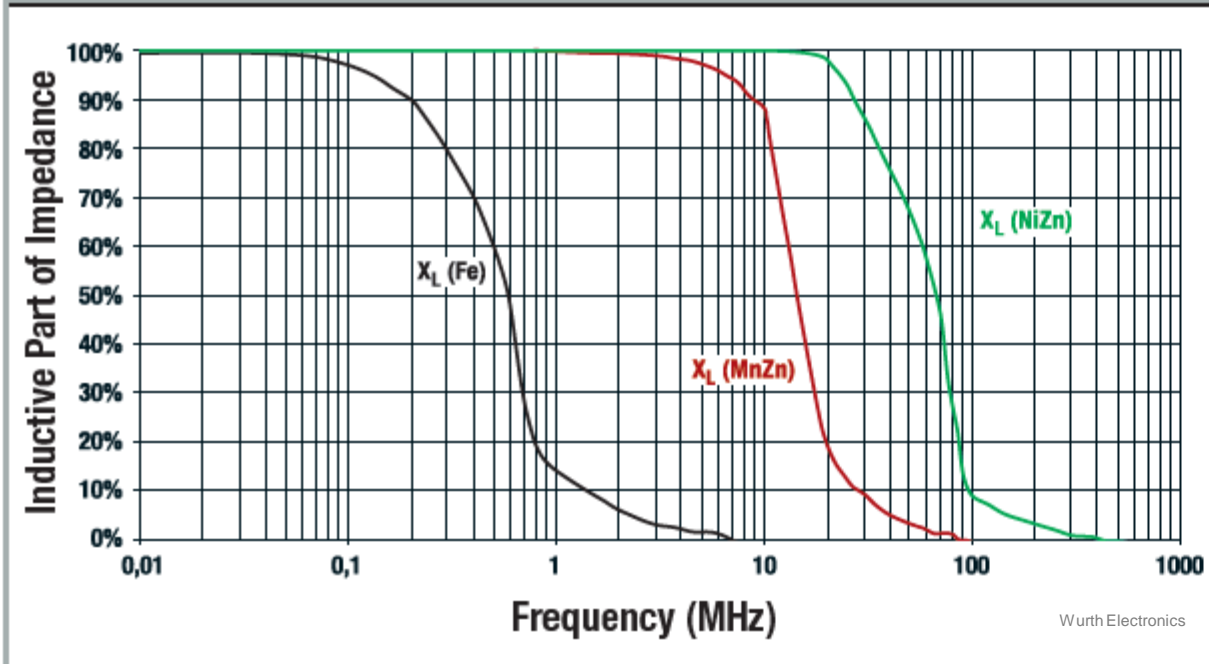


Resistive Part of Impedance

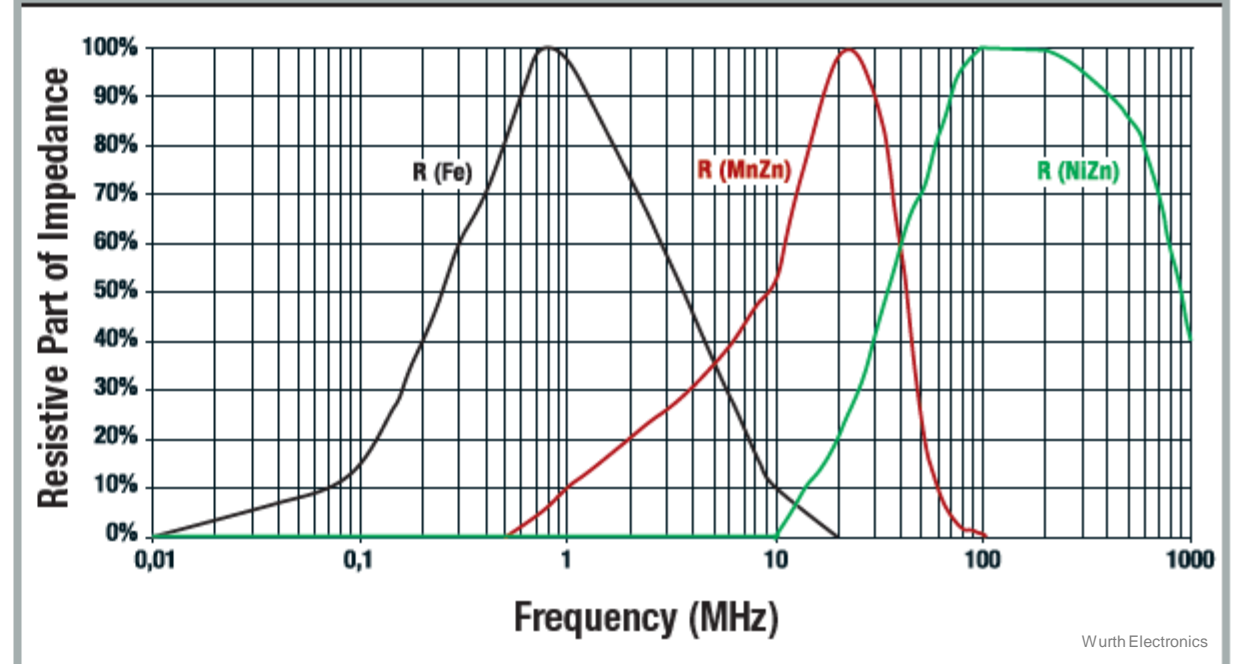

CORE MATERIALS COMPARISON

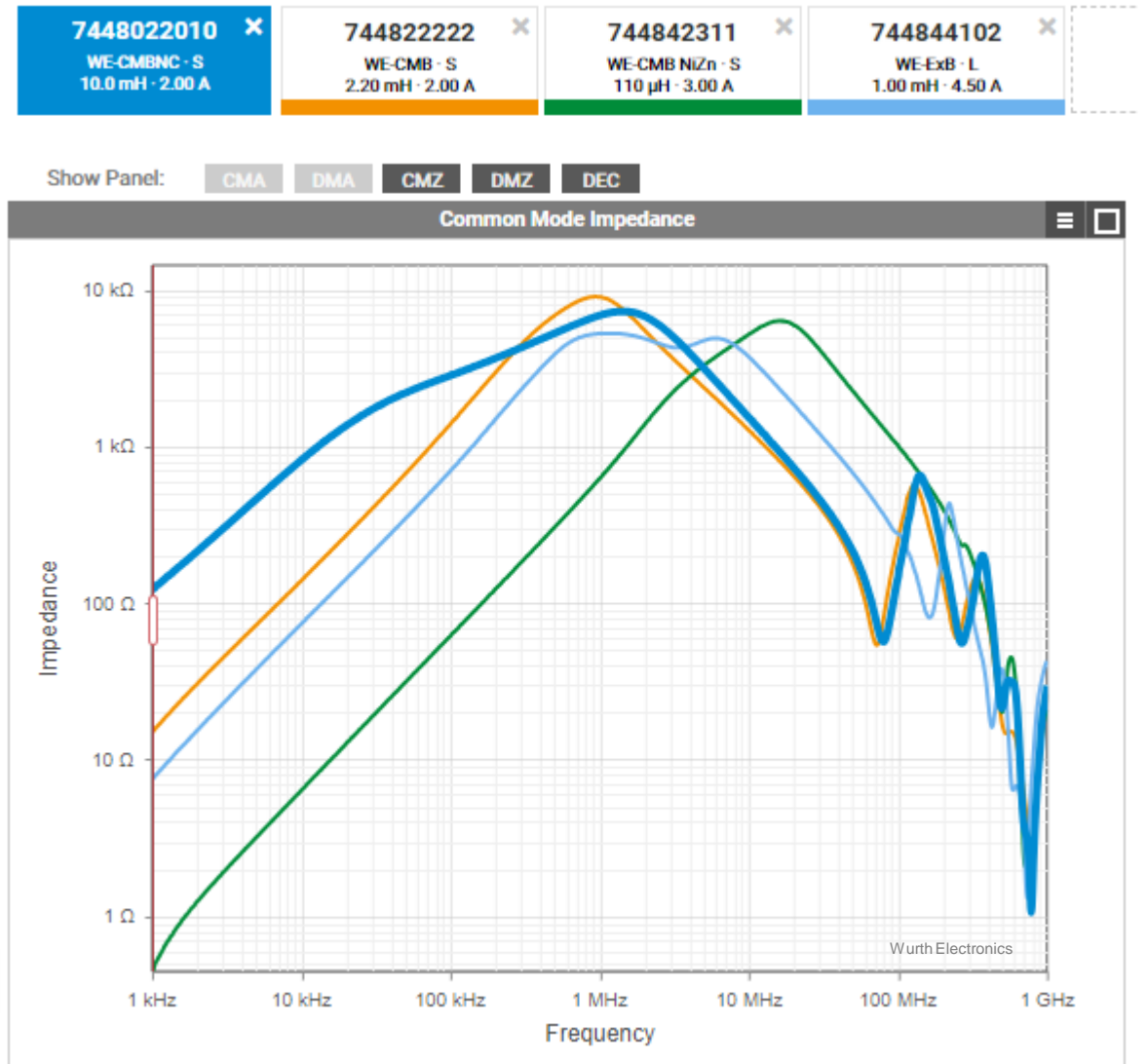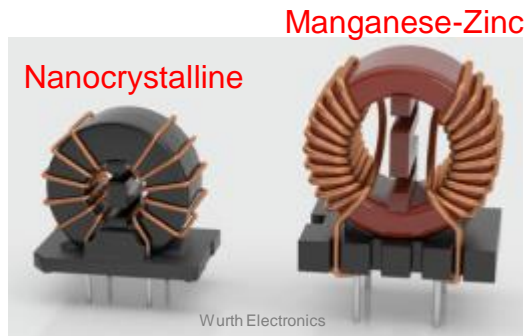- MnZn
- NiZn
- Both together
- Nanocrystalline



Filters: Is selected

System

Order Code	Series	Size	Spec	V _R	L ₀	I _R	Z _{CM, Min @300 kHz}	Lines	T _{op}	V _T	Assembl...	L	W	H	L _s	Certificates
744822222	WE-CMB	S		250 V	2.20 mH	2.00 A	4.48 kΩ	2	125°C	1.50 kV	THT	17.5 mm	13.0 mm	22.0 mm		
744802210	WE-CMBNC	S		250 V	10.0 mH	2.00 A	4.27 kΩ	2	125°C	1.50 kV	THT	18.0 mm	14.0 mm	22.0 mm		
744821201	WE-CMB	XS		250 V	1.00 mH	2.00 A	1.90 kΩ	2	125°C	1.50 kV	THT	15.0 mm	7.50 mm	18.0 mm		
7448012002	WE-CMBNC	XS		250 V	1.60 mH	2.00 A	1.00 kΩ	2	125°C	1.50 kV	THT	14.0 mm	7.50 mm	16.0 mm		
744842311	WE-CMB NiZn	S		250 V	110 μH	3.00 A	183 Ω	2	125°C	1.50 kV	THT	18.5 mm	14.5 mm	22.0 mm		
744841247	WE-CMB NiZn	XS		250 V	47.0 μH	2.00 A	91.1 Ω	2	125°C	1.50 kV	THT	16.0 mm	7.50 mm	17.5 mm		

7448012002 WE-CMBNC - XS 1.60 mH - 2.00 A

744802210 WE-CMBNC - S 10.0 mH - 2.00 A

744821201 WE-CMB - XS 1.00 mH - 2.00 A




744822222 WE-CMB - S 2.20 mH - 2.00 A

744841247 WE-CMB NiZn - XS 47.0 μH - 2.00 A

744842311 WE-CMB NiZn - S 110 μH - 3.00 A

Click and type or drop an Order Code here


Show Panel: CMA DMA CMZ DMZ DEC

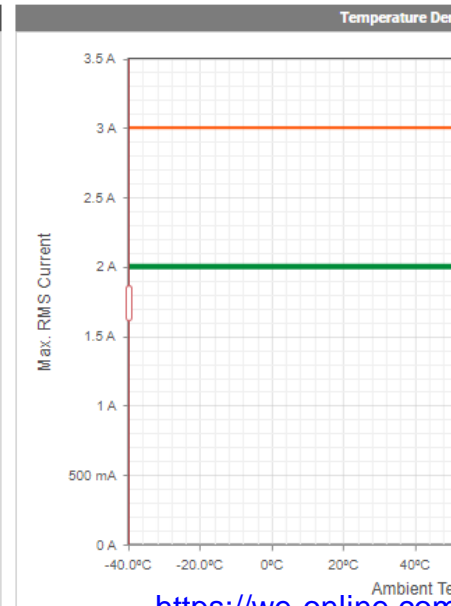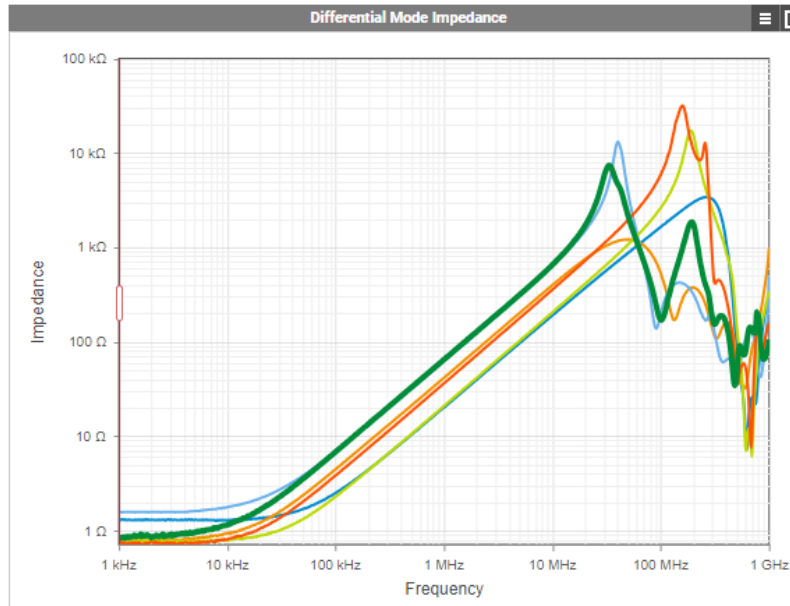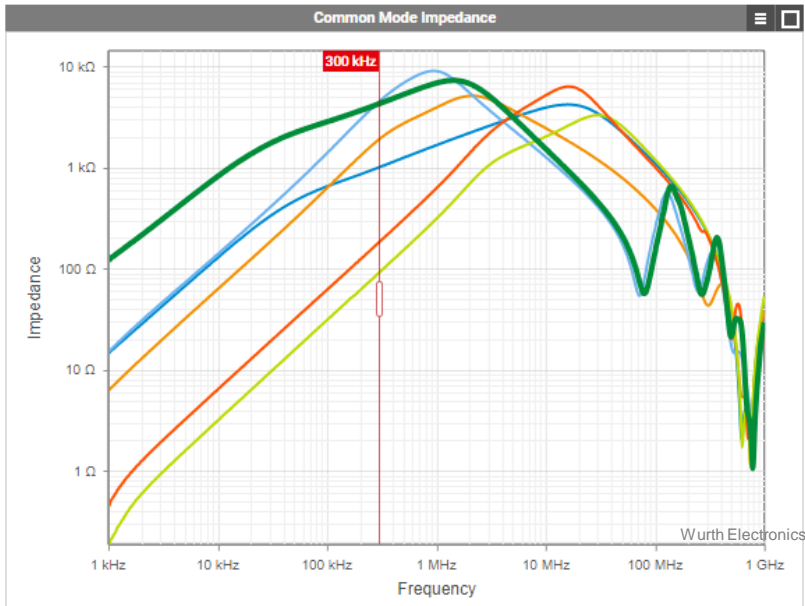

<https://we-online.com/re/5oCBbSaH>

CMC DEMO

BLUE IS CM AND RED IS DM


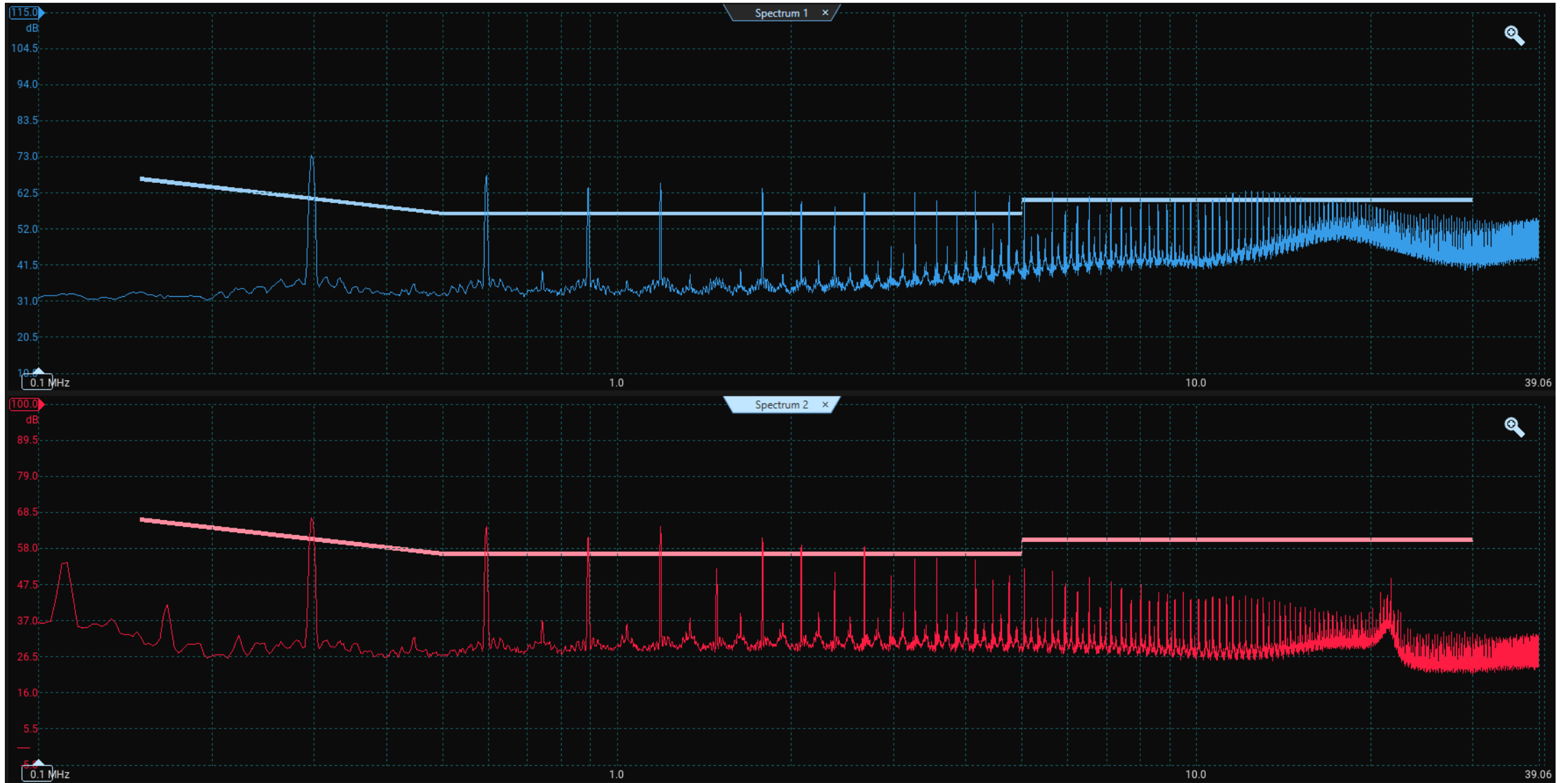


X CAPACITOR SELECTION



X CAPACITORS

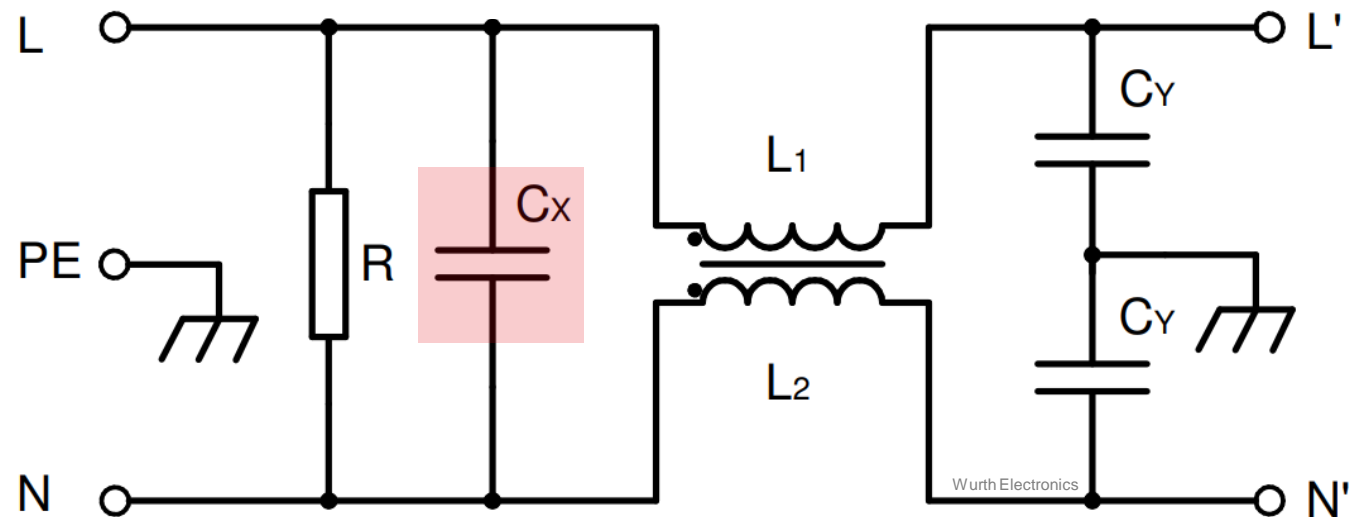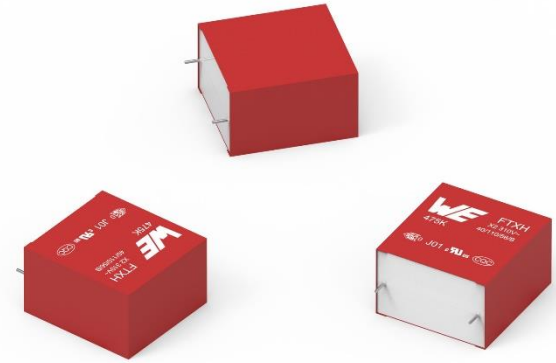- X capacitors are meant to filter differential noise.
- Need to meet special safety criteria since they are connected to between line and neutral.
- X1 - Peak Impulse 4 kV
- X2 – Peak Impulse 2.5 kV
- X class capacitors can be substituted by Y class capacitors of the same or higher voltage rating.



CALCULATING X CAPACITOR VALUE

Estimating Differential (Leakage) Inductance


$$\blacksquare f_{DM} = \frac{1}{2\pi\sqrt{L_{DM}\cdot C_x}}$$

$$\blacksquare C_x = \frac{1}{(2\pi\cdot f_{DM})^2\cdot L_{DM}} = \frac{1}{(2\pi\cdot 25kHz)^2\cdot 10mH\cdot 0.025}$$

$$\blacksquare C_x = 162nF$$

X capacitor DEMO

BLUE IS CM AND RED IS DM

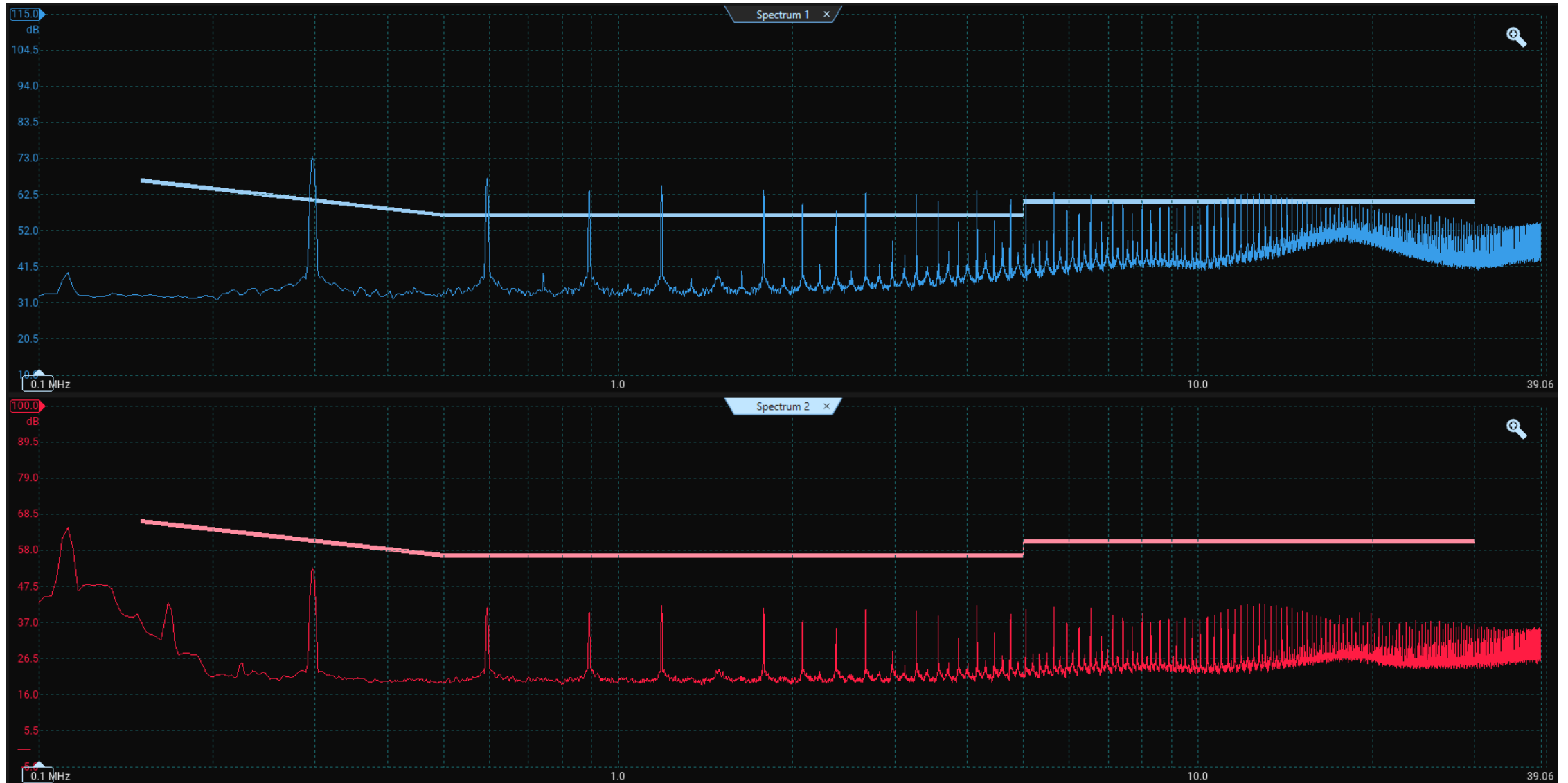

WHERE DID MY IMPEDANCE GO?

CALCULATING X CAPACITOR VALUE

Calculating Differential (Leakage) Inductance



$$L_{DM} = \frac{Z_{DM}}{2\pi \cdot f_{DM}} = \frac{20}{2\pi * 300KHZ} = 10\mu H$$

$$C_x = \frac{1}{(2\pi \cdot f_{DM})^2 \cdot L_{DM}}$$

$$= \frac{1}{(2\pi \cdot 25kHz)^2 \cdot 10\mu H}$$

$$C_x = 4.7\mu F$$

$$C_{x_Effective} = 3.4\mu F$$

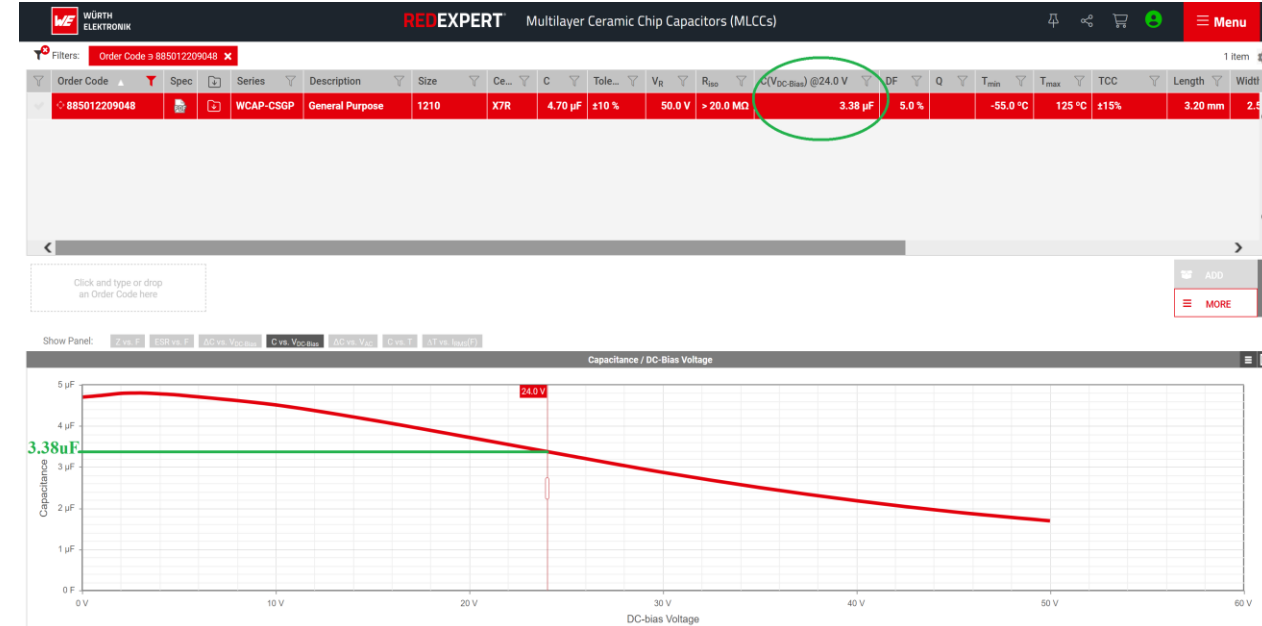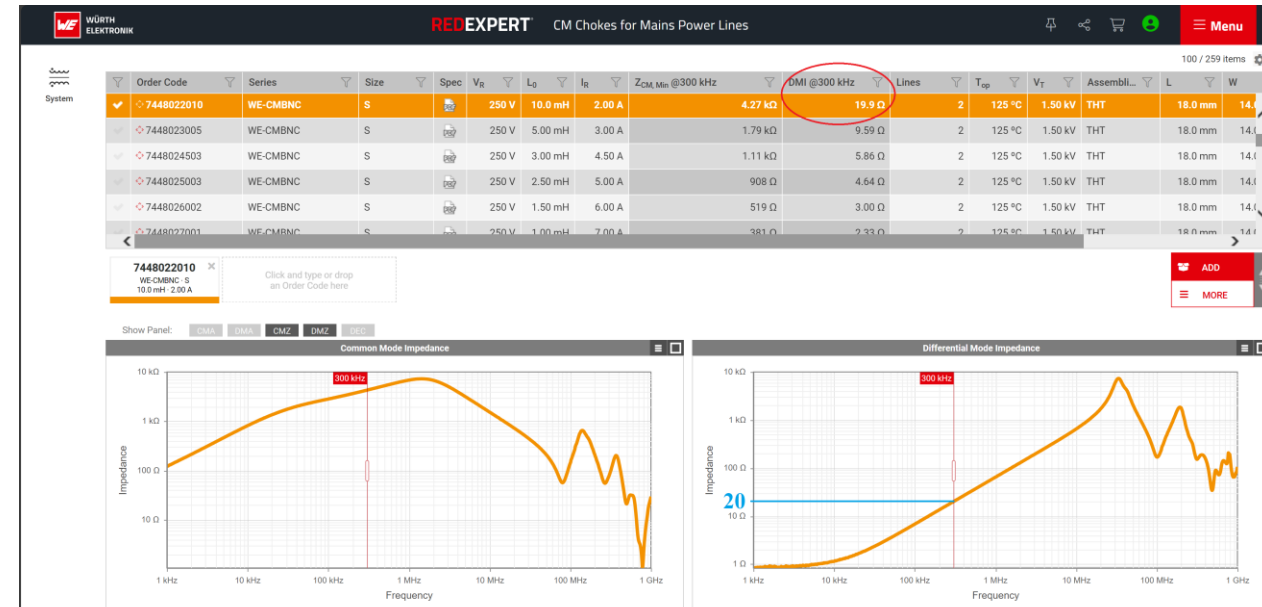

CALCULATING X CAPACITOR VALUE

So which One is it?



- $f_{Cut-off_DM} = \frac{1}{2\pi\sqrt{L_{DM} \cdot C_x}}$
- $f_{Cut-off_DM_Estimate} = \frac{1}{2\pi\sqrt{10\mu H \cdot 162nF}} = 130\text{KHz}$
- $f_{Cut-off_DM_Calculated} = \frac{1}{2\pi\sqrt{10\mu H \cdot 3.4\mu F}} = 26.2\text{KHz}$
- $Att_{DM_Estimate} = \log\left(\frac{f_{SW}=300\text{KHz}}{f_{DM_Estimate}=130\text{KHz}}\right) \cdot 40\text{dB} = 14\text{dB}$
- $Att_{DM_Calculated} = \log\left(\frac{f_{SW}=300\text{KHz}}{f_{DM_Estimate}=26\text{KHz}}\right) \cdot 40\text{dB} = 42\text{dB}$

Y CAPACITOR SELECTION



Y CAPACITORS

- Y capacitors filter common mode noise
- Need to meet special safety criteria since they are connected to earth.
- Y1
 - Double or Reinforced Insulation
 - 0-500V rated voltage
 - 8 kV peak impulse voltage
- Y2
 - Basic or supplementary insulation
 - 150-500V rated voltage
 - 5 kV peak impulse voltage
- Y4
 - Basic or supplementary insulation
 - 0-150V
 - 2.5 kV peak impulse voltage
- Y class capacitors can only be substituted by Y class capacitors of the same or higher voltage rating!

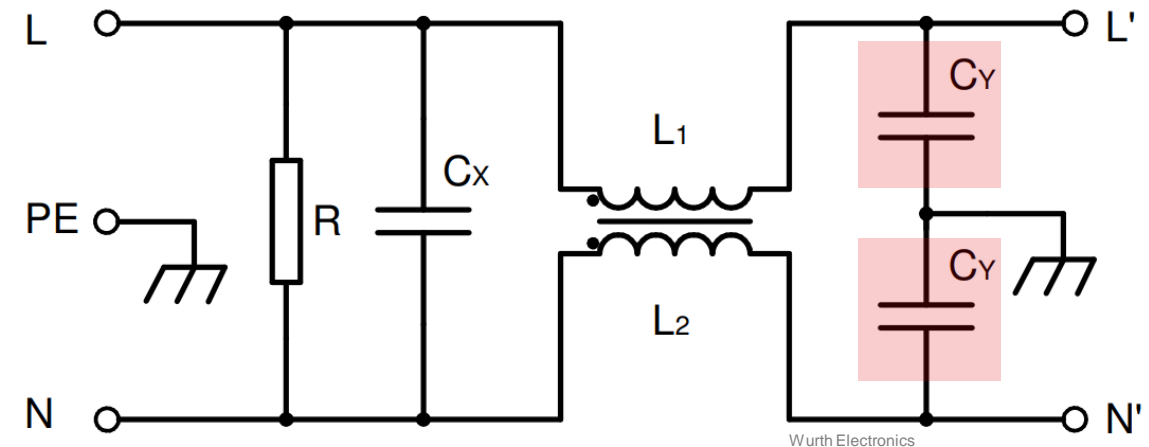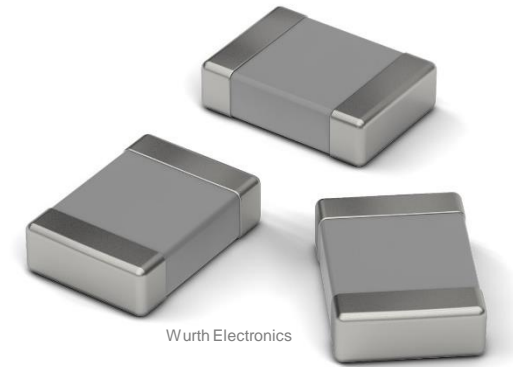

CALCULATING Y CAPACITOR VALUE

$$\blacksquare f_{CM} = \frac{1}{2\pi\sqrt{L_{CM}\cdot C_y}}$$


$$\blacksquare C_y = \frac{1}{(2\pi\cdot f_{CM})^2\cdot L_{CM}} = \frac{1}{(2\pi\cdot 25kHz)^2\cdot 10mH}$$

$$\blacksquare C_y = 4100pF$$

Pay attention to leakage current limits for your standard!


Y capacitor DEMO

BLUE IS CM AND RED IS DM

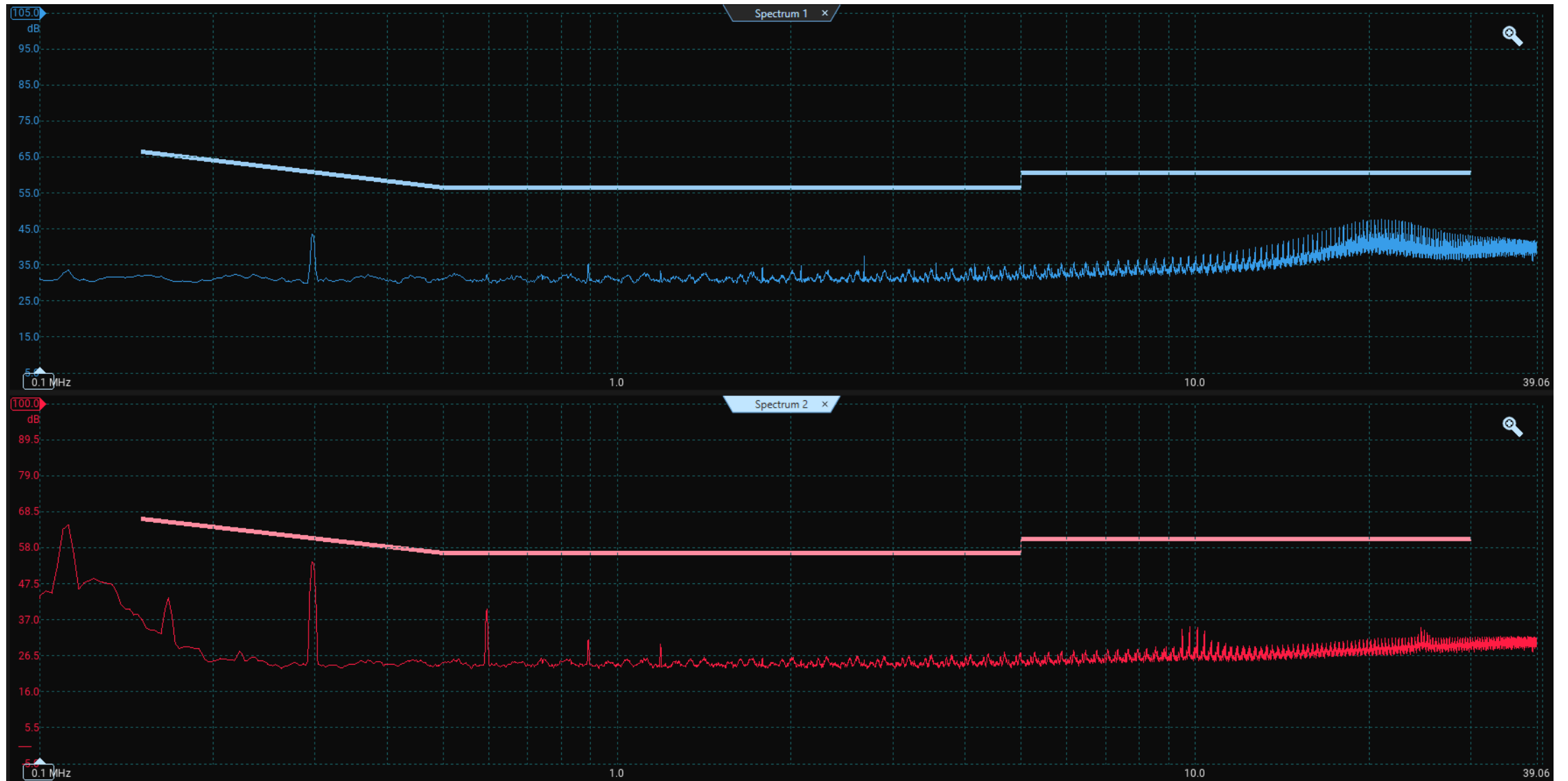

FILTER IN LT SPICE

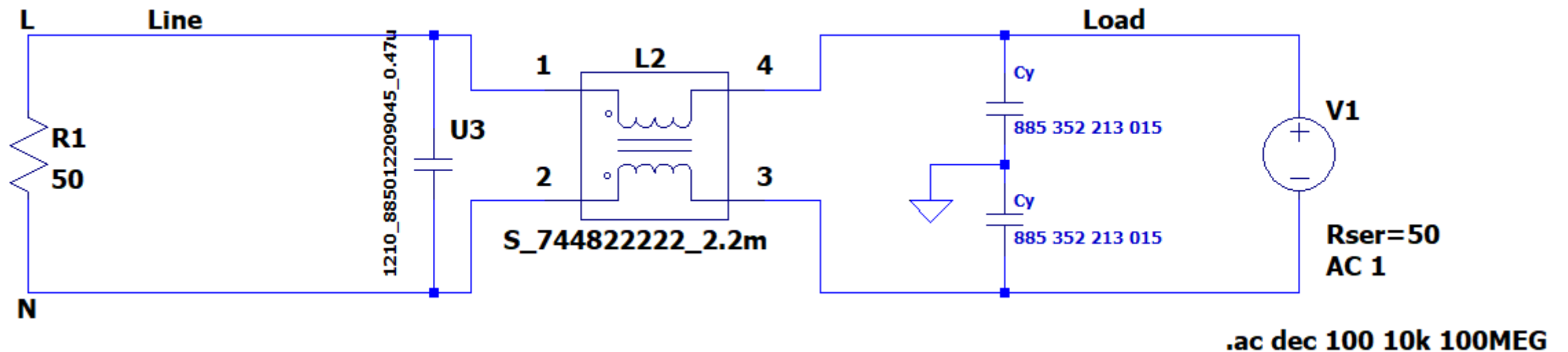- Models found in the "Contrib" folder in LTspice.
- Latest updates automatically downloaded when LTspice is updated.
- Use equivalent circuits of real components.
- Do not use to simulate saturation! (Since models do not include accurate nonlinear BH loop)




NEED DESIGN HELP?

- 7 different textbooks (magnetics, Ltspice, etc.) Nearly 1000 pages of practical information.
- Over 110 application notes
- Local assistance (email, phone, video call, online chat, etc.)
- [Design for Electromagnetic Compatibility--In a Nutshell: Theory and Practice | SpringerLink](#)



Würth Elektronik

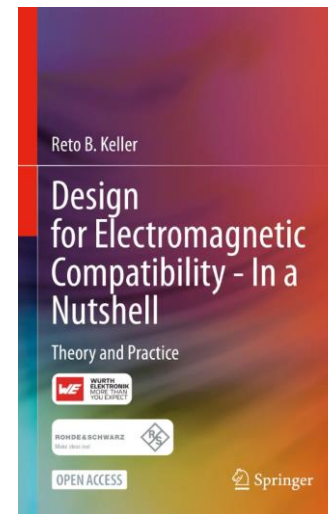

Keller, Reto, Design for Electromagnetic Compatibility – In a Nutshell, Springer Cham, Nov. 22, 2022



Würth Elektronik

