

# THE SYMPHONY OF OSCILLATORS: HARMONIZING SIGNALS FOR SUCCESS

Susanna Engel Rodrigues Field Application Engineer - Frequency Products

WURTH ELEKTRONIK MORE THAN YOU EXPECT

#### **AGENDA**

- Introduction
- Types of Noises
  - Oscillator
  - Power Line
  - Output Line
- PCB Layout Recommendations



![](_page_1_Picture_9.jpeg)

#### Introduction

- What is EMI and EMC?
  - Electromagnetic interference and electromagnetic compatibility
- In respect of oscillators?
  - Oscillators can both be effected by EMI but also generate EMI
- In general
  - Appropriate measures must be taken

![](_page_2_Picture_9.jpeg)

Type of Noises

![](_page_3_Figure_2.jpeg)

![](_page_3_Picture_4.jpeg)

Noise From Oscillator

![](_page_4_Figure_2.jpeg)

![](_page_4_Picture_4.jpeg)

## **NOISE FROM OSCILLATOR**

Choice of Specification Parameters

- Type of Oscillator
- Size
- Output Signal
- Rise & Fall Time
- Frequency
- Supply Voltage

- OCXO: good; VCXO & TCXO: not so good; XO: good compromise
- $\rightarrow$  smaller is better
- CMOS: worse; Sinewave: good but sensitive;
   Differential: good if designed properly
- → take it slow
- $\rightarrow$  lower is better
- → smaller is better

![](_page_5_Picture_15.jpeg)

## **NOISE FROM OSCILLATOR**

Spread Spectrum Oscillators

• Spectrum measurement of an CFSS-2 @ 50 MHz

![](_page_6_Figure_3.jpeg)

![](_page_6_Figure_4.jpeg)

![](_page_6_Picture_6.jpeg)

![](_page_7_Figure_1.jpeg)

![](_page_7_Picture_3.jpeg)

Decoupling Capacitor

Minimum recommendation

![](_page_8_Figure_3.jpeg)

![](_page_8_Picture_5.jpeg)

#### Decoupling Capacitor

![](_page_9_Figure_2.jpeg)

![](_page_9_Picture_4.jpeg)

#### Decoupling Capacitor

![](_page_10_Figure_2.jpeg)

![](_page_10_Picture_4.jpeg)

Filtering

- Low pass filter
- Theoretically 20 dB/decade attenuation per filter component
- Ideally filter up to ~10<sup>th</sup> harmonic
- Various filter topologies
  - CL Filter
  - Π Filter

![](_page_11_Picture_9.jpeg)

CL - Filter

- Recommended to add at least as mounting option
  Adds theoretically 40 dB/decade  $f_r = \frac{1}{2\pi\sqrt{L*C}}$ V<sub>5</sub>
  U<sub>5</sub>
  C<sub>2</sub>
  C<sub>1</sub>
  Out Oscillator
  I GND
  I GND<
- $f_r$  = resonance frequency of the filter should be 1/10 of oscillator frequency

![](_page_12_Picture_5.jpeg)

 $\Pi$  - Filter

Theoretically adds 60 dB/decade

![](_page_13_Figure_3.jpeg)

![](_page_13_Picture_5.jpeg)

Noise From Output Line

![](_page_14_Figure_2.jpeg)

![](_page_14_Picture_4.jpeg)

#### Serial Resistance

- In line between oscillator & μC
- Recommended to be added as mounting option / equipped with 0 Ω
- Eliminate undesired waveform distortions  $V_{\rm S}$
- Test for ideal value

![](_page_15_Figure_6.jpeg)

![](_page_15_Picture_8.jpeg)

RC - Filter

- Recommended to be added as mounting option
- ~20 dB attenuation
- Cutoff frequency higher than oscillator frequency

$$f_C = \frac{1}{(2\pi R_S C_F)}$$

• Optional: Use LC Filter

![](_page_16_Figure_7.jpeg)

![](_page_16_Picture_9.jpeg)

Termination / Impedance Matching

- Between oscillator & GND
- Mainly important when having long traces
- May add as a mounting option

![](_page_17_Figure_5.jpeg)

![](_page_17_Picture_7.jpeg)

Termination + RC - Filter

 Attention: R<sub>s</sub> & R<sub>T</sub> build a voltage divider → R<sub>s</sub> << R<sub>T</sub> !!

![](_page_18_Figure_3.jpeg)

![](_page_18_Picture_5.jpeg)

Shielding

- Effect of oscillator housing
  - Plastic enclosures do not have any effect on shielding
  - Metal lids without connection to ground will only have a minor effect
  - Metal lids with connection to ground still only have a small effect
- May enclose the oscillator circuit (+µC) in
  - Metallic enclosures
  - Shielding cans

![](_page_19_Picture_10.jpeg)

#### PCB LAYOUT

**General Notes** 

- Keep the traces as short as possible!
- Avoid 90° bends round right angles!
- Do not cross any other signal lines!
- Do not run any signals and lines under oscillator or close by!
- No loops!
- Keep differential output traces the same or close to the same length and close to each other!

![](_page_20_Figure_8.jpeg)

![](_page_20_Picture_10.jpeg)

## PCB LAYOUT

#### Oscillator Specific Notes

![](_page_21_Figure_2.jpeg)

![](_page_21_Picture_4.jpeg)

![](_page_22_Picture_0.jpeg)

![](_page_22_Picture_2.jpeg)