




# EMI FILTER DESIGNER **RE**DEXPERT

Oscar Gonzalez – Technical Chat Engineer

**WÜRTH ELEKTRONIK** MORE THAN YOU EXPECT
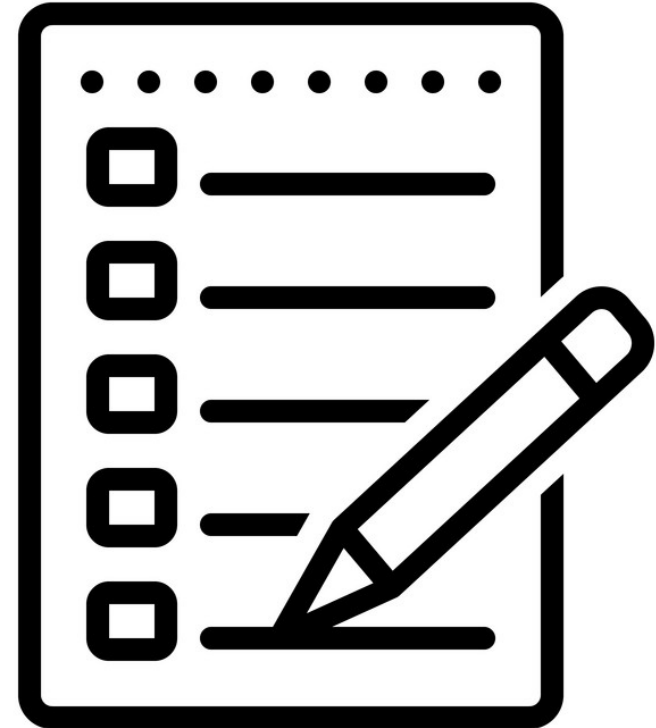
# AGENDA

- Differential EMI Filter.
- Low Pass Filter topologies.
- Main parameters.
- Solution using **REDEXPERT**.
- Application examples.




# INTRODUCTION TO DIFFERENTIAL EMI FILTER

# DIFFERENTIAL EMI FILTER
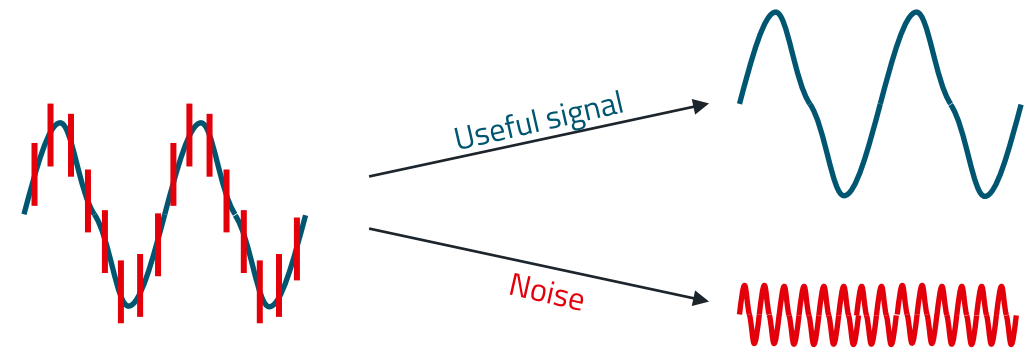
## What is it?


- It's a filter designed to attenuate **differential** mode noise – **REDEXPERT** focuses on Power Supply Lines.
  - Transformer outputs.
  - Vcc lines.
  - DC-DC converters.
- **Noise** has a higher frequency than the useful signal.
- A **low pass** filter is needed:
  - To **pass** the low-frequency (or CC) useful signal.
  - To **attenuate** the high-frequency noise.



# DIFFERENTIAL EMI FILTER
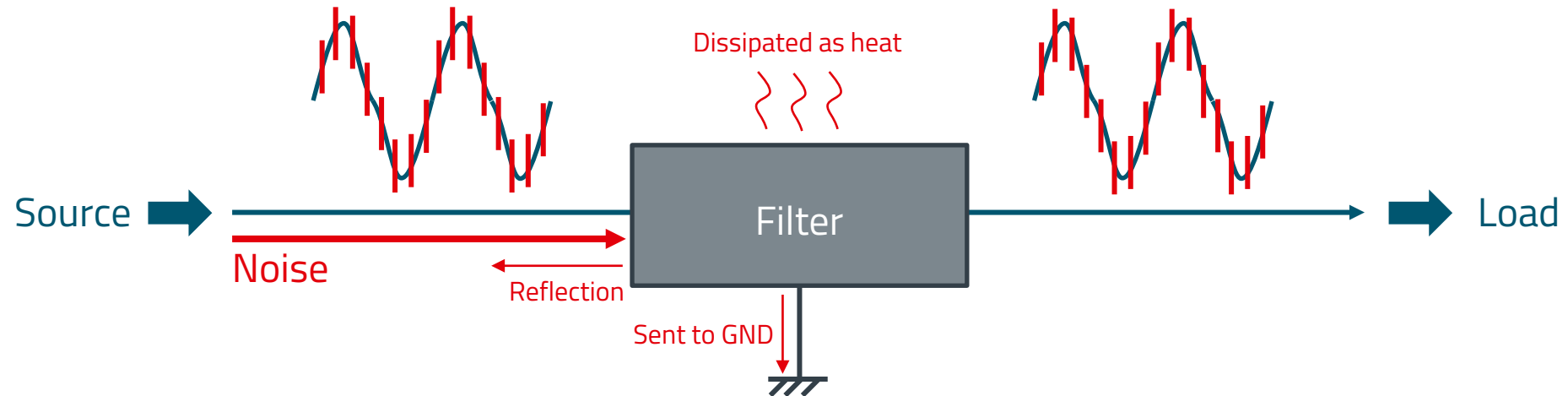
## How does it work?







- The **useful signal** goes through the filter mostly unaffected.
- The **noise** is attenuated by the filter.



# LOW PASS FILTER TOPOLOGIES

# LOW PASS FILTER TOPOLOGIES

Topologies in **REDEXP**ERT

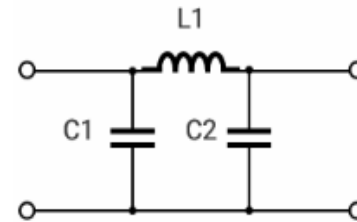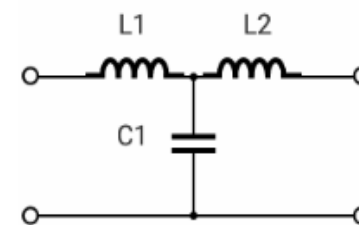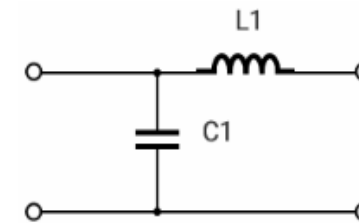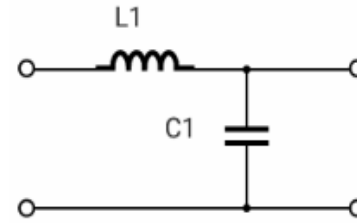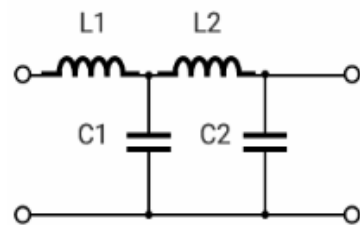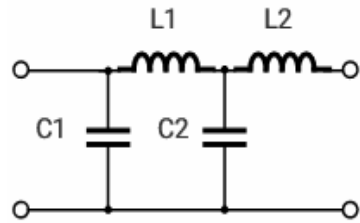

Passive  
filter  
topologies

# LOW PASS FILTER TOPOLOGIES

## Selection criteria

- Arrangement of capacitors and ferrites:
  - $Z_{\text{source}} > Z_{\text{load}} \rightarrow$  Ferrite first.
  - $Z_{\text{source}} = Z_{\text{load}} \rightarrow$  Ferrite or Capacitor first.
  - $Z_{\text{source}} < Z_{\text{load}} \rightarrow$  Capacitor first.
- Order of the filter – Number of passive components:
  - The more the dB per decade, the more passive components – 20 dB per decade per component.

Project's Title:  
Title  
My EMI Filter project

Input parameters:  
Operating voltage 12 V  
Operating current 1 A  
Load / LISN impedance 100  $\Omega$   
Noise source impedance 10  $\Omega$

Cut-off frequency  150 kHz  
Attenuation  60 dB at Frequency 1500 kHz

Topology:

- LC
- CL
- Pi (RECOMMENDED)
- T-Filter
- 4th-Order LC-LC
- 4th-Order CL-CL


60 dB from 150 kHz to 1.5 MHz  
(1 decade)  
 $\rightarrow$  3 passive components.



# MAIN PARAMETERS


# MAIN PARAMETERS

## System Parameters

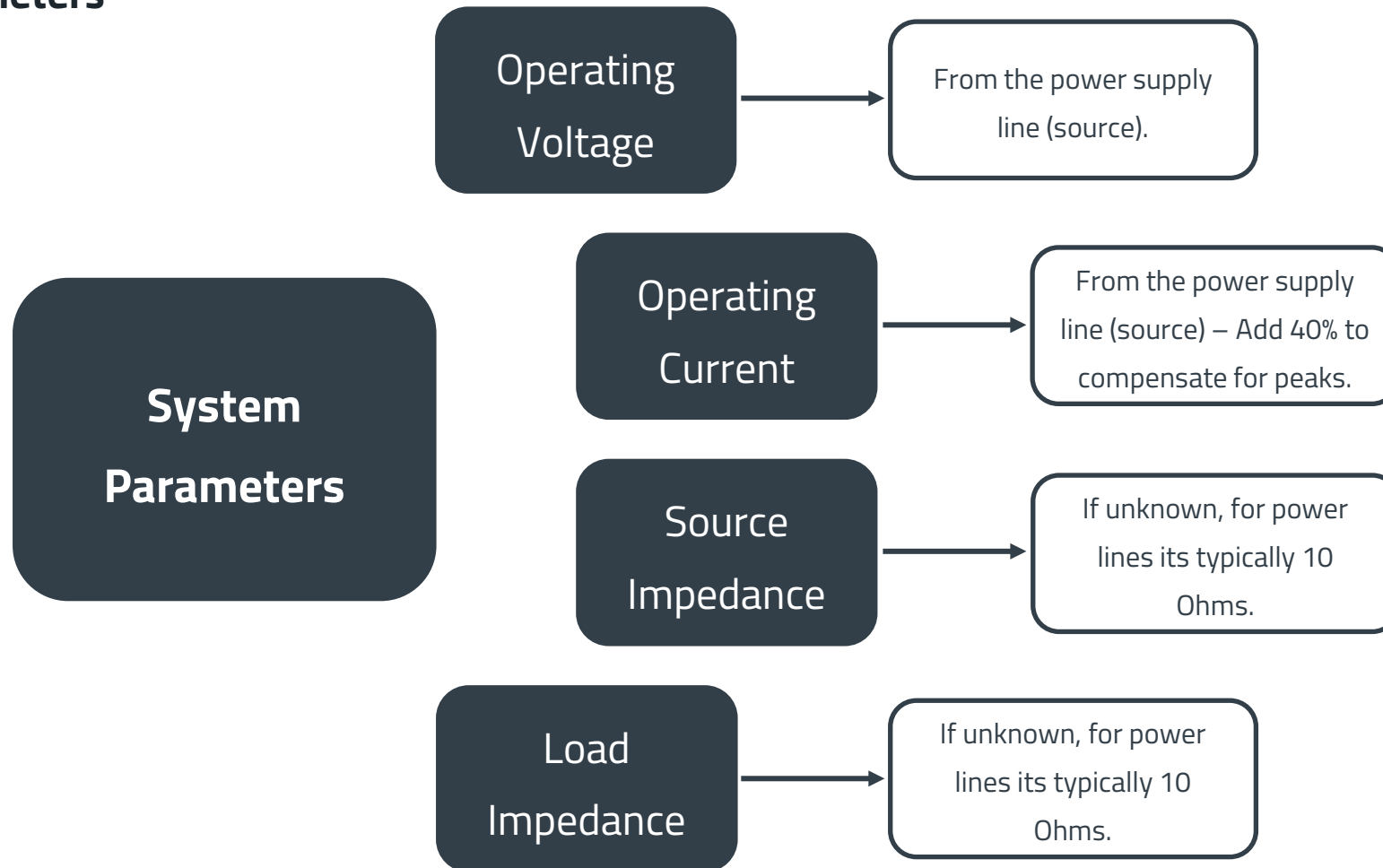

# MAIN PARAMETERS

## Attenuation Requirements

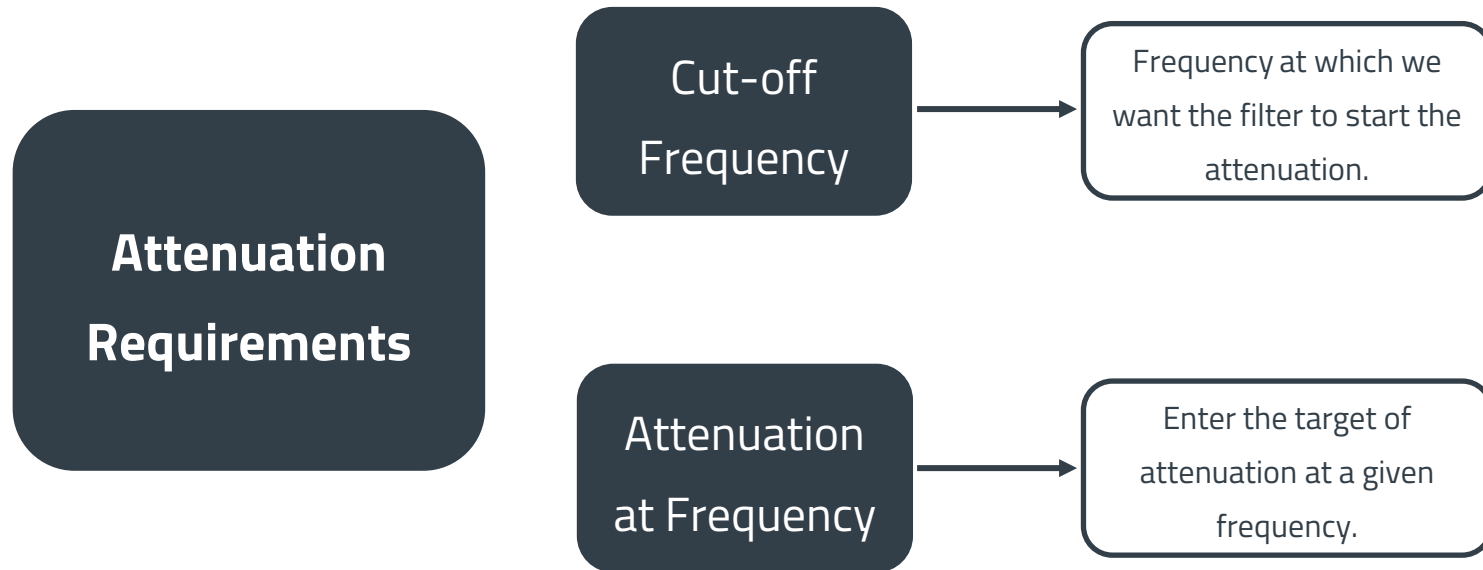

### Considerations

- Cut-Off Frequency must be lower than the Attenuation at Frequency.
- At least one value must be filled out.
- Conducted emissions: 150 kHz – 30 MHz.

# SOLUTION USING **RE**DEXPERT

# SOLUTION USING REDEPERT

## Parameters

- USB 3.1 60W – Low pass filter for the Vcc line.



- Operating voltage: 20V.
- Operating current: 3 A – 5 A to prevent peaks.
- Source impedance: 10 Ohms.
- Load impedance: 10 Ohms.
  
- Cut-Off frequency: 100 kHz.
- Special interest at 5MHz, attenuation of 100 dB.

# SOLUTION USING REDEPERT

## Parameters

Project's Title:

Title  
Power Line USB 3.1 60W

Input parameters:

Operating voltage  
20 V

Operating current  
5 A

Load / LISN impedance  
10  $\Omega$







Noise source impedance  
10  $\Omega$

Cut-off frequency  
 100 kHz

Attenuation  
 100 dB

at Frequency  
5000 kHz

Topology:

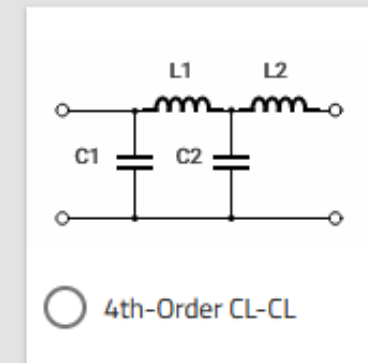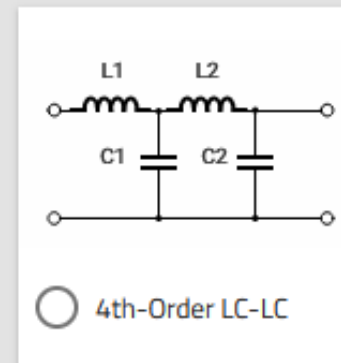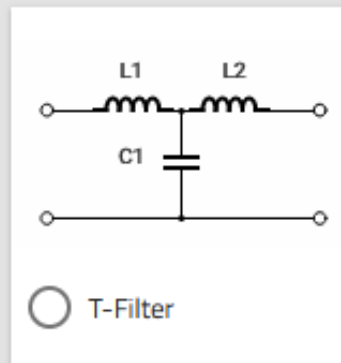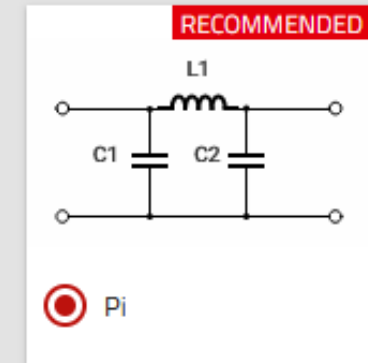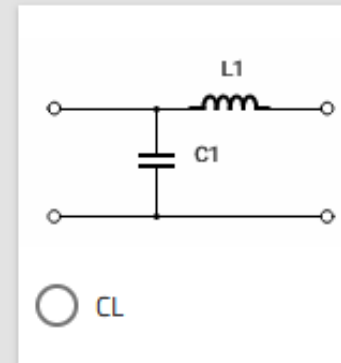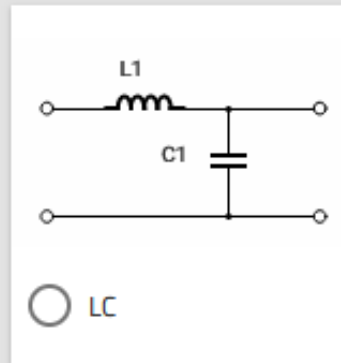

# SOLUTION USING REDEPERT

## Selection and simulation - Capacitors

Power Line USB 3.1 60W

C1		1.00 μF	25.0 V	8.58 mΩ	
L1		33.0 μH	5.20 A	35.0 mΩ	
C2		1.00 μF	25.0 V	8.58 mΩ	

Details


Calculated C1 Capacitance	Calculated C2 Capacitance
159 nF	159 nF
Calculated L1 Inductance	Insertion Loss
31.8 μH	-108 dB@5.00 MHz

	C	C@20.0 V
<input checked="" type="checkbox"/>	1.00 μF	163 nF

The voltage across a capacitor decreases its capacitance – **REDEPERT** considers the capacitance drop to pick the right part.

# SOLUTION USING REDEPERT
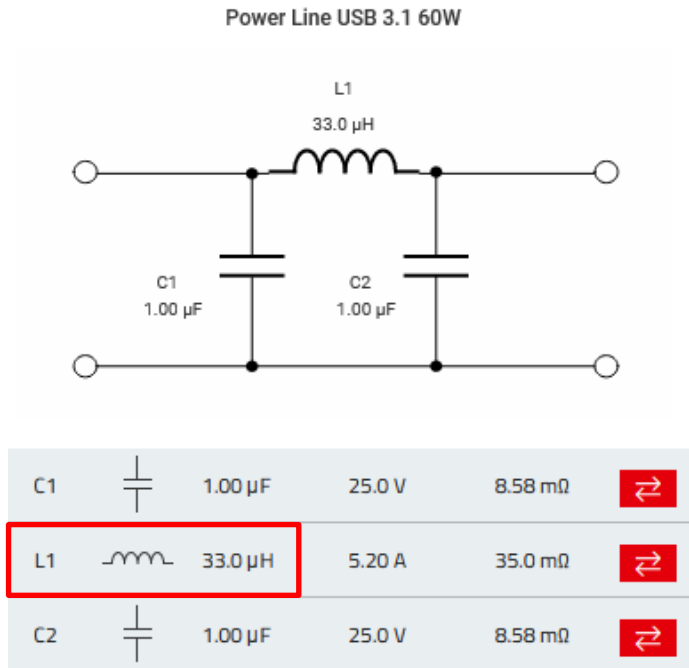
## Selection and simulation – Ferrite / Inductor



Details

Calculated C1 Capacitance	159 nF	Calculated C2 Capacitance	159 nF
Calculated L1 Inductance	31.8 μH	Insertion Loss	-108 dB@5.00 MHz


	L	L@5.00 A	I <sub>R</sub>
<input checked="" type="checkbox"/>	33.0 μH	31.7 μH	5.20 A

The current driven in a ferrite decreases its inductance – **REDEPERT** considers the inductance drop to pick the right part.



# SOLUTION USING REDEXPERT

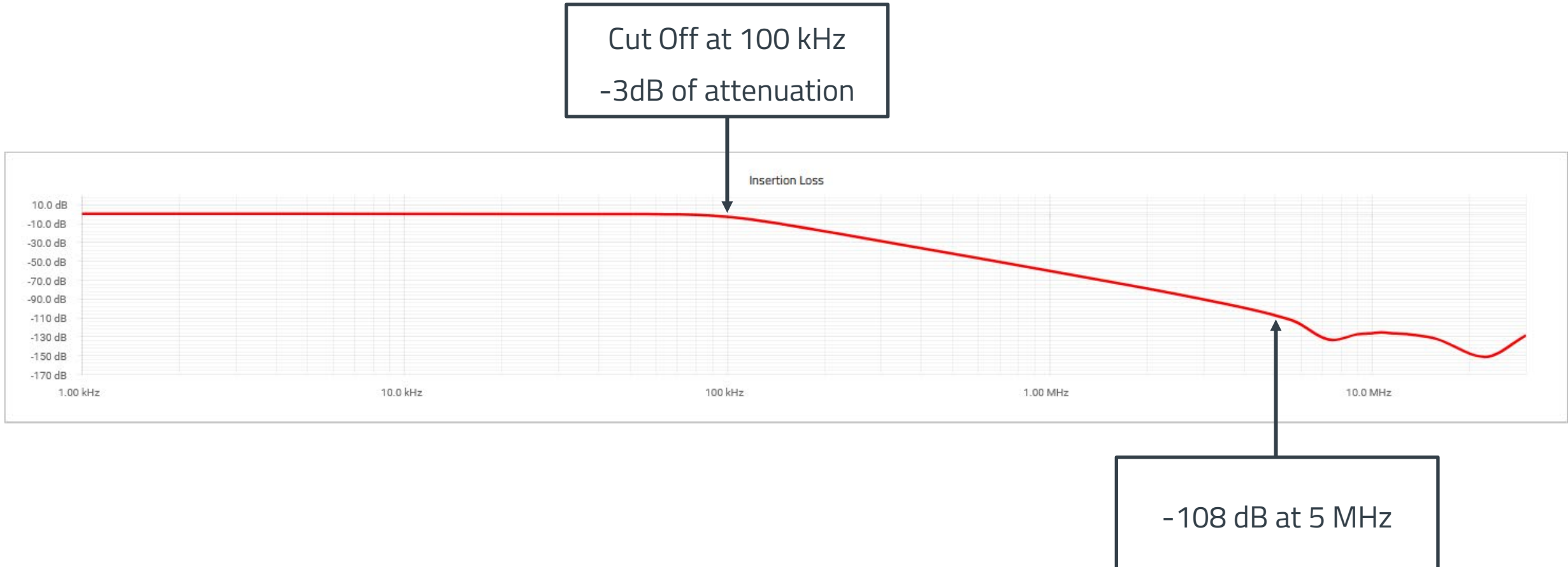
## Selection and Simulation - Insertion Loss



# SOLUTION USING REDEXPERT

## Summary

### Circuit Schematic

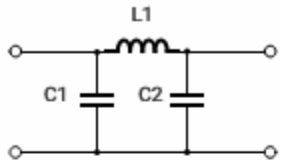

### Specifications

Edit

"Power Line USB 3.1 60W"

TYPE: Pi

V<sub>op</sub>: 20.0 V

I<sub>op</sub>: 5.00 A

LOAD / LISN IMPEDANCE: 10.0 Ω


NOISE SOURCE IMPEDANCE: 10.0 Ω

ILOSS -108 dB@5.00 MHz

### Bill Of Materials

ADD

#	N...	Order Code	Value	Properties	Qty
1.	C1...	885012106022	1.00 μF	Assembling Technology = SMT Capacitance = 1.00 μF Rated Voltage = 25.0 V Height = 800 μm	2
2.	L1	7447704330	33.0 μH	Inductance = 33.0 μH Rated Current = 5.20 A	1

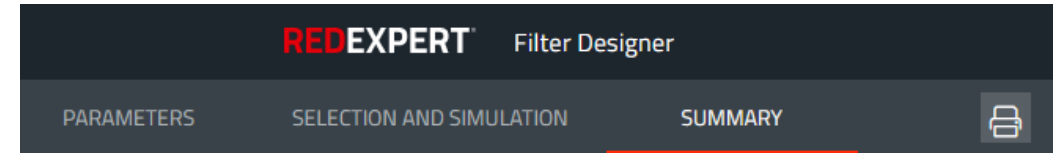


Print the summary

# APPLICATION EXAMPLES

# APPLICATION EXAMPLES
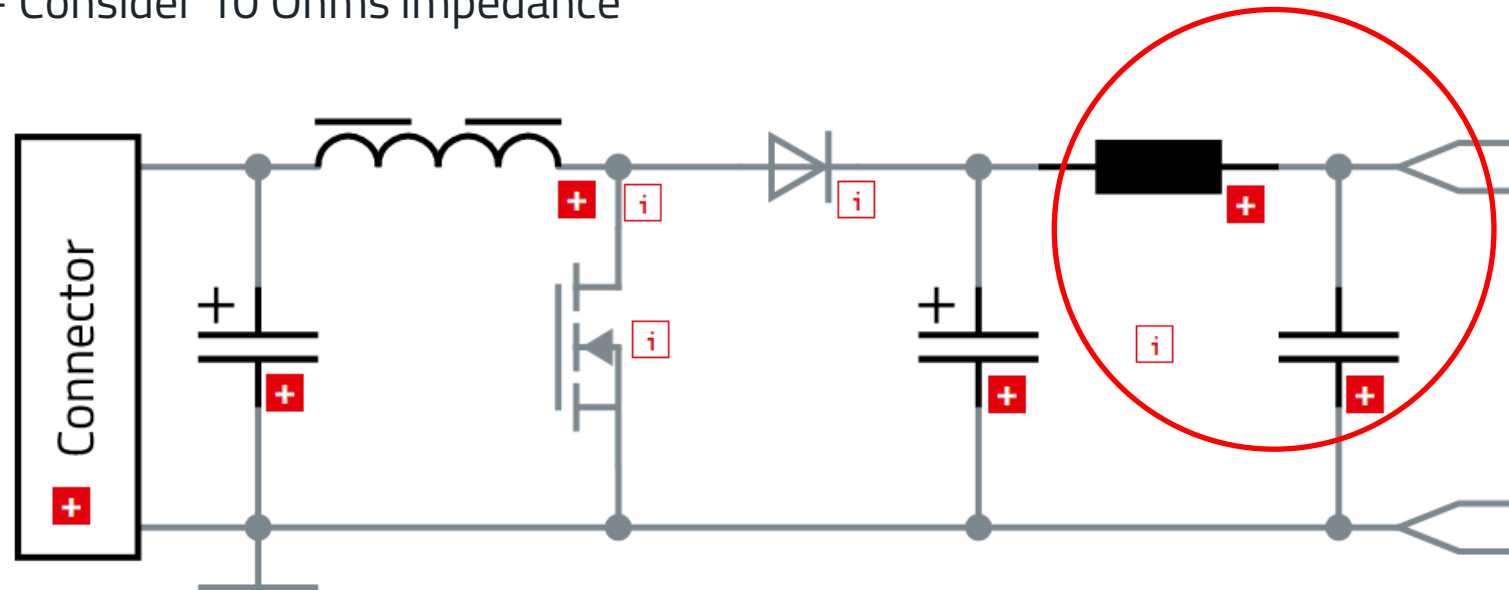
## Example 1


- Offer a filter for an output of a Boost Converter:
  - The output power is 24W (48 V @ 0.5 A) – Add more current for peaks, 0.7 A.
  - Cut-Off frequency required at 25 kHz
  - Power line – Consider 10 Ohms impedance



# APPLICATION EXAMPLES

## Example 1 - Summary

### Circuit Schematic

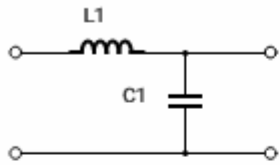

### Specifications

[Edit](#)

"Boost Converter 24W"

TYPE: LC

$V_{op}$ : 48.0 V

$I_{op}$ : 800 mA

LOAD / LISN IMPEDANCE: 10.0  $\Omega$

NOISE SOURCE IMPEDANCE: 10.0  $\Omega$

ILOSS -5.92 dB@25.0 kHz

### Bill Of Materials

[ADD](#)


#	N...	Order Code	Value	Properties	Qty
1.	C1	885012210032	2.20 $\mu$ F	Assembling Technology = SMT Capacitance = 2.20 $\mu$ F Rated Voltage = 50.0 V Height = 2.50 mm	1
2.	L1	7447462101	100 $\mu$ H	Inductance = 100 $\mu$ H Rated Current = 800 mA	1



# APPLICATION EXAMPLES
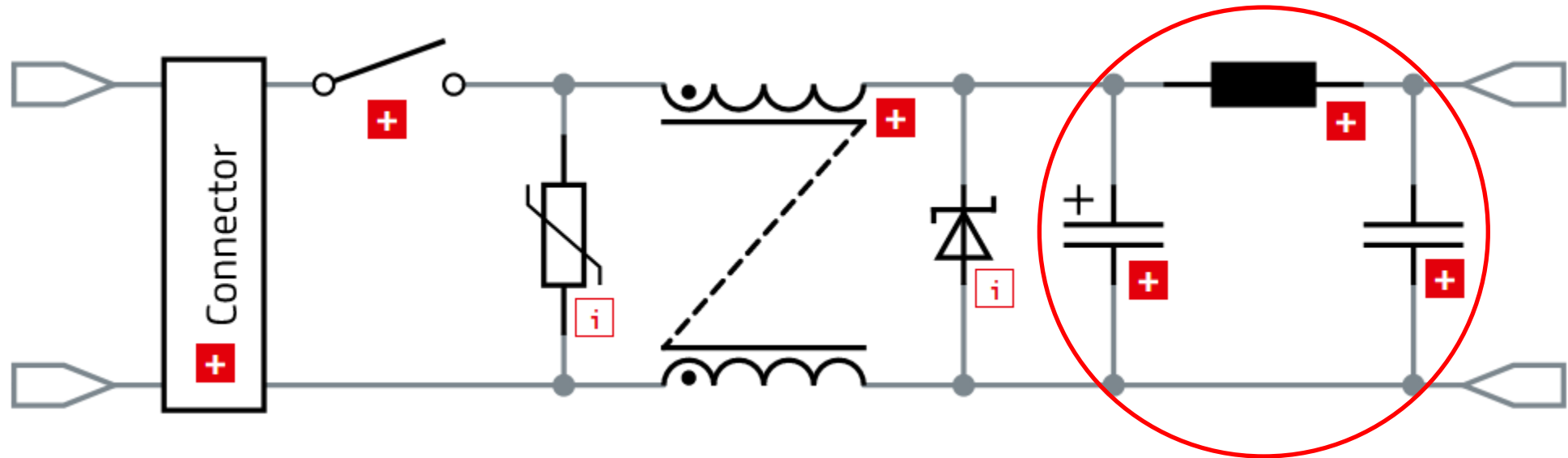
## Example 2


- Offer a filter for an output of a battery:
  - The battery provides 18 A up to 50 VDC (nominal 36 VDC) – Let's set the current to 25 A for peaks.
  - Cut off frequency at 150 kHz – 120 dB needed at 30 MHz



# APPLICATION EXAMPLES

## Example 2 - Summary

### Circuit Schematic

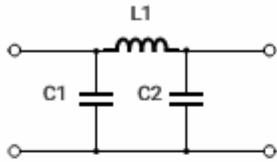

### Specifications

[Edit](#)

"Battery"

TYPE: Pi

$V_{op}$ : 50.0 V

$I_{op}$ : 25.0 A

LOAD / LISN IMPEDANCE: 10.0  $\Omega$


NOISE SOURCE IMPEDANCE: 10.0  $\Omega$

ILOSS -126 dB@30.0 MHz

### Bill Of Materials

[ADD](#)


#	N...	Order Code	Value	Properties	Qty
1.	C1...	885012207100	220 nF	Assembling Technology = SMT Capacitance = 220 nF Rated Voltage = 50.0 V Height = 1.25 mm	2
2.	L1	7443763540220	22.0 $\mu$ H	Inductance = 22.0 $\mu$ H Rated Current = 40.6 A	1

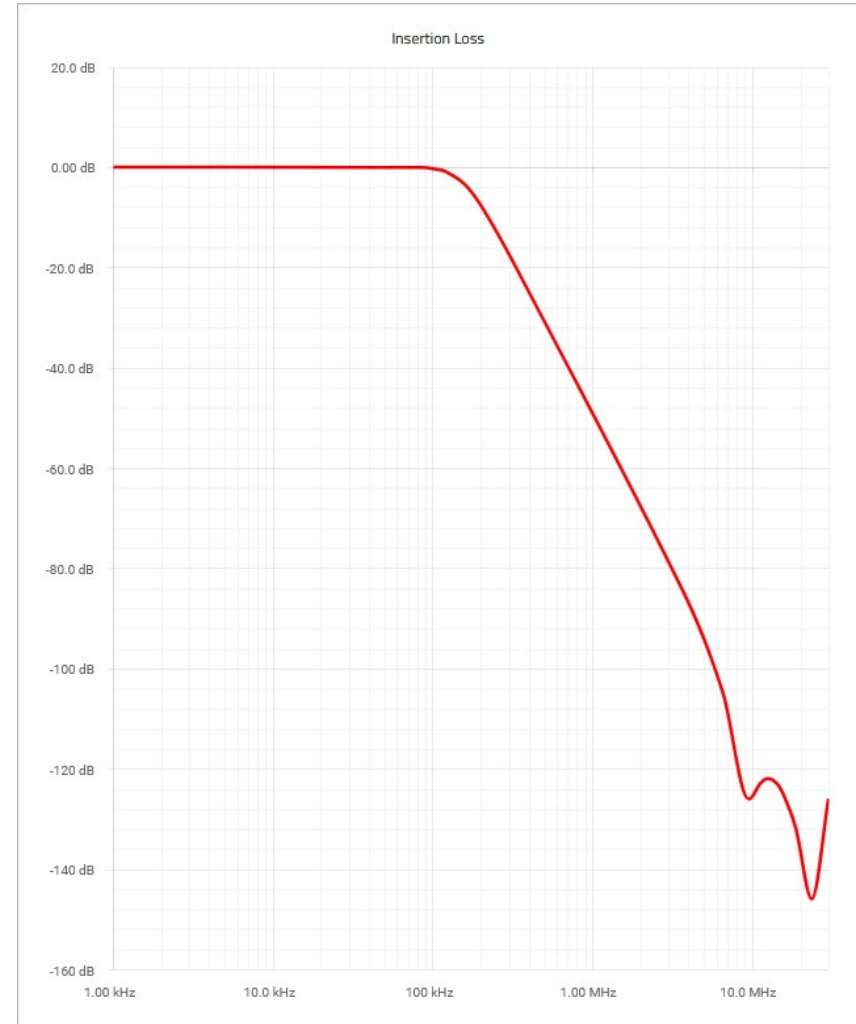

# APPLICATION EXAMPLES
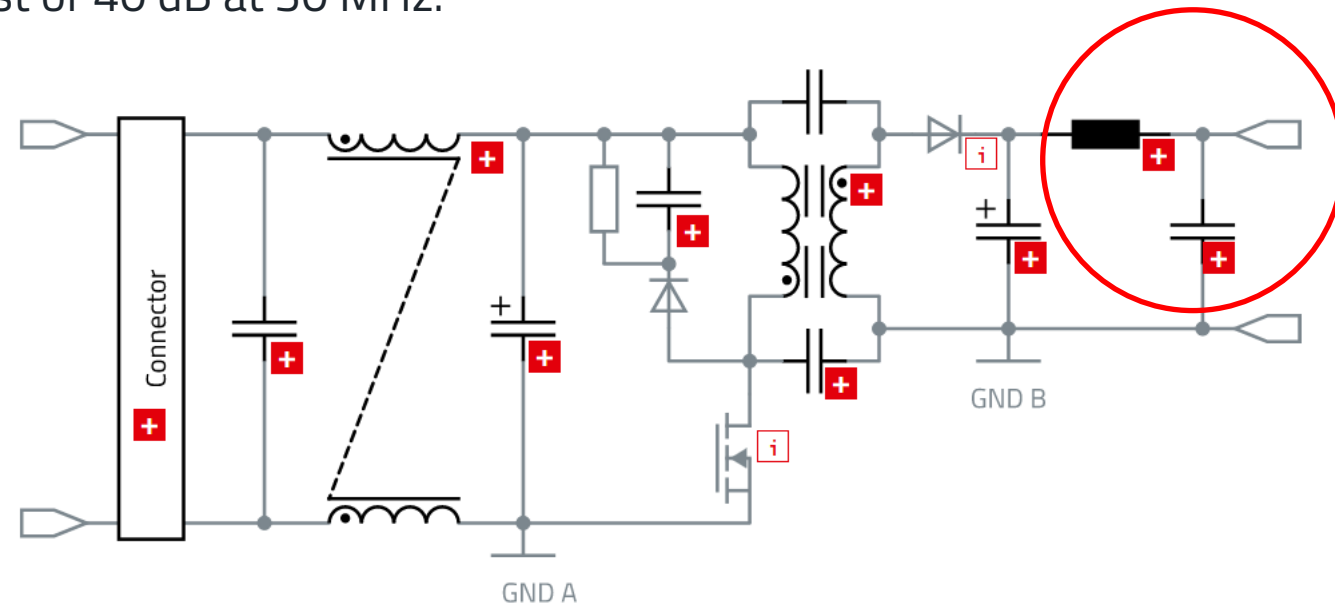
## Example 3

- Offer a filter for the output of the transformer 750370041:
  - Output of 5 V at 1 A (let's do 1.5 A to compensate for peaks).
  - Switching at 1 MHz – Cut off at the frequency of operation, interest of 40 dB at 30 MHz.






# APPLICATION EXAMPLES

## Example 3 - Summary

### Circuit Schematic

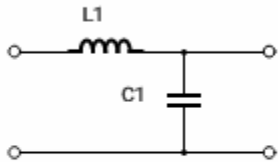

### Specifications

[Edit](#)

"Transformer"

TYPE: LC

V<sub>op</sub>: 5.00 V

I<sub>op</sub>: 1.50 A

LOAD / LISN IMPEDANCE: 10.0 Ω

NOISE SOURCE IMPEDANCE: 10.0 Ω

ILOSS -65.8 dB@30.0 MHz

### Bill Of Materials

[ADD](#)

#	N...	Order Code	Value	Properties	Qty
1.	C1	885012205015	33.0 nF	Assembling Technology = SMT Capacitance = 33.0 nF Rated Voltage = 10.0 V Height = 500 μm	1
2.	L1	74438343022	2.20 μH	Inductance = 2.20 μH Rated Current = 1.65 A	1



# QUESTIONS?



## CHAT WITH US!



[www.we-online.com/en/components/products](http://www.we-online.com/en/components/products)

- Live Technical Chat
- Real People
- Sales Support
- Engineering Assistance
- Quick Problem Solving
- 24 hours Monday - Friday

# THANK YOU



# PRESENTATION FEEDBACK

