

GaN FET Layout

Wurth Power Day

Boston, Oct. 22, 2024

brian.miller@epc-co.com




Agenda

- Why use GaN FETs?
- Layout Optimization Benefits
- Layout
 - Shortcuts to get a good layout
- Examples
- Resources

GaN FET Overview

GaN FETs: like MOSFETs but...

 
- Smaller
- Switch faster
- Reverse voltage conduction
 - Main channel, not a parasitic element
- Zero reverse recovery (Q_{RR})
- Miller ratio < 1 (Q_{GD}/Q_{GS_Th})
(dv/dt immunity)
- Exceptional reliability



GaN FET Overview

Benefits:

 - Smaller, due to:
 - Smaller devices
 - Higher frequency
 - Smaller heat sinks
- More efficient
- Exceptional reliability



EPC 200 V vs. Si Devices

Si MOSFET
Benchmark




9.9 x 11.7 mm

eGaN FET



4.6 x 1.6 mm

eGaN FET

 



3 x 5 mm

Parameter	IPT111N20NFD (@ 10 V _{GS})	EPC2215 (@ 5 V _{GS})	EPC2304 (@ 5 V _{GS})
R _{DS(on)} typ	9 mΩ	6 mΩ	3.4 mΩ
R _{DS(on)} max	11.1 mΩ	8 mΩ	5 mΩ
Q _G typ	65 nC	10 nC	20 nC
Q _{GD} typ	8 nC	1.6 nC	3.2 nC
Q _{oss} typ	162 nC	68 nC	68 nC
Q _{RR} typ	309 nC	0 nC	0 nC
Device Size	115.83 mm ²	7.36 mm ²	15 mm ²

15x smaller, less losses, no reverse recovery, higher f_{sw}

GaN FETs: Zero Reverse Recovery

 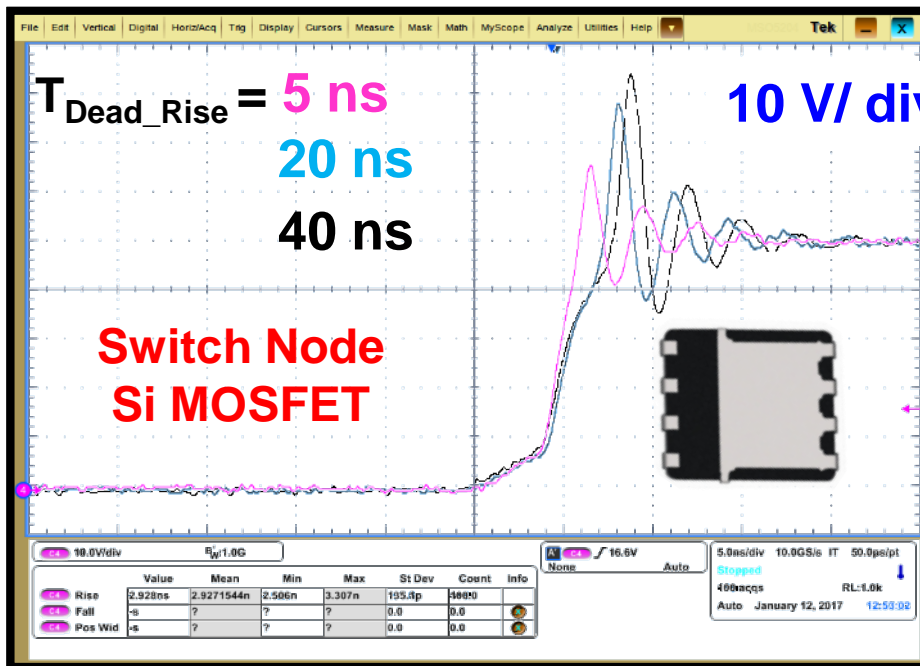- Higher hard-switching frequencies without penalty
- Lower switching distortion




$$V_{\text{IN}} = 48 \text{ V}, V_{\text{OUT}} = 12 \text{ V}, I_{\text{OUT}} = 20 \text{ A}, f_{\text{sw}} = 500 \text{ kHz}, L_{\text{Buck}} = 4.7 \mu\text{H}$$

Layout

Layout - Efficiency

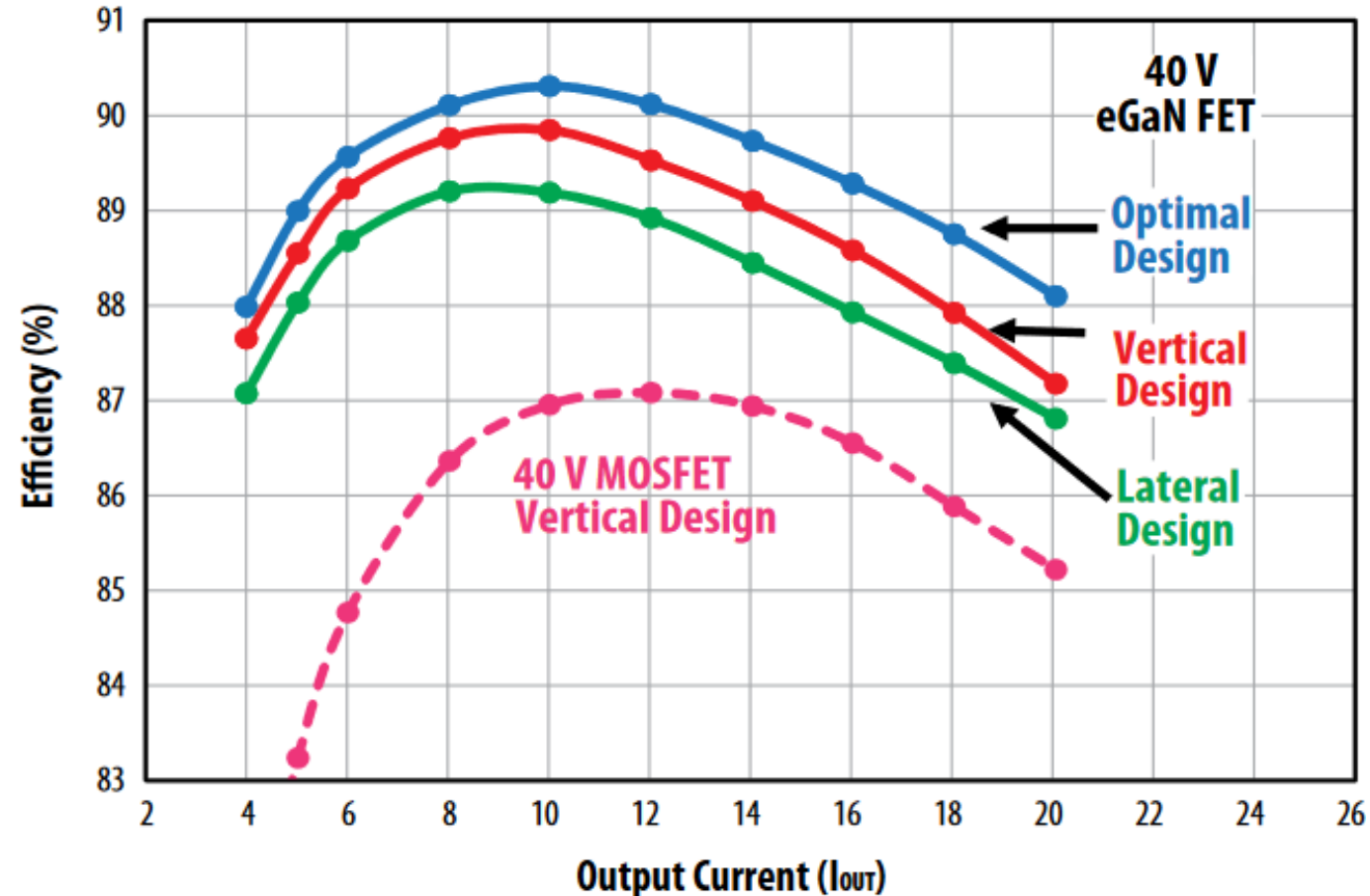- Starting with results:
 - Solid lines: same EPC GaN FET
- Free efficiency improvement
 - Due to layout
 - Same schematic, same FETs




Buck converter, 1 MHz, 12 V to 1.2 V

[App note link](#)

Layout - Noise

 - Starting with results:
 - Blue line and Green Line: same FETs, same schematic
 - EPC GaN FETs
- Free ringing improvement
 - Due to layout
 - MOSFETs don't benefit as much...




Buck converter, 1 MHz, 12 V to 1.2 V

[App note link](#)



Layout – How?

 - “Secret”: minimizing the loop inductances
 - power loop, gate loop
- Easier said than done?
- Not too difficult, because GaN FETs are:
 - Small: less board area
 - Lateral devices: active area near PCB, and no bond wires
 - Pins on GaN FETs help




Layout – How?

  - Layout options:
 - Conventional Lateral Loop




- Conventional Vertical Loop

 

(a)




(b)

 


Layout – How?

 
- Layout options:
 - Optimal Power Loop
 - Top View, (a):
 - Current path is a straight line
 - But, what about return current?
 - First inner layer
 - Ground return
 - Side View:
 - Minimal loop lateral *and* vertical



(a)

 



(b)

 

[app note link](#)



Layout – Variations

 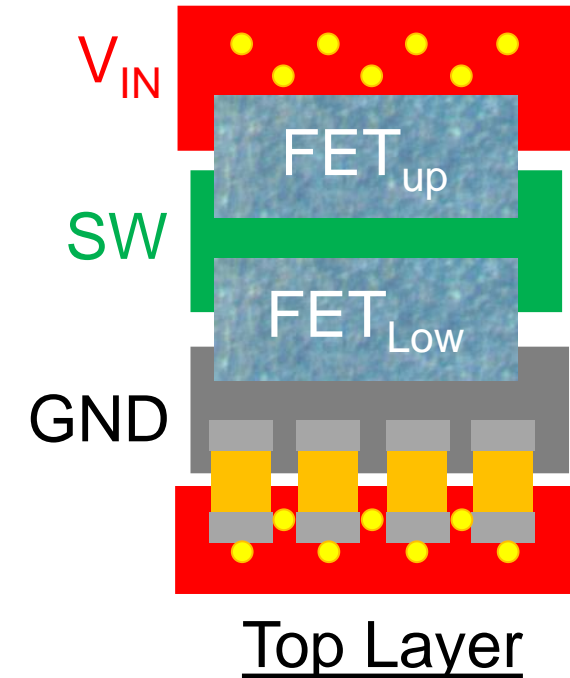- Variations on the Optimal Layout
- Half bridge is a current loop circle of 3 components:
 - Top FET
 - Bottom FET
 - Capacitor(s)
 - So: 3 variations (so far...)
- “Rotate” the loop:
 - Vin buried (first inner layer)
 - Good for top FET cooling



Layout – Variations

  - Variations on the Optimal Layout
- “Rotate” the loop, 3rd option:
 - Switch node buried (first inner layer)
 - Reduces E-field EMI
 - Capacitors in the middle



SW is inner layer return

Bus capacitors between the FETs

Layout – System

- How about the Inductor?
 - dv/dt
 - Würth: polarized inductor
 - Input = switch node \rightarrow close to PCB / ground
 - Output = DC level \rightarrow “up in the air”
 - Flatter inductors help


 
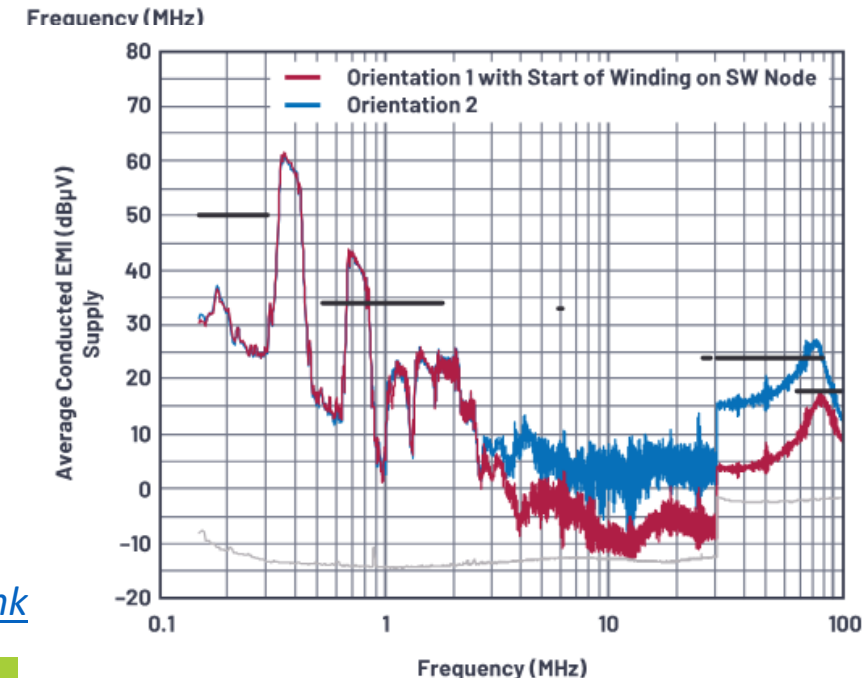


Figure 6: [WE-XHMI](#) and [WE-PD2](#) with the 'dot' identifying the location of the start of the winding.

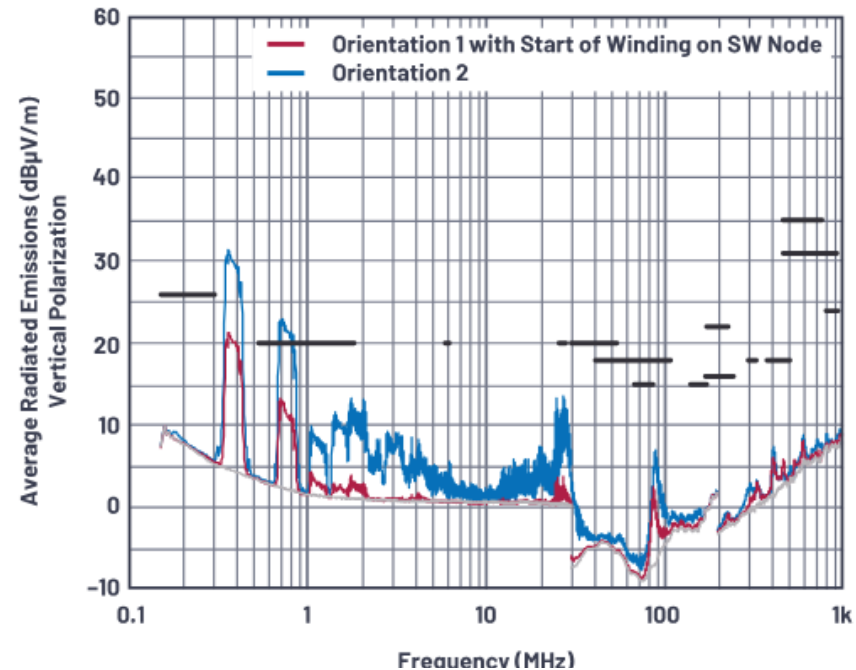

Source: Analog Devices, test of Würth 74439346150 high performance inductor; [Link](#)

Parasitic inductances


1. Common source inductance
2. Power loop inductance
3. Gate loop inductance

[WP010: Optimizing PCB Layout](#)



[How to GaN 05](#)

[How to GaN 05a](#)




- Turn-on
- Turn-off

 

Impact of Common Source Inductance

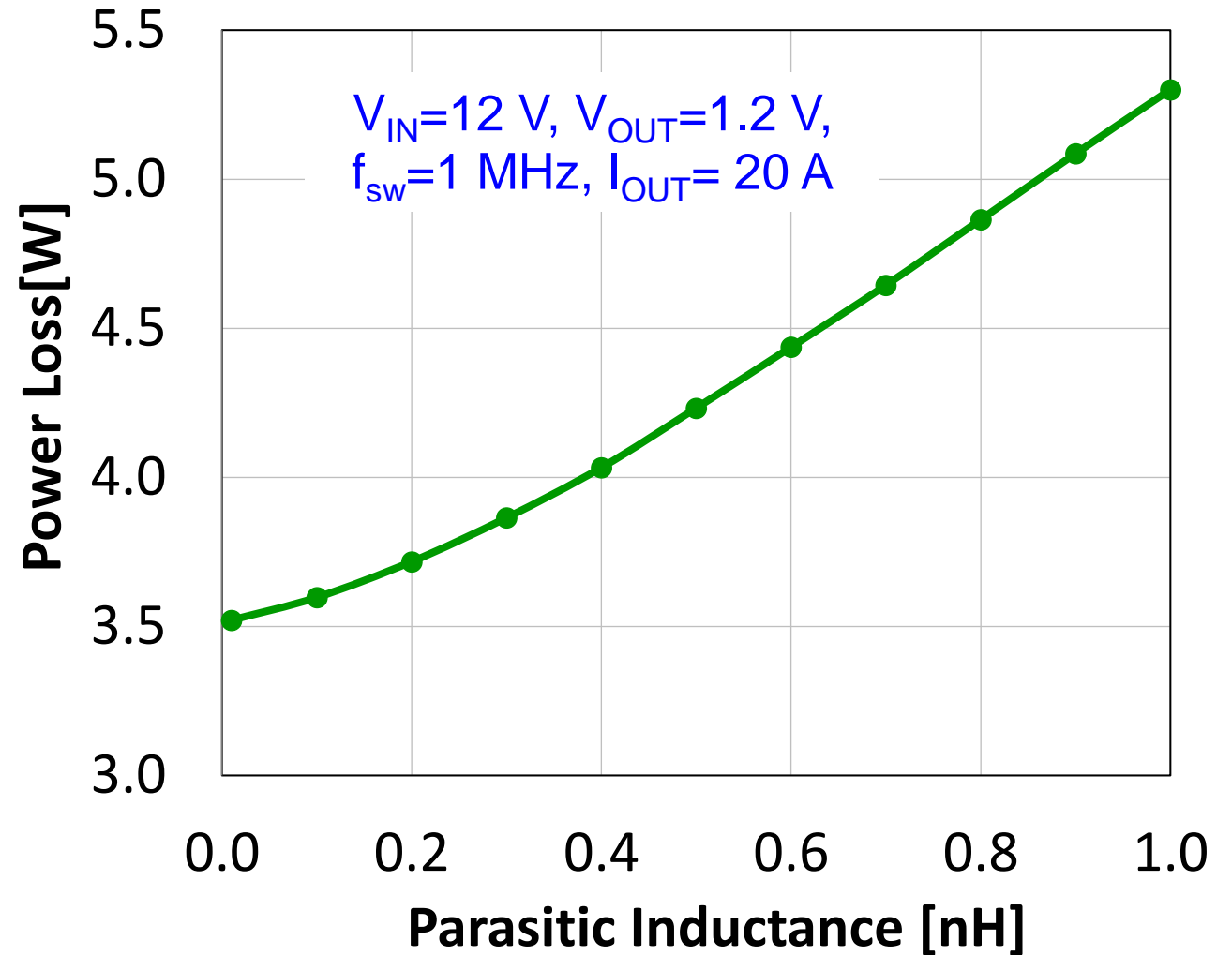
 


Impact of Power Loop Inductance


 
 
 


Impact of Gate Loop Inductance

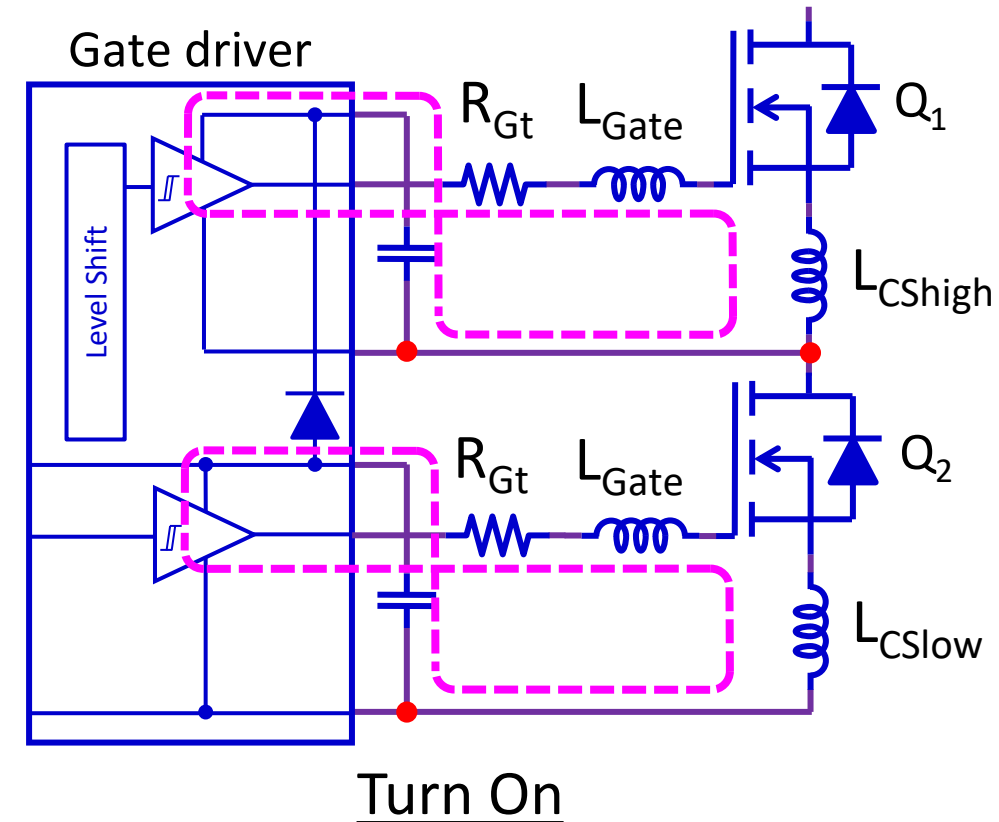 - Two loops to consider: Turn-on & Turn-off
- L_{Gate} requires R_{Gt} to damp ringing overshoot
 - slows transition




Layout Comparisons

    


Top Layer
Mirror (Inner Layer 1)

Lateral

 

Top Layer
Bottom Layer


External Vertical

 


Top Layer
Inner Layer 1

Internal Vertical


Layout Inductance Comparison

 



Lateral

 

Ext. Vertical

 



**Int. Vertical
Best Choice**

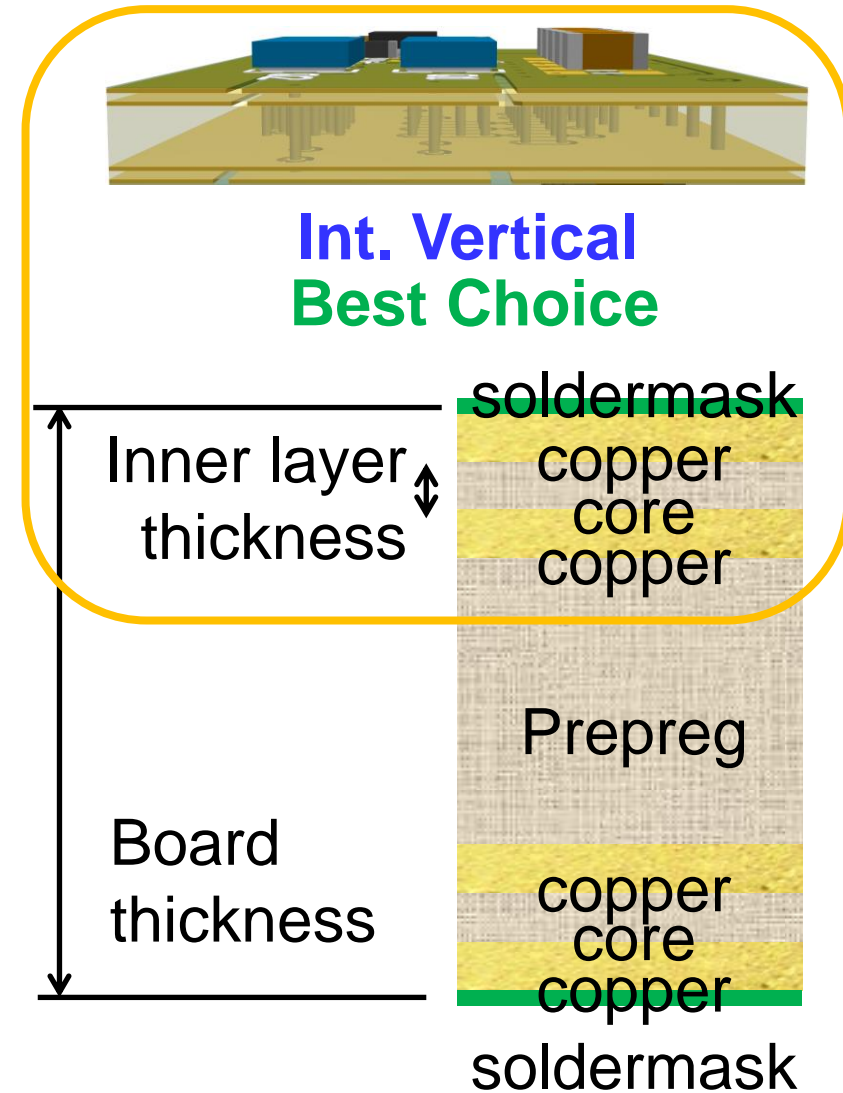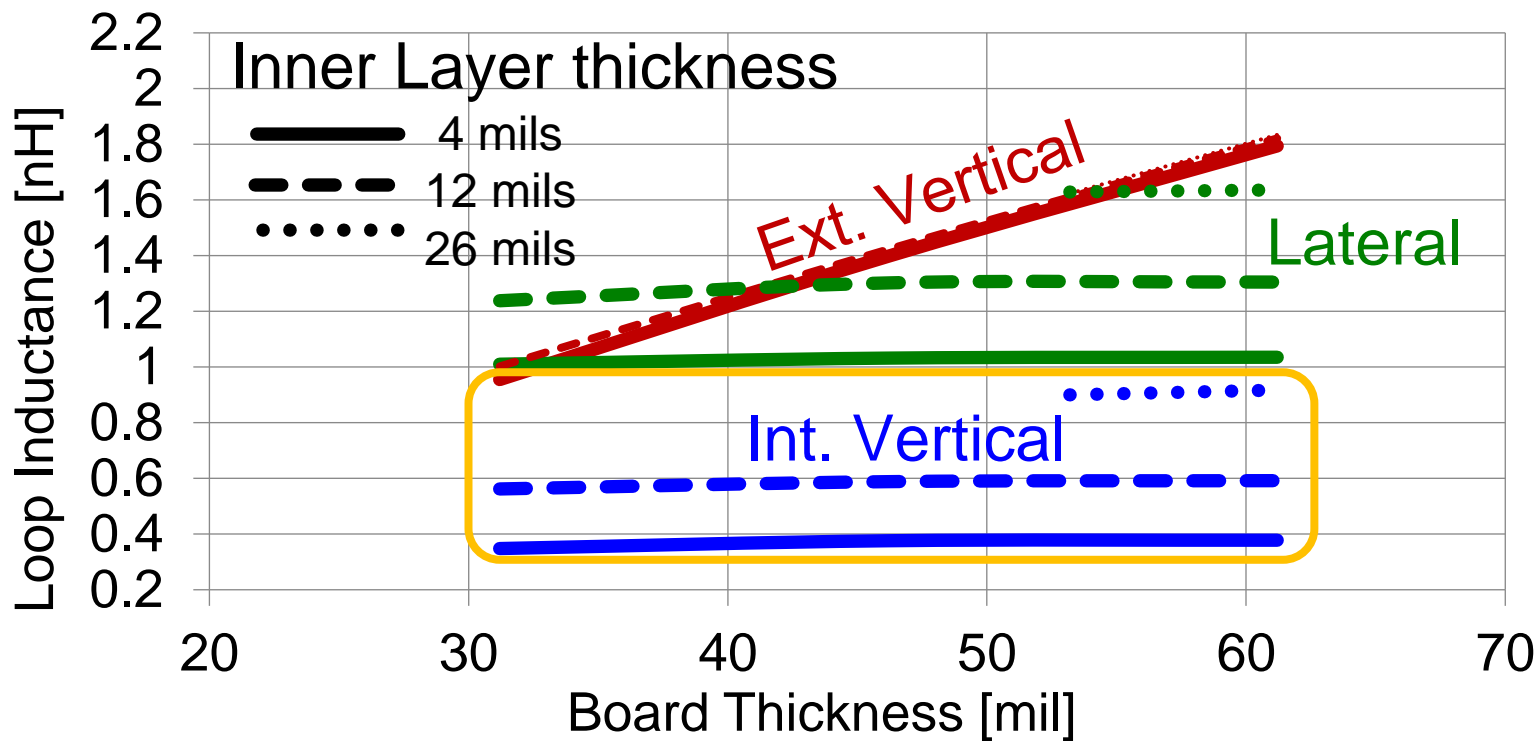

Designing a Low Inductance Layout

Internal vertical (optimal) power loop:

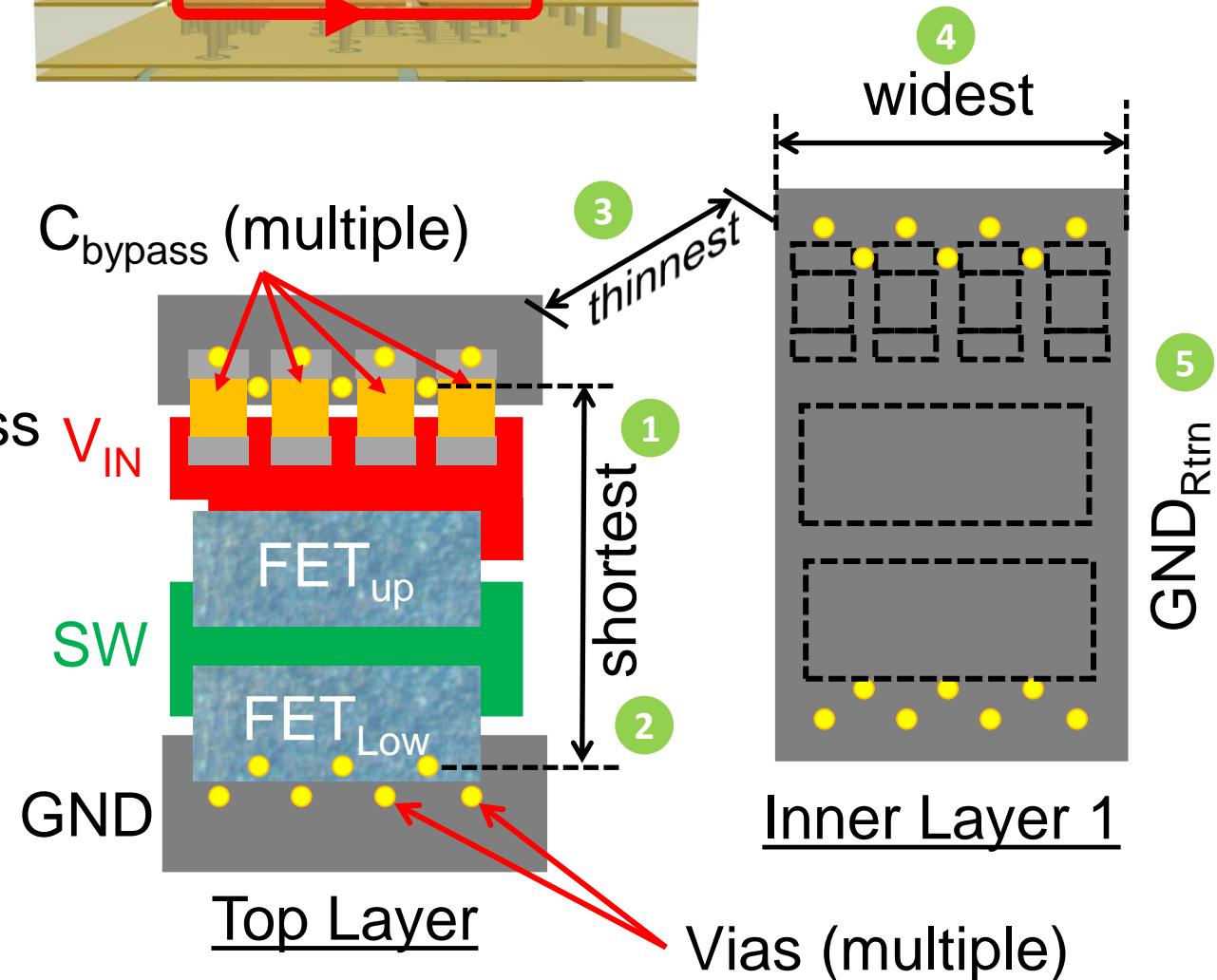 
1. Place components as close as possible
2. Place (many) vias as close to the innermost electrical connection
3. Thinnest permissible substrate thickness between outer and first inner layer
4. Spread out via connections at innermost connect
5. GND return does not need to carry the full current




Alternative Layout Configurations

- Improves cooling for upper FET
- Useful for specific layout restrictions

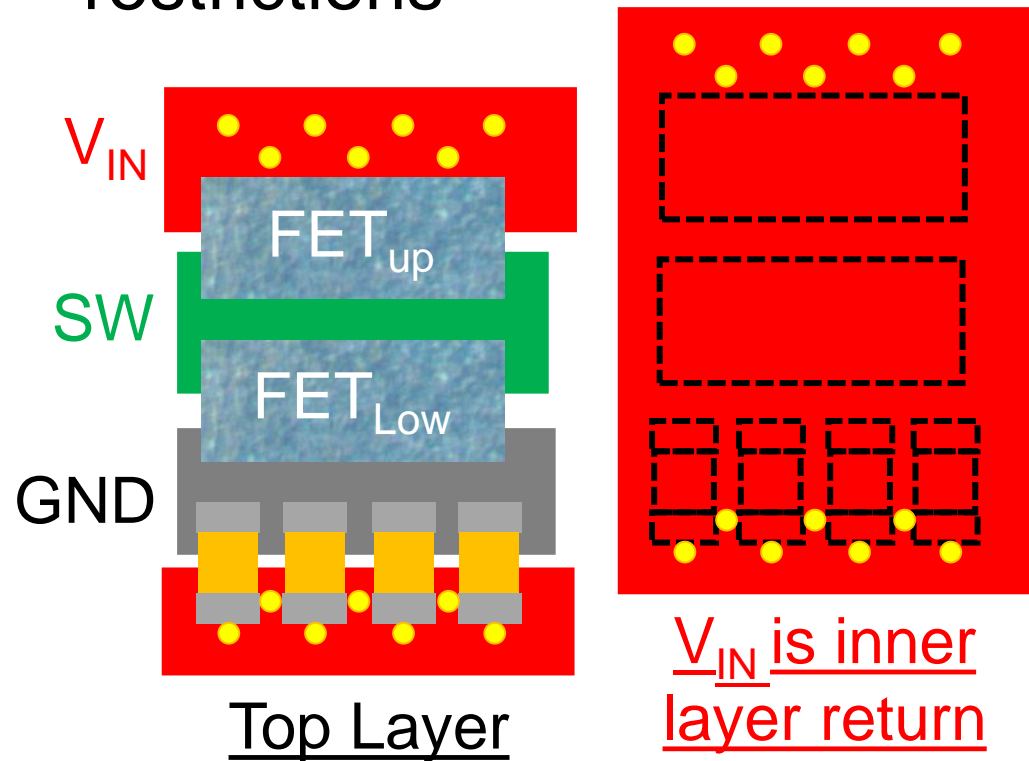- Buries SW-node inside the board
 - Reduces E-field EMI




Bus capacitors beside lower FET

 

Bus capacitors between the FETs


What About the Gate Connection

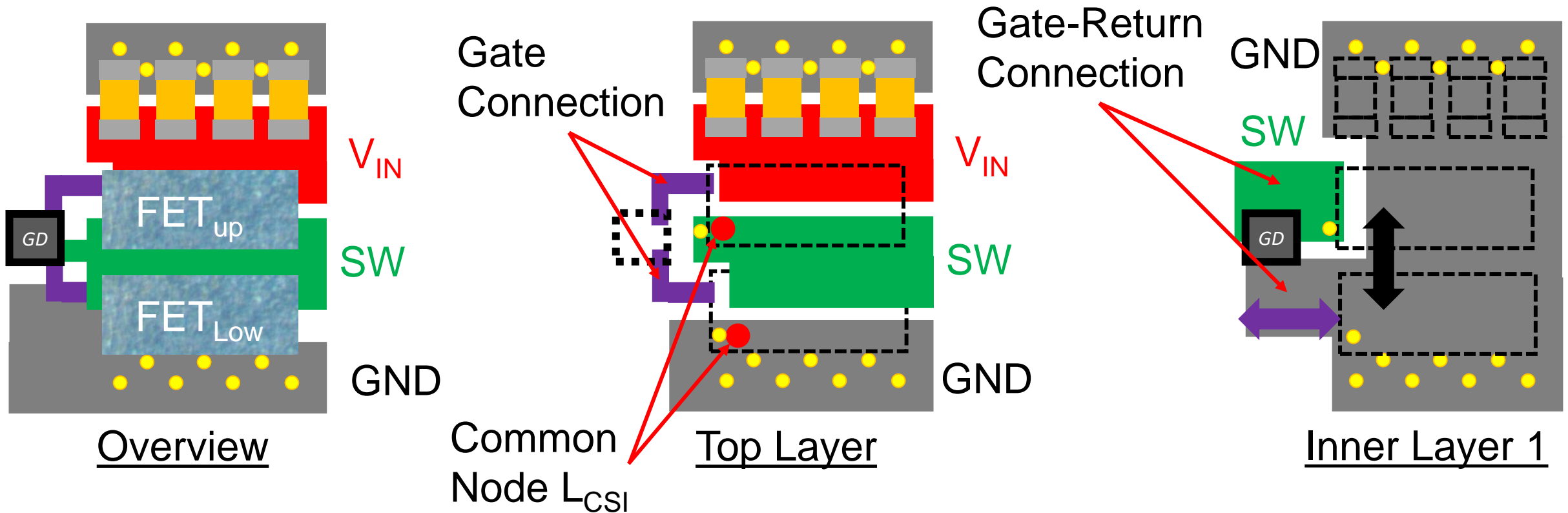- Gate drive track with return polygon (its source!) on next layer
- Orthogonal gate to power connection reduces coupling between them



To Kelvin or not to Kelvin?

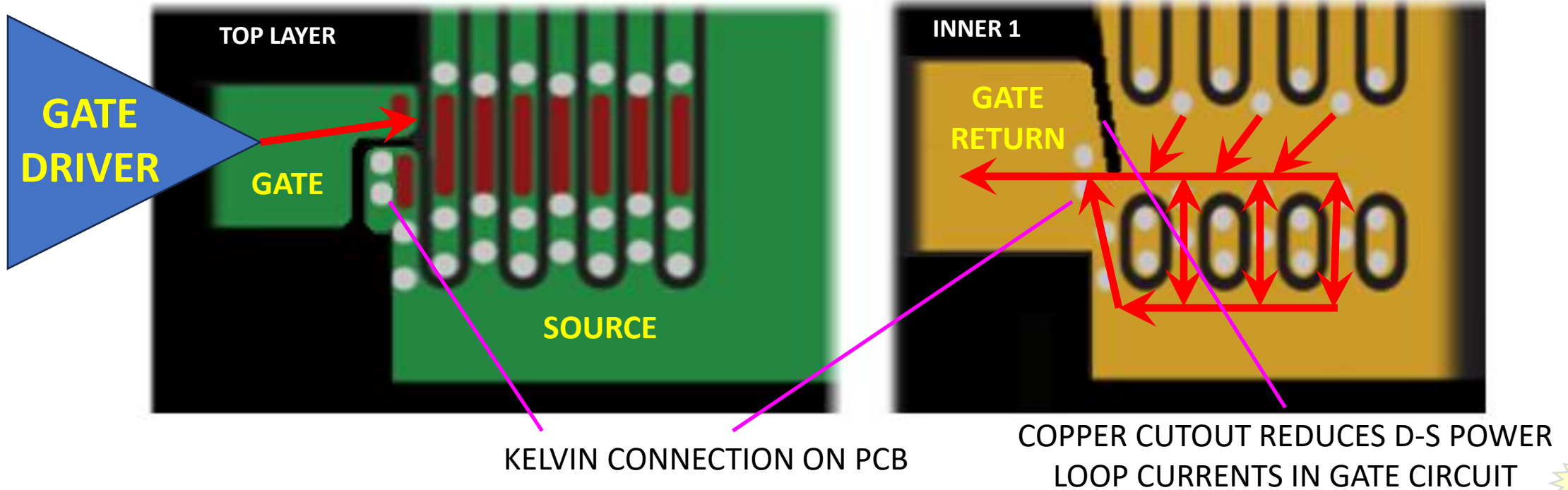
- Connect **ALL** the source pads together
- place one or few vias near to the source pad closest to the gate pad
- those vias will be the only connection between power loop and gate return polygon: this is the Kelvin connection






Via Construction

Via-In-Pad-Plated-Over (VIPPO)

 - Wall thickness = 20 μm per IPC standard class 2
- Hole diameter (typical) = 0.2 mm
- Annular ring = 0.35 mm minimum
- Plated over
- Non-conductive filled
- Tented on both sides of the board
- Used for under bump and close to component pads
- Usable up to 2 oz (2.8 mil / 70 μm) copper thickness
- **IPC4761 Via Type VII**




Layout – Parallel half bridges

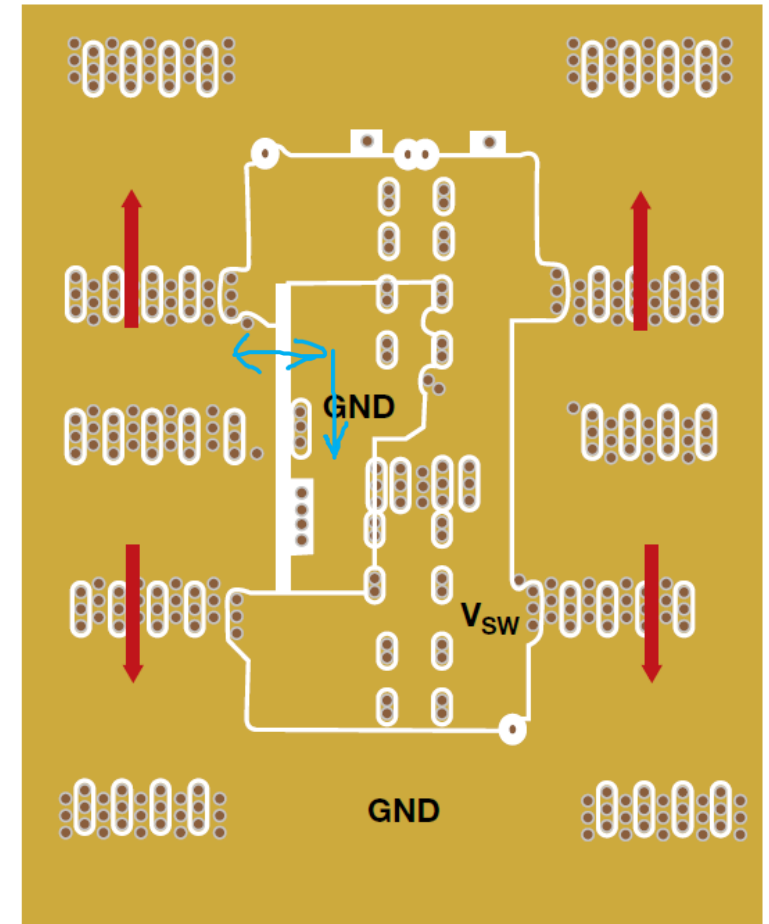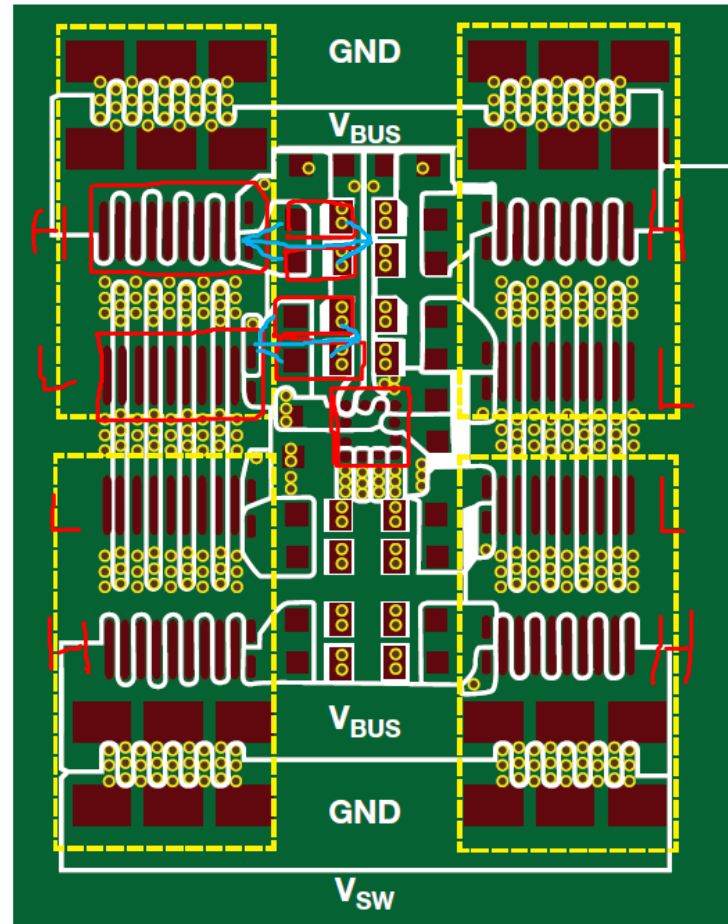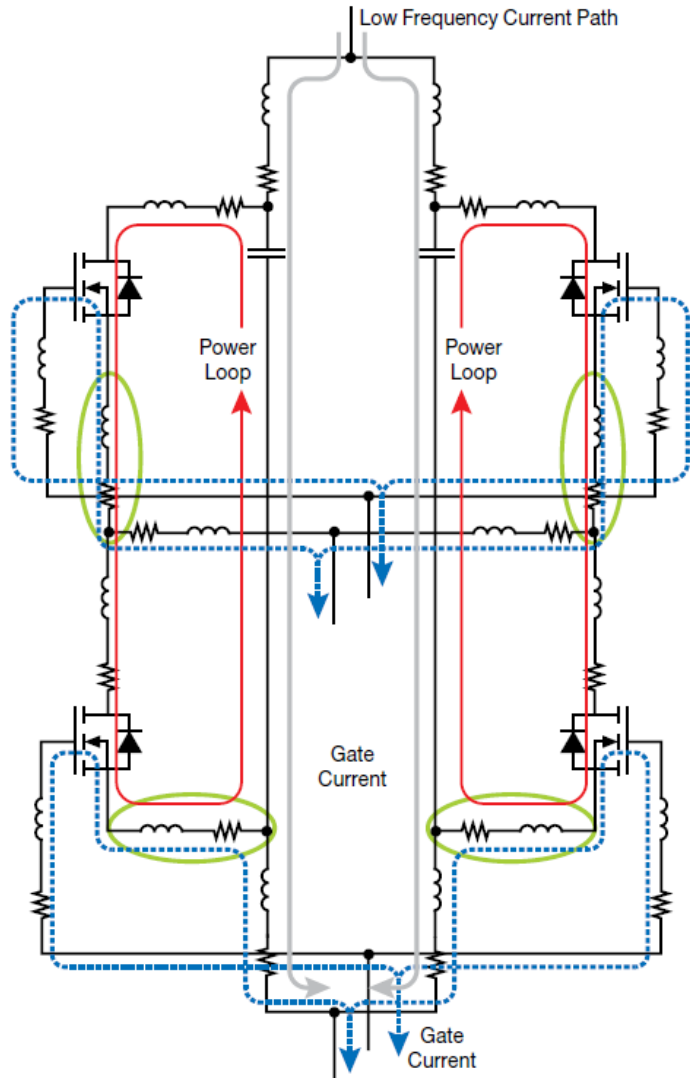

Layout Shortcuts *(how to cheat)*



Shortcut #1

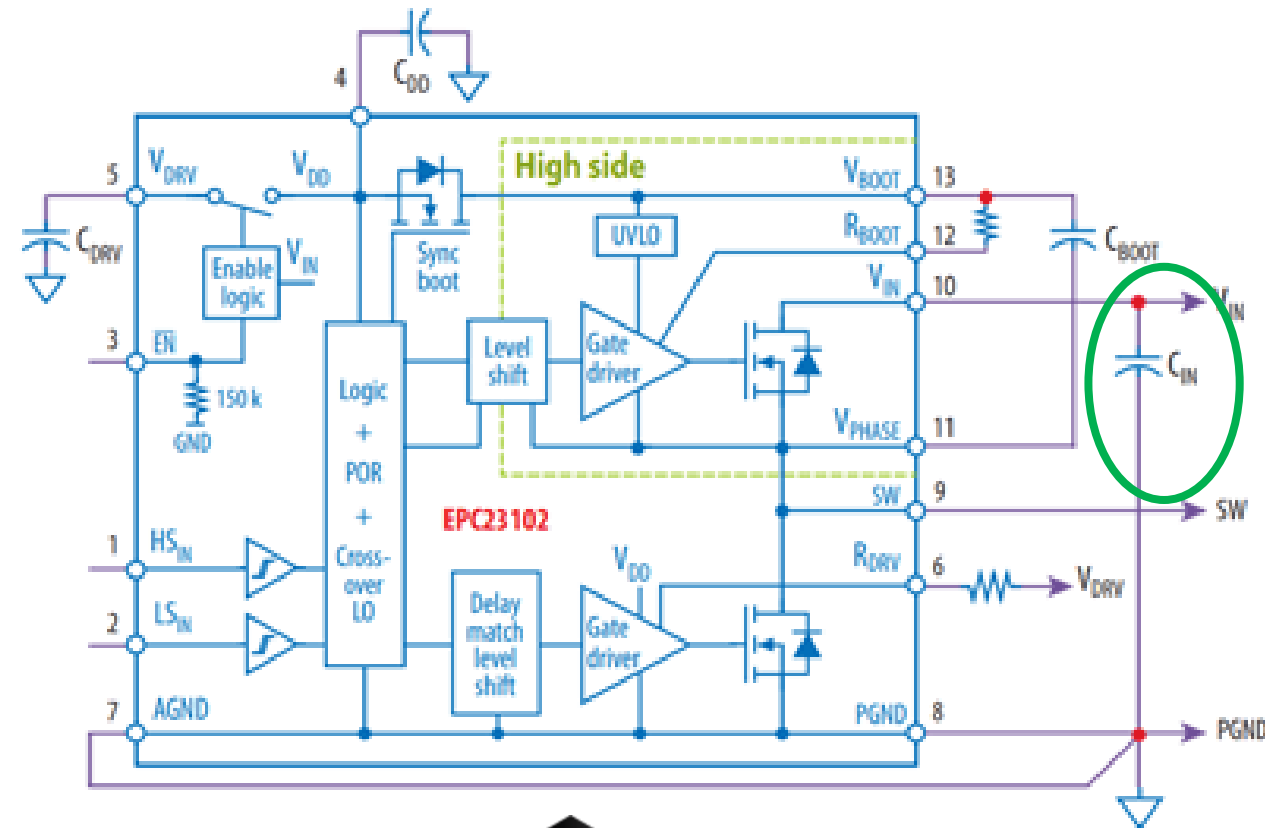- Want to avoid most of the Power Loop and Gate Drive layout?
 - Yet get the benefits of good layout?
- EPC's new Power Stages
- Gate drive: internal
- Power Loop: mostly internal
- Remaining: **decoupling capacitor**



Power Stages in QFN

	EPC23102	EPC23103	EPC23104	EPC23101	EPC2302
V_{DS}	100 V	100 V	100 V	100 V	100 V
$R_{DS(on) (max)}$	6 mΩ	8 mΩ	10 mΩ	3.3 mΩ	1.8 mΩ
I_{DC}	35 A	20 A	15 A	65 A	101 A
Package	QFN 3.5mm x 5mm			QFN 3.5mm x 5mm	QFN 3mm x 5mm
Samples	Now	Now	Now	Now	Production

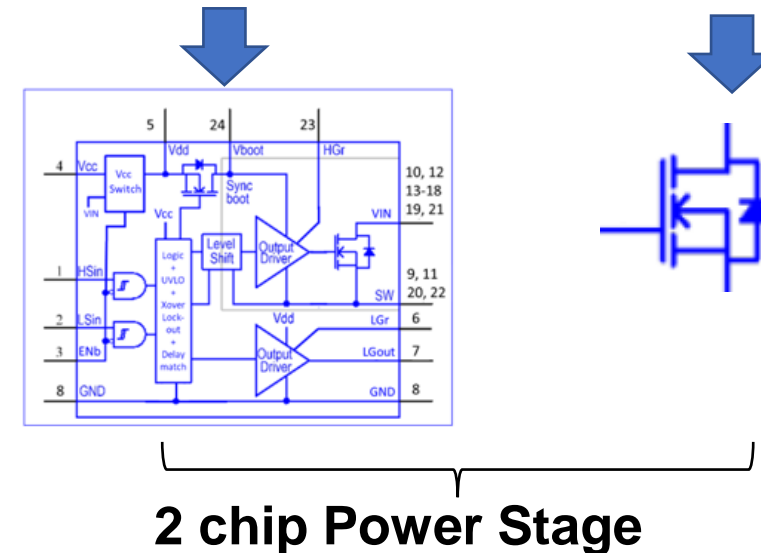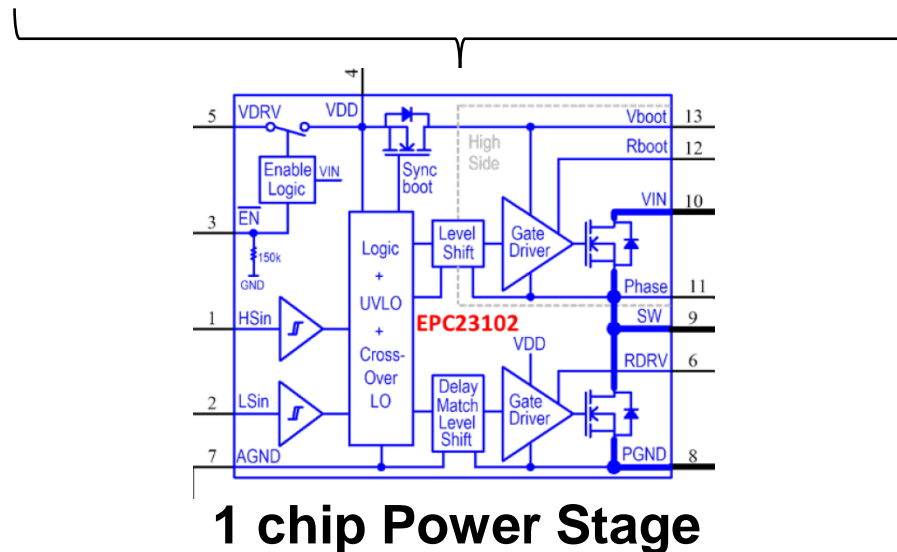

Shortcut #2



- Want to have a good layout, using discrete GaN FETs?
- Copy a reference design!
- Example: DC-DC
 - Board part # EPC9195
 - Input 36 – 60 V, output 13 V @ 16 A
- Online: Gerbers, schematics, etc.
 - [Link to home page](#)
 - Altium files available upon request



Buck Converter – ADI controller





  - EPC9158 -based
- 2-phase buck converter
- EPC9158: includes new, very efficient ADI controller
 - LTC7890
 - 500 kHz
 - Output power:
 - With FETs now on EPC9158 board: 600 W
 - FETs = Gen 5, EPC2218... better with Gen 6



Other Topics

eGaN FETs in 3x5 mm QFN

  


	<i>EPC2361</i>	<i>EPC2302</i>	<i>EPC2306</i>	<i>EPC2305</i>	<i>EPC2308</i>	<i>EPC2304</i>	<i>EPC2307</i>
V_{DS}	100 V	100 V	100 V	150 V	150 V	200 V	200 V
$V_{DS, \text{transient}}$	120 V	120 V	120 V	170 V	180 V	240 V	240 V
$R_{DS(on) \text{ max}}$		1.8 m Ω	3.1 m Ω	3 m Ω	6 m Ω		10 m Ω
$R_{DS(on) \text{ typ}}$	1.0 m Ω	1.4 m Ω	2.5 m Ω	2.2 m Ω	4.5 m Ω	3.1 m Ω	8.2 m Ω
$Q_G \text{ typ}$	28 nC	23 nC	12.3 nC	22 nC	11.7 nC	24 nC	10.6 nC
$Q_{GD} \text{ typ}$	2.5 nC	2.3 nC	1.1 nC	2.1 nC	1 nC	2.5 nC	1.3 nC
Q_{OSStyp}	86 nC	85 nC	44 nC	103 nC	50 nC	116 nC	58 nC
$Q_{RR} \text{ typ}$	0 nC	0 nC	0 nC	0 nC	0 nC	0 nC	0 nC
$R_{\theta JC}$	0.2 °C/W	0.2 °C/W	0.5 °C/W	0.2 °C/W	0.5 °C/W	0.2 °C/W	0.5 °C/W
I_D	101 A	101 A	62 A	102 A	63 A	102 A	48 A
Production	Q2 2025	Now	Now	Now	Now	Q4 2024	Q4 2024

note: preliminary specs in *italics*



Synchronous Rectification

 - Advantage of GaN FETs
 - Smaller
 - No reverse recovery (no Q_{rr})
 - Faster switching
- But what about EMI?



Synchronous Rectification

- dv/dt
 - But turn-on and turn-off of FETs at low voltage
- Ringing
 - No C_{rr} (reverse recovery capacitance)
 - Shown to be an EMI concern for MOSFETs
- Size and Layout
 - Small size limits loop
 - GaN is lateral: active area nearest the board

Summary

- Advantages of GaN FETs
 - Small, for good board placement
 - Lateral device, for current closer to the board
 - Higher frequency, for smaller EMI filters
 - No reverse recovery charge (no Q_{rr})
- Optimized Layout Benefits
- Layout Details
- Shortcuts: GaN power ICs, EPC reference designs




Click on images to learn more




How To GaN Video Series


epc-co.com

 

4th Edition Textbook

 

eGaN[®] FETs and ICs

 

Evaluation Kits