

Constant-On-Time, Peak Current Mode, or Zero Delay PWM: How to Make the Right Decision?

POWER LIKE A BOSS Seminar

-Monolithic Power Systems/WE


April, 2024

Harras El Mehdi:
elmehdi.harras@monolithicpower.com




Voltage Mode Control – Method of Operation

Legend
 Fast Change: ↑
 Slow change: ↑

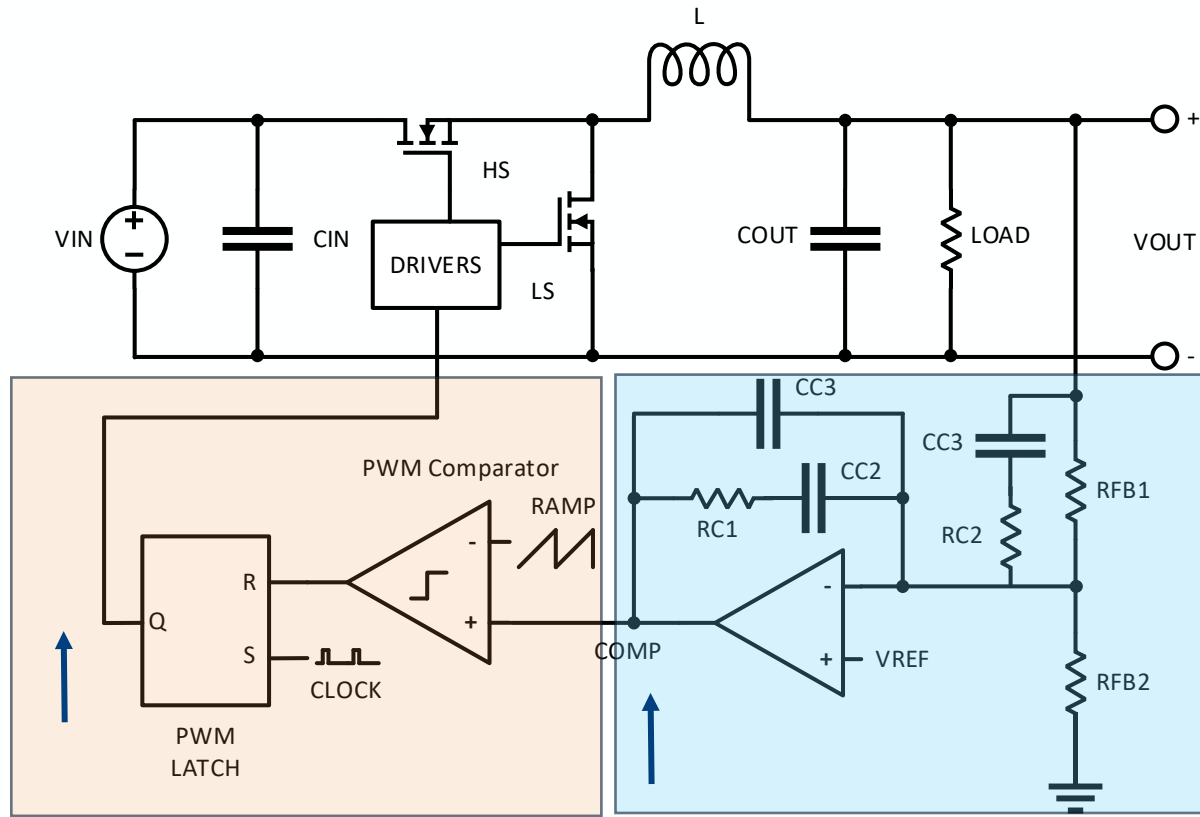

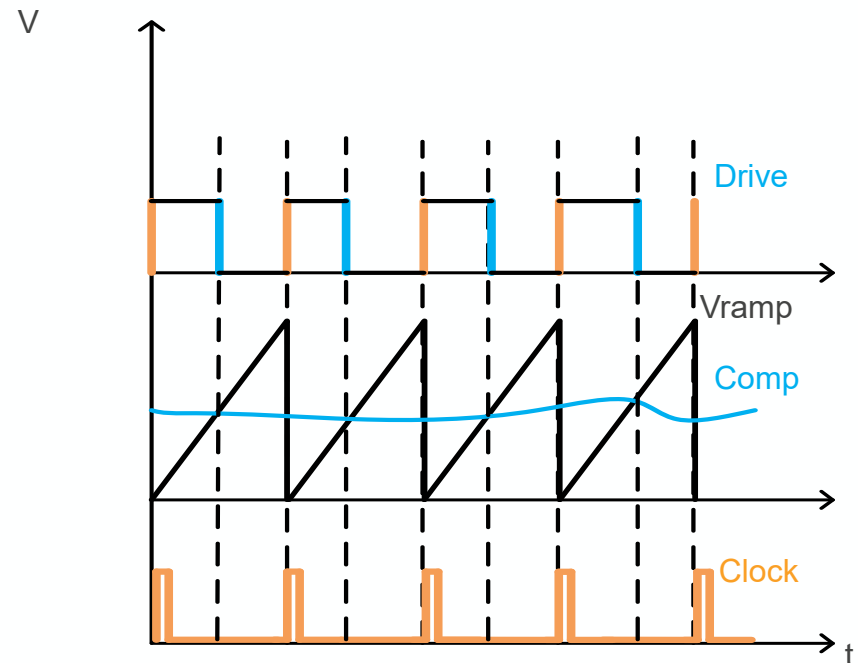1. Sudden load current increase causes VOUT to drop




3. COMP increases causes duty cycle to increase

Slow Loop → Voltage



2. VOUT drop causes COMP to increase

Stability is sensitive to Vin, Cout, and Iout!!!

Voltage Mode Control – Pros and Cons

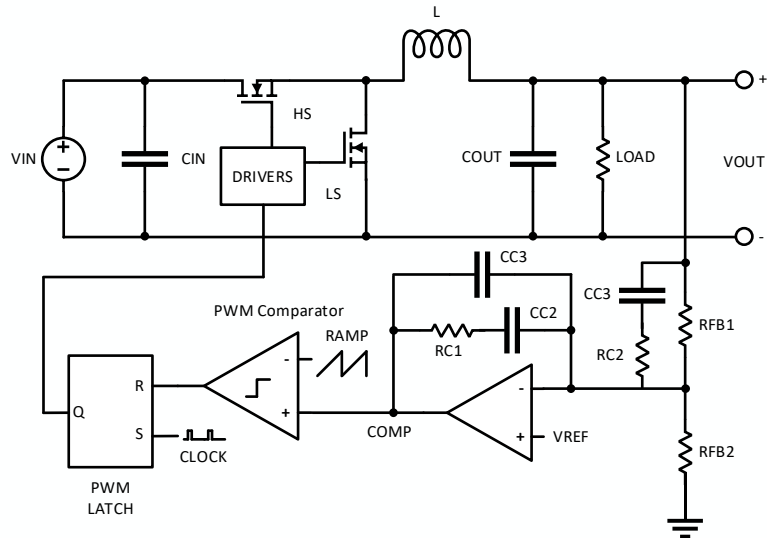

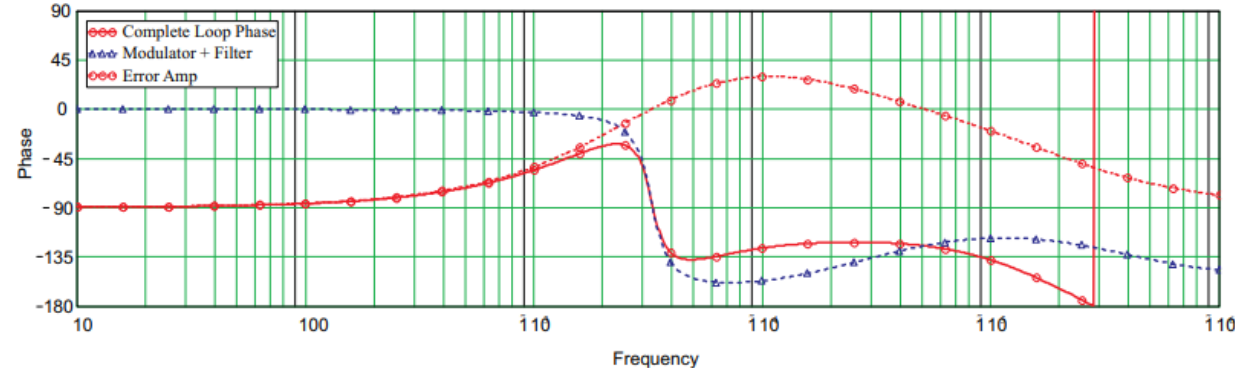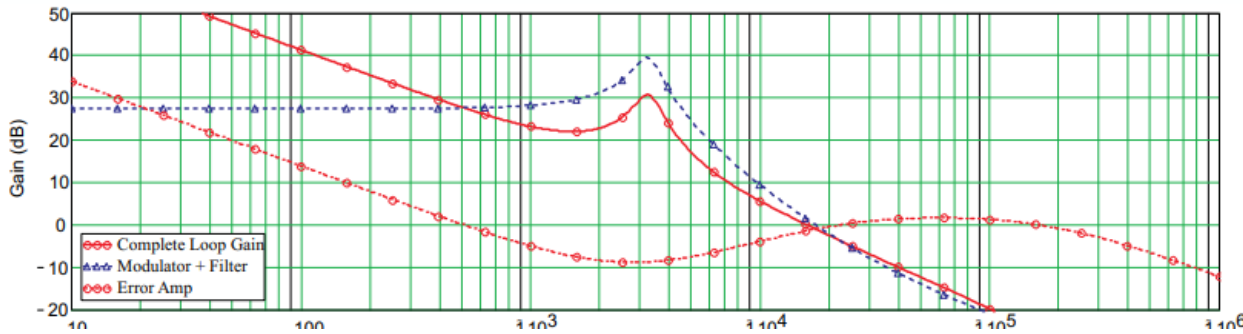
- + Simplest Control Method 😊
- + Good noise immunity 😊
- Due to undamped LC output filter, requires high ESR capacitors or type III compensation 😞
- Control loop gain is inversely proportional to V_{IN} , so crossover gain will shift as V_{IN} change. 😞
- Line transient performance is poor. Load transient performance is okay 😞




Control loop gain and line transient performance can be mitigated if ramp is made proportional to V_{IN} .

How Is The Control Method Evolving? – Peak Current Mode Control

Legend
 Fast Change: ↑
 Slow change: ↑

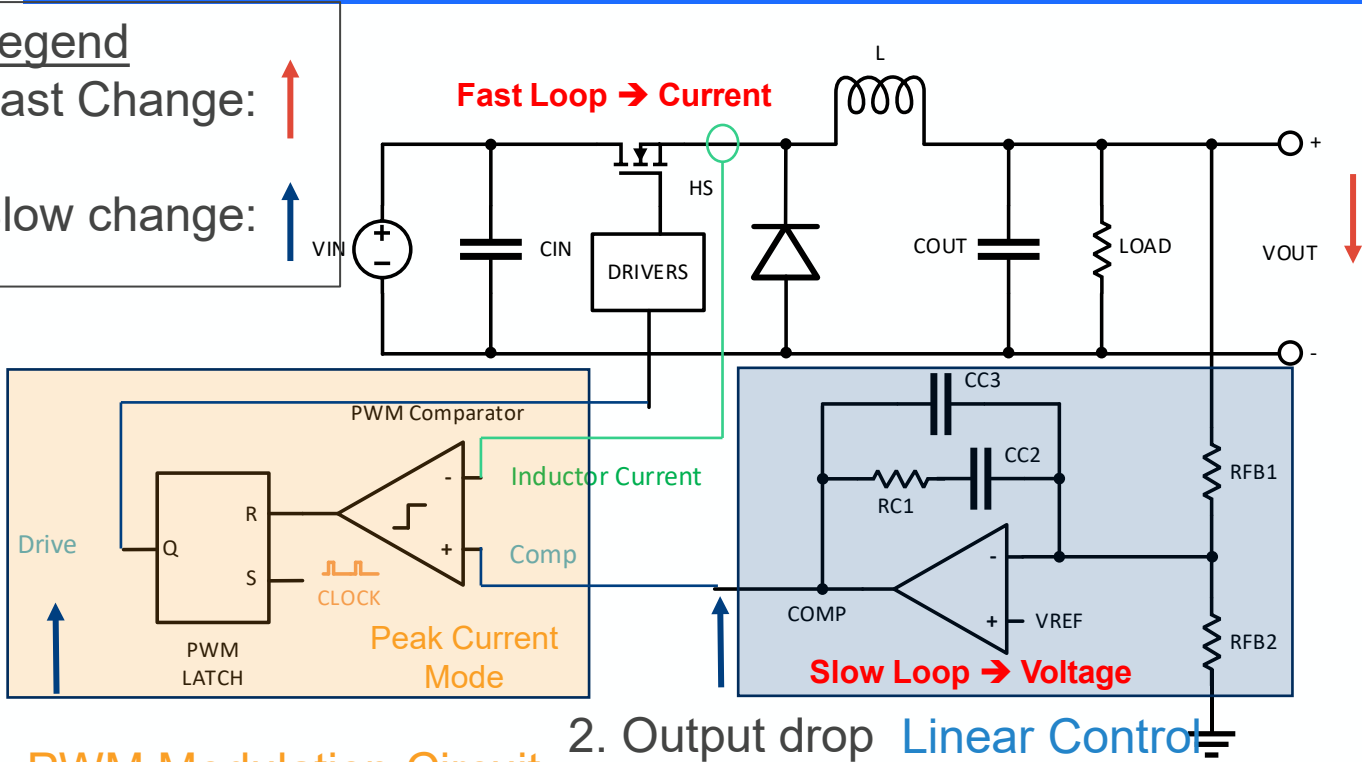

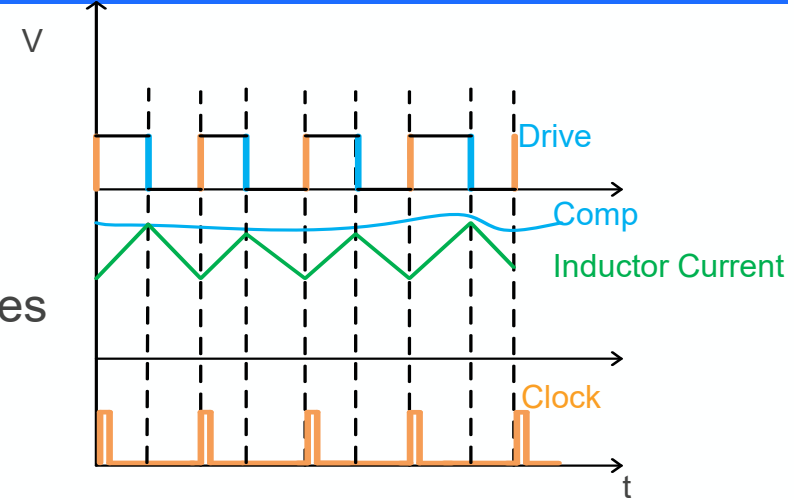1. Sudden Current Increase causes output to drop




PWM Modulation Circuit



3. Comp increases causes duty cycle to increase

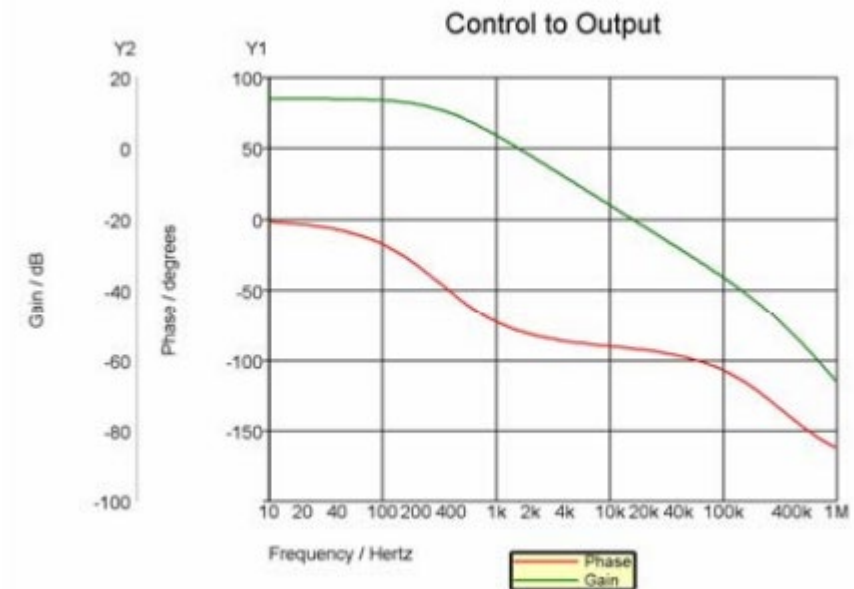2. Output drop causes comp to increase

- Get rid of the double pole
- Power stage bode plot likes RC filter
- Stability is not sensitive to V_{in} , C_{out} and I_{out}






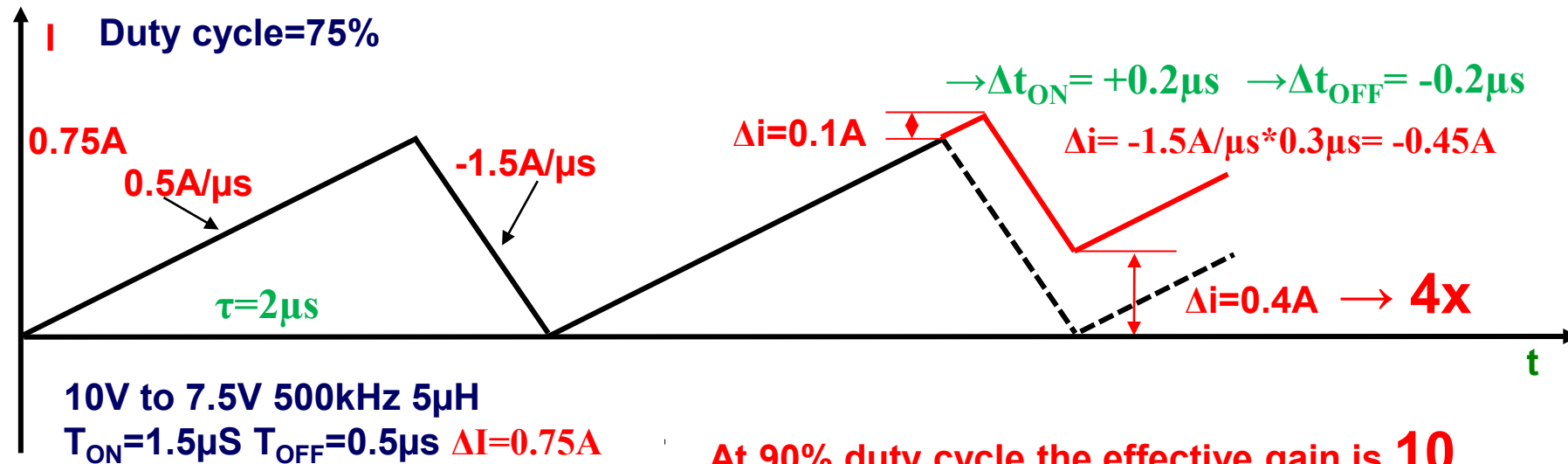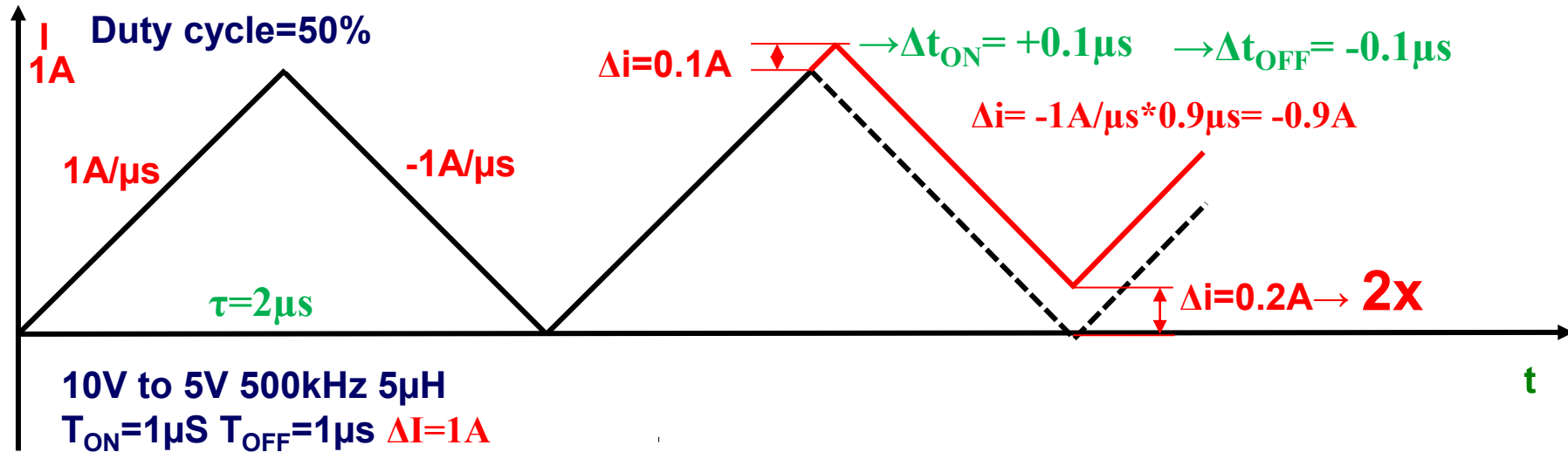Slope Problem in fixed frequency peak Current Mode




At 90% duty cycle the effective gain is **10**

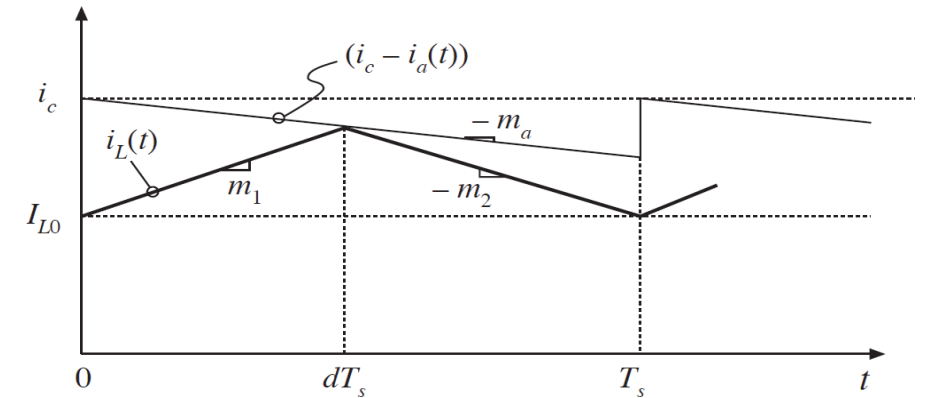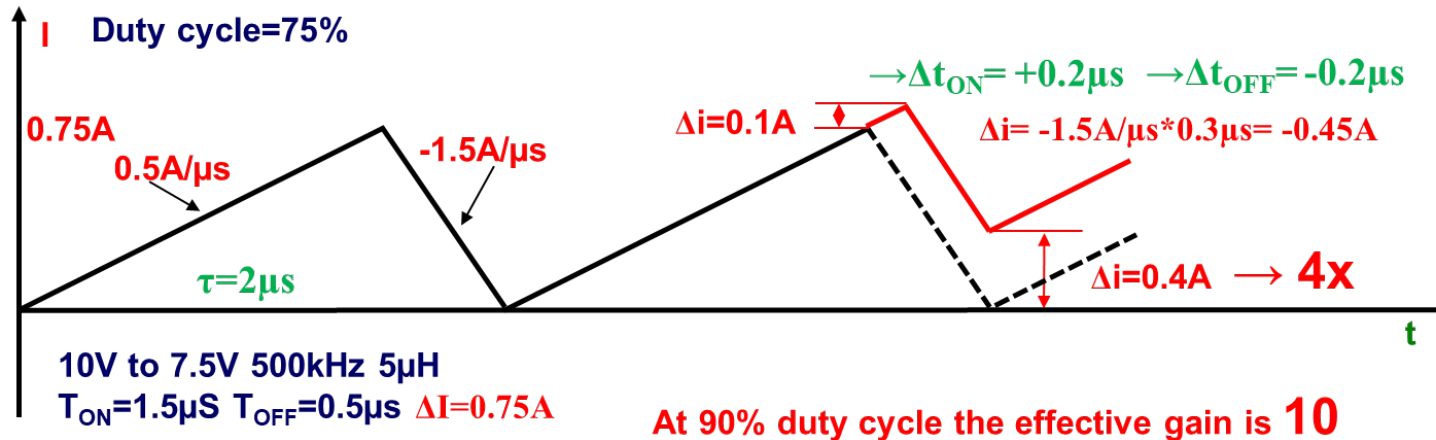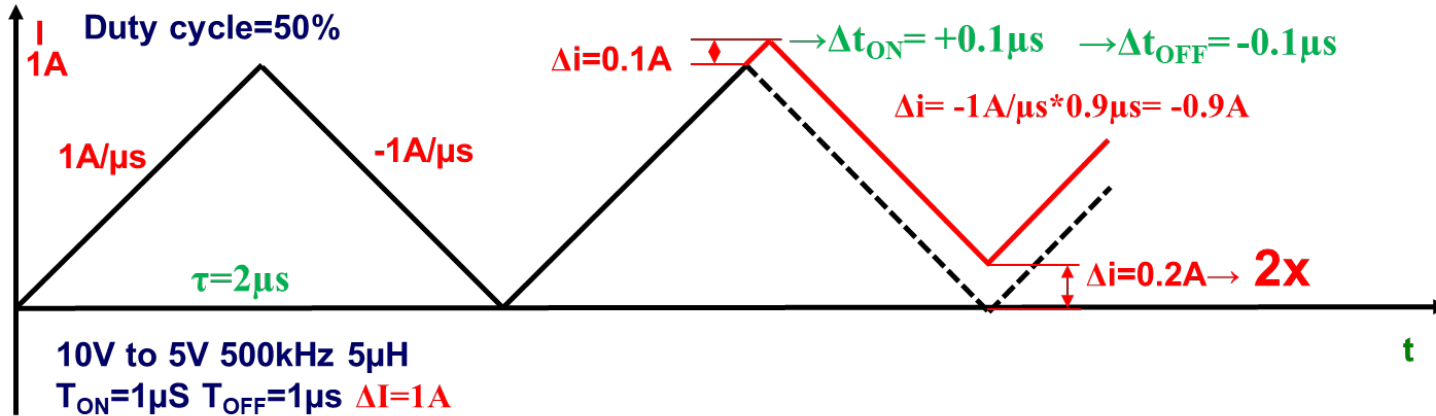
Slope Problem in fixed frequency peak Current Mode



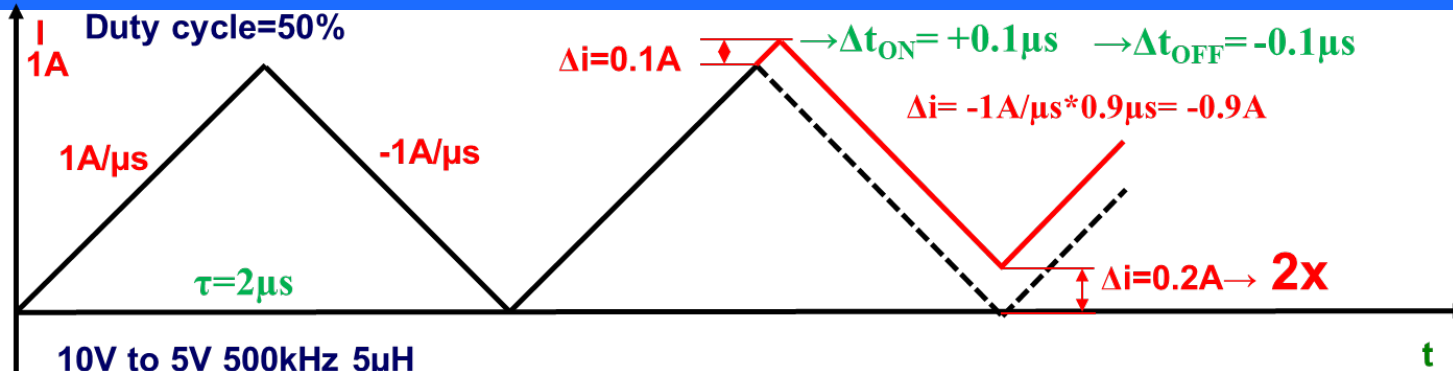Slope Problem in fixed frequency peak Current Mode




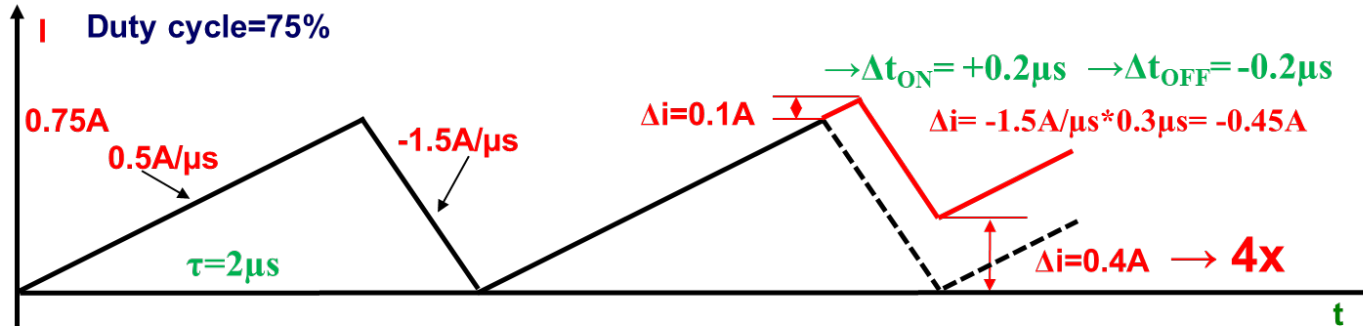10V to 5V 500kHz 5μH
 $T_{\text{ON}}=1\mu\text{s}$ $T_{\text{OFF}}=1\mu\text{s}$ $\Delta I=1\text{A}$




10V to 7.5V 500kHz 5μH
 $T_{\text{ON}}=1.5\mu\text{s}$ $T_{\text{OFF}}=0.5\mu\text{s}$ $\Delta I=0.75\text{A}$

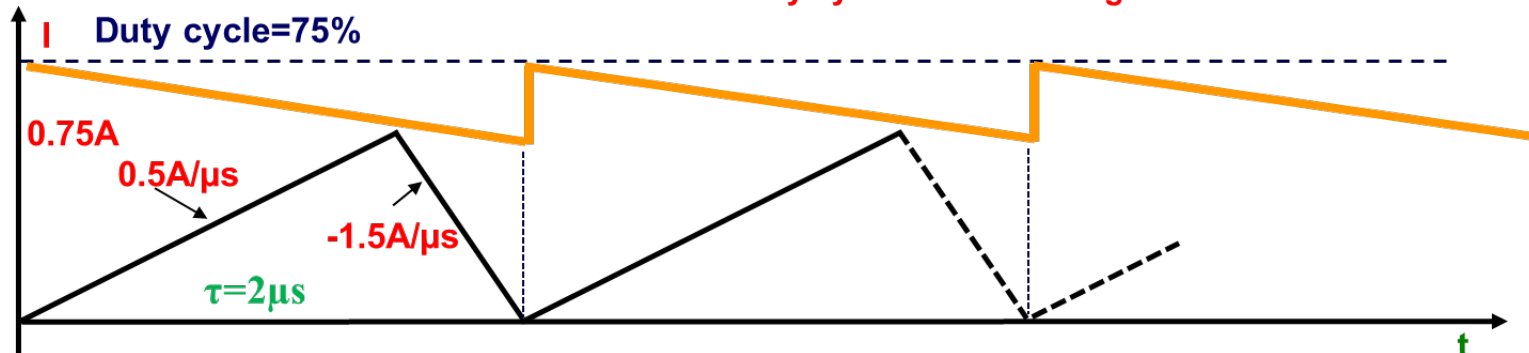At 90% duty cycle the effective gain is 10



10V to 7.5V 500kHz 5μH
 $T_{\text{ON}}=1.5\mu\text{s}$ $T_{\text{OFF}}=0.5\mu\text{s}$

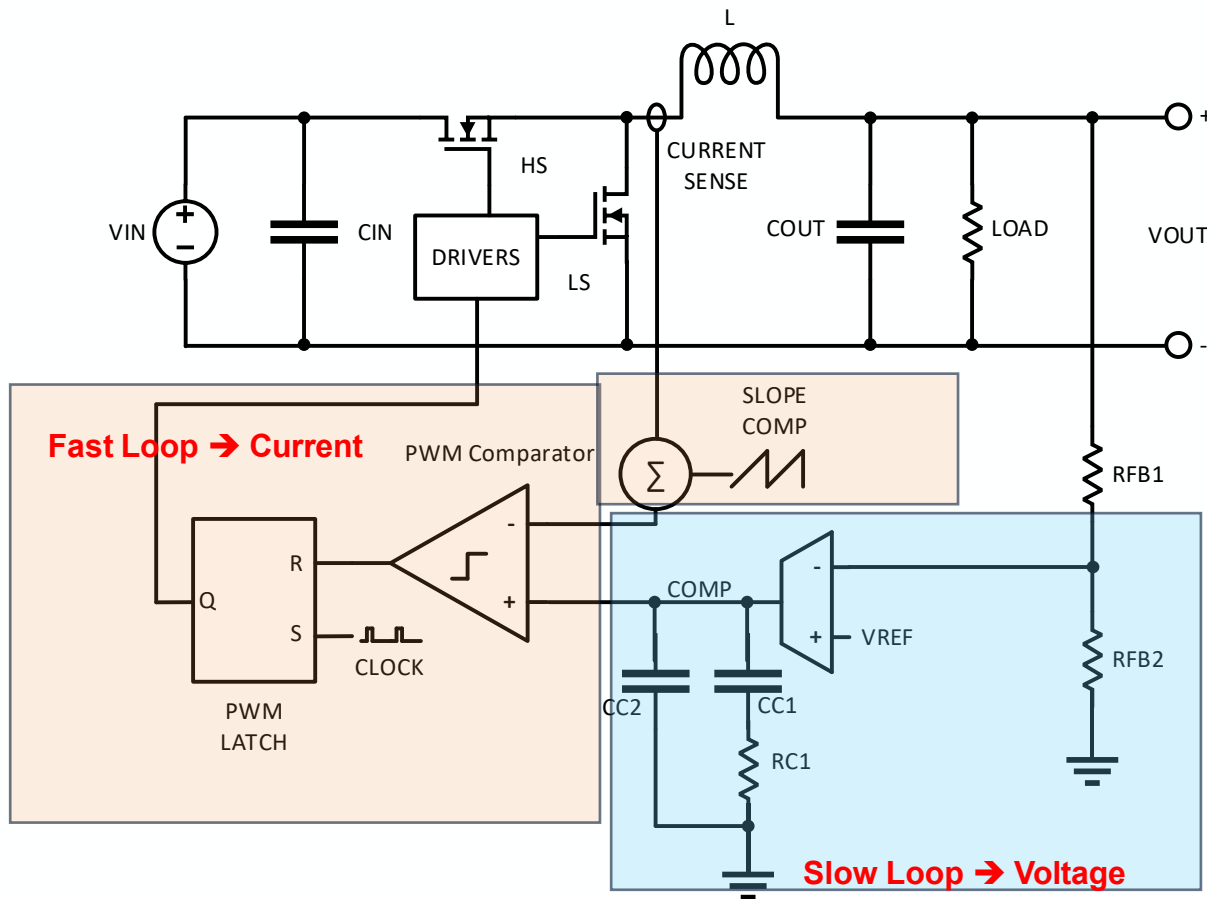Peak Current Mode Control – Pros and Cons




- + Current feedback acts as a lossless resistor damping the output LC filter, so only type II compensation is required. 😊
- + Stable crossover with V_{in} 😊
- + Good line transient performance 😊
- Okay load transient performance 😞
- Requires current sensor 😞
- Requires slope compensation for $>50\%$ duty cycle 😞
- Large min on time limits minimum conversion ratio 😞


Constant-On-Time (COT) Control

For applications where fast transient responses are required, current mode control is not fast enough.

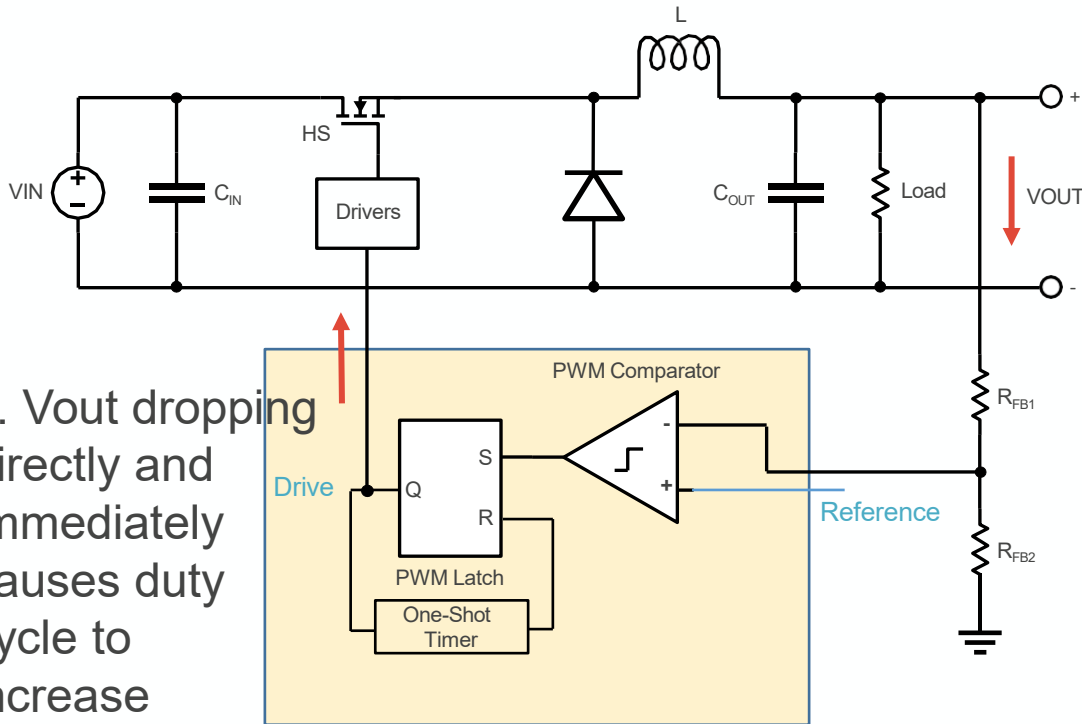- **Goal:** Faster transient response
- **Thought Process:** Transient response can be improved by not waiting for the clock.
- **Solution:** Use constant-on-time (COT) control to fix the on time while allowing the frequency to change.



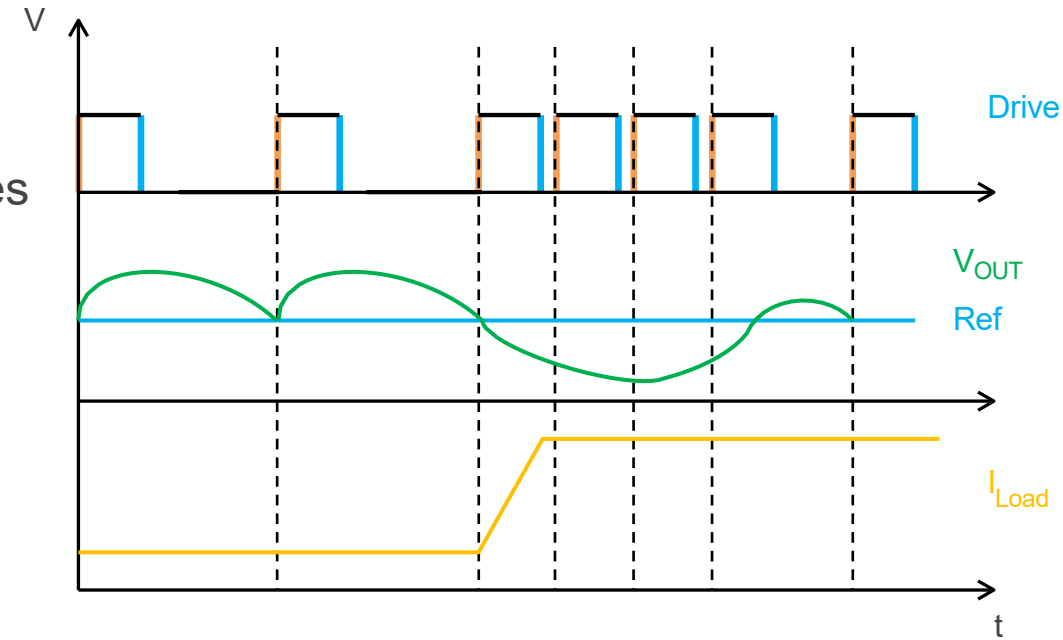1. Sudden Current Increase causes output to drop




2. Vout dropping directly and immediately causes duty cycle to increase

PWM Circuit

Constant-On- Time (COT) Control

| Advantages | Disadvantages |
|---|---|
| <ul style="list-style-type: none">• Excellent load transient performance:<ul style="list-style-type: none">○ About 4x faster compared to fixed-frequency current mode• Simple architecture does not require compensation• Seamless transition between light loads and heavy loads• Does not require an internal oscillator | <ul style="list-style-type: none">• Must generate a slope on FB (e.g. using COUT_ESR)• The switching frequency (f_{sw}) is not constant due to variations in the off time• Output filter design is difficult and undesired in many sensitive systems |

Solution: Adaptive COT Control

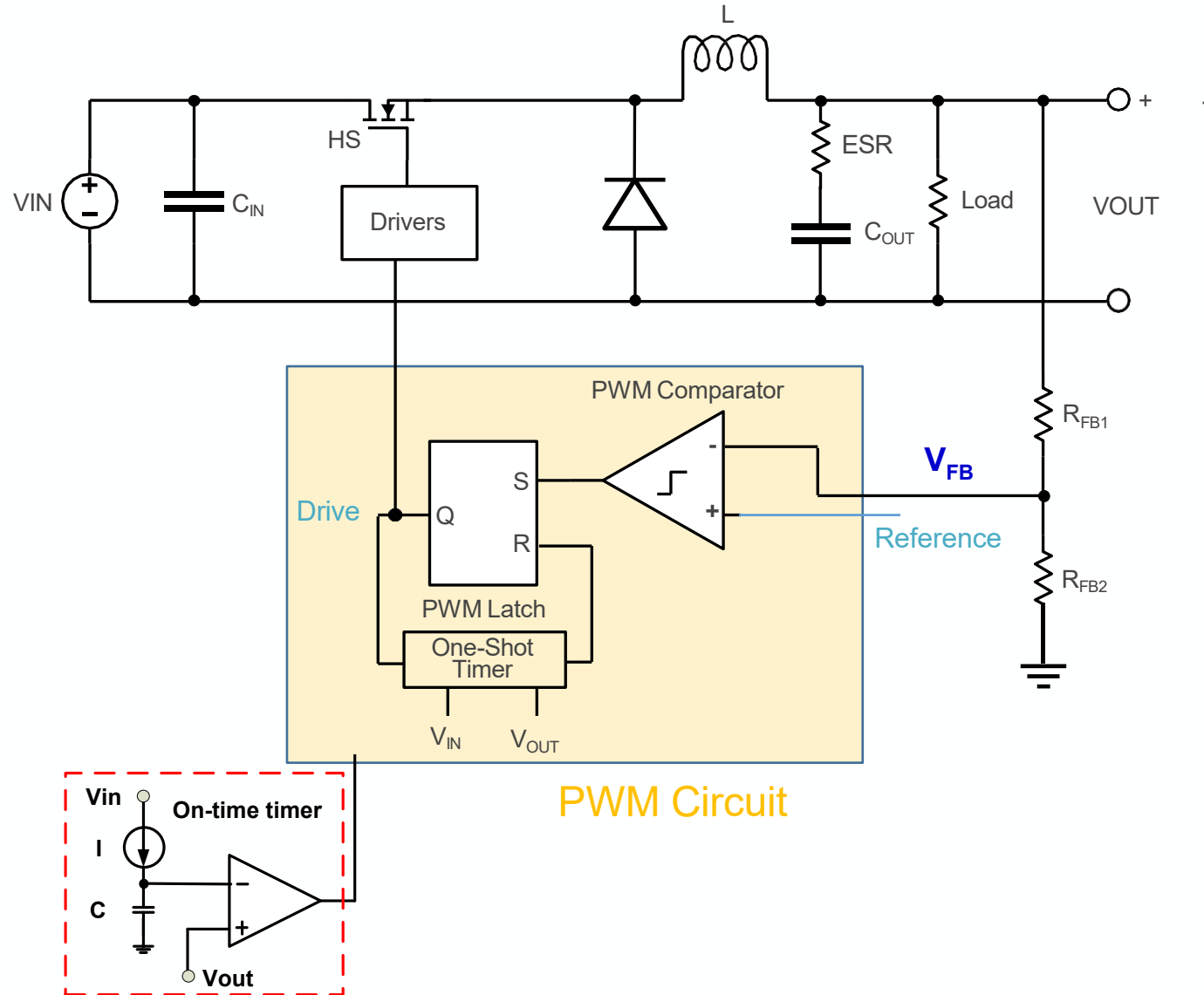

Adaptive COT control uses the conversion ratio (V_{OUT}/V_{IN}) to adjust the one-shot timer that sets the on time (t_{ON}).

This enables a steady f_{SW} during steady state, without affecting the converter's ability to immediately change the frequency when faced with a load step.


Constant-On- Time (COT) Control

Advantages

- Excellent load transient performance:
 - About 4x faster compared to fixed-frequency current mode
- Simple architecture does not require compensation
- Seamless transition between light loads and heavy loads
- Does not require an internal oscillator
- Quasi-stable frequency during state-state operation

Disadvantages

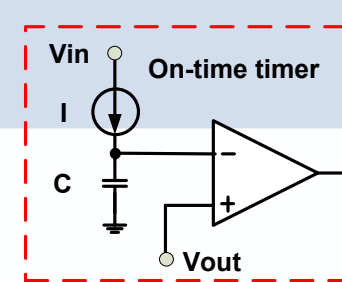- Must generate a slope on FB (e.g. using COUT_ESR)
- ~~The switching frequency (f_{sw}) is not constant due to variations in the off time~~
- Output filter design is difficult and undesired in many sensitive systems





COT Challenge: Stability Is Dependent on ESR

COT control compares the feedback voltage to a set reference voltage.

The feedback voltage ripple has two main components:



1. ESR ripple: Directly proportional to the inductor current (I_L), with no delay/phase difference
2. V_{CAP} ripple: Caused by charging/discharging the output capacitor, and is delayed with respect to I_L

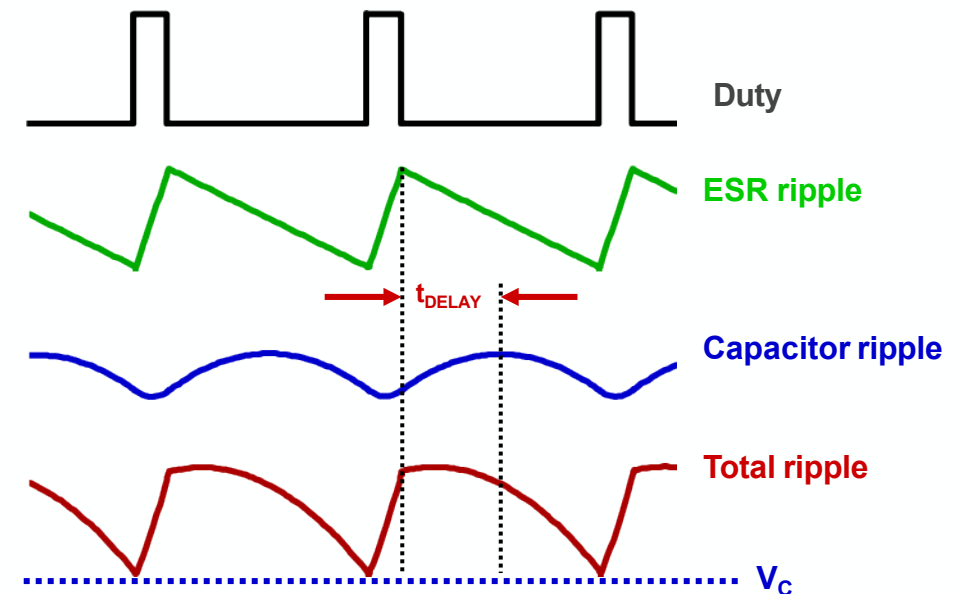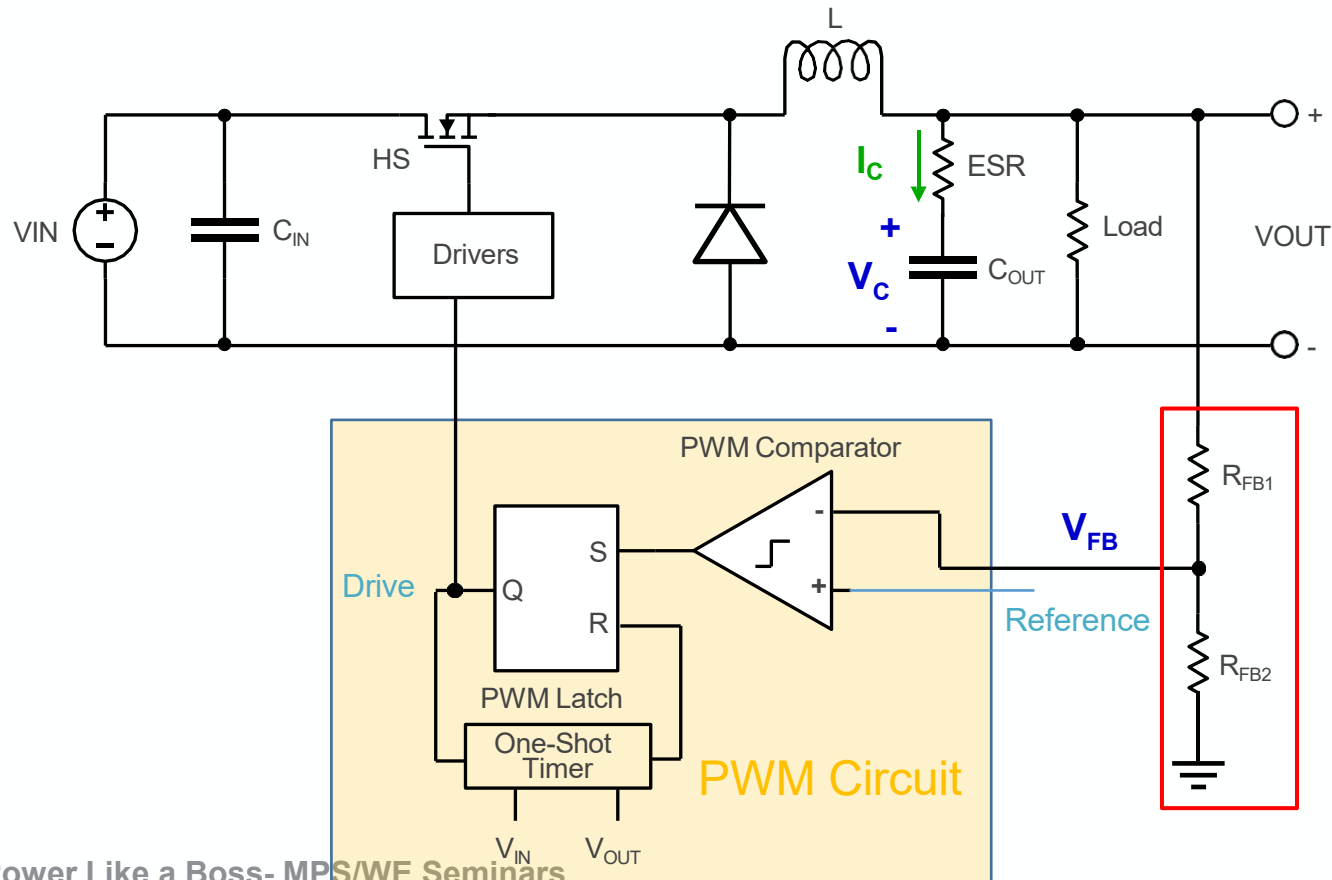

Solution 1: Stability Is Dependent on ESR- Solution 1

If the ESR ripple dominates, the V_{OUT} ripple is in phase with I_L , and the circuit operates correctly.

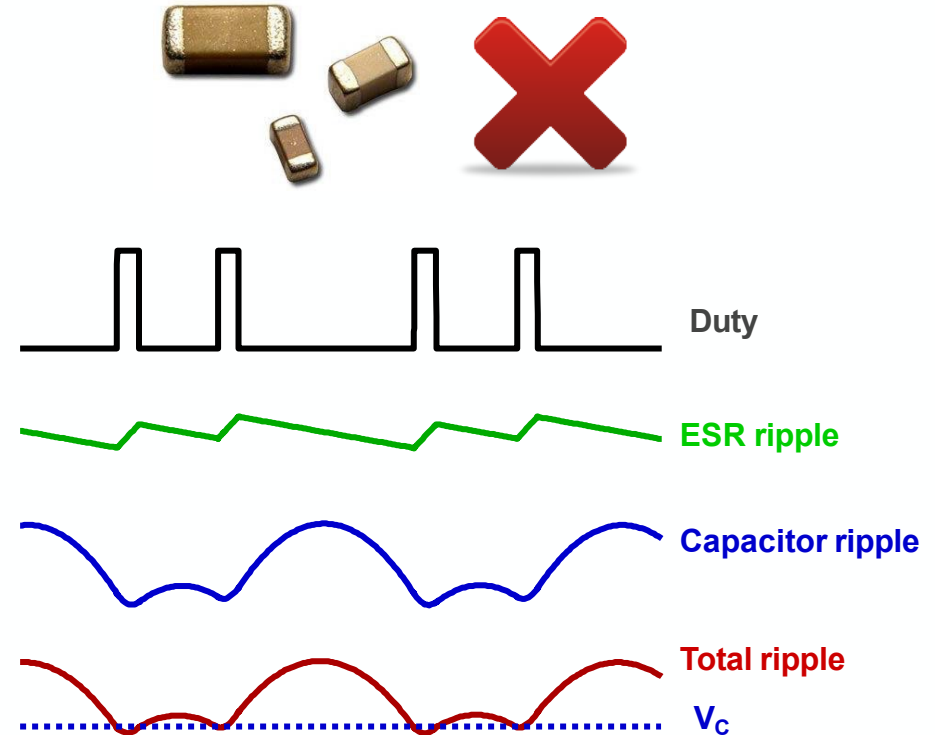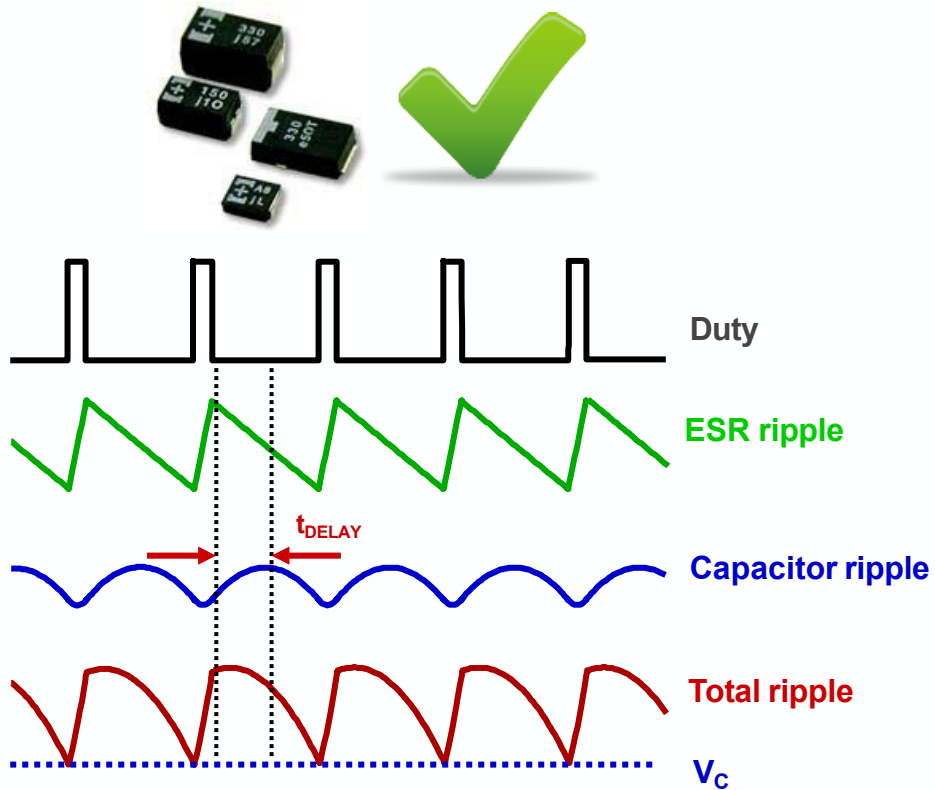If the V_{CAP} ripple dominates, the V_{OUT} ripple is out of phase with I_L , and the circuit can enter subharmonic oscillation.





COT requires output capacitors (C_{OUT}) with large ESR for stability.

If low-ESR capacitors are used (e.g. MLCC), the circuit may become unstable.


MPS Solution 2: Current Ripple Injection

Option 2: Add an external ramp

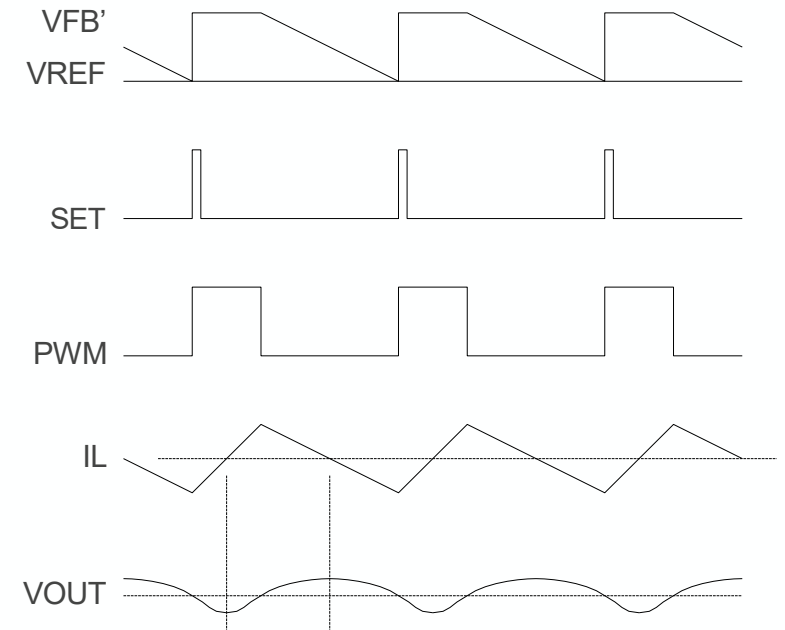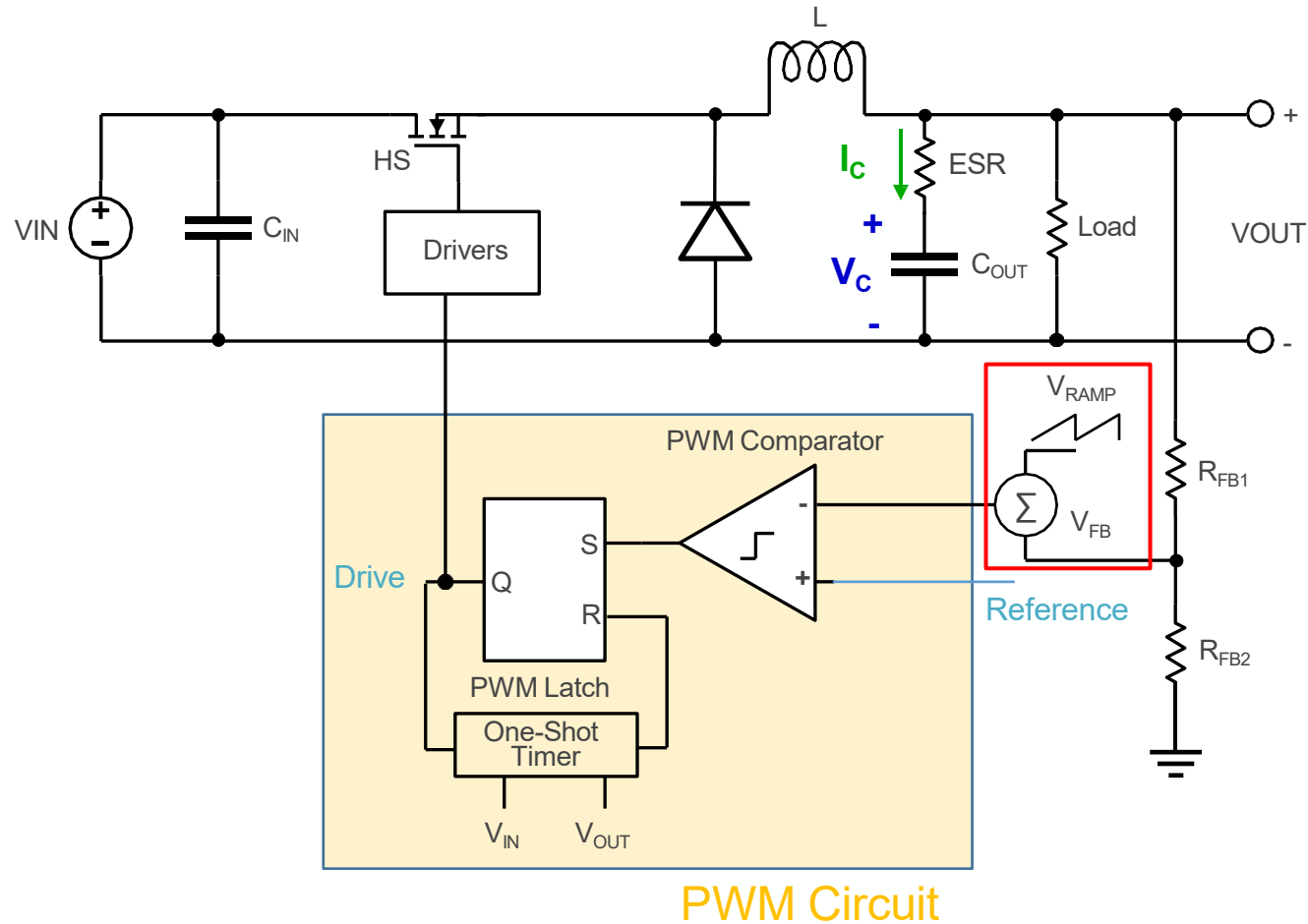

MPS Solution 3: Current Ripple Injection

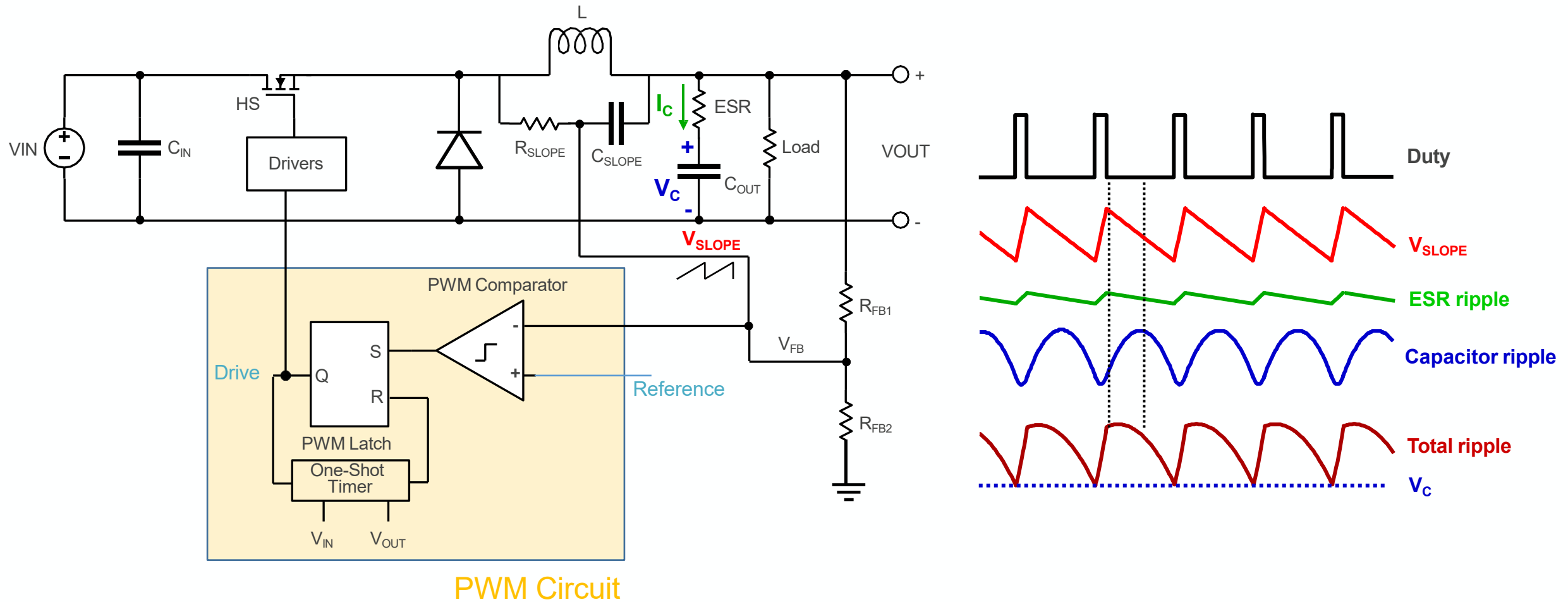Option 3: Use the RC circuit to generate a slope voltage and ensure that the FB ripple is in phase with I_L




Constant-On- Time (COT) Control

| Advantages | Disadvantages |
|--|---|
| <ul style="list-style-type: none">• Excellent load transient performance:<ul style="list-style-type: none">○ About 4x faster compared to fixed-frequency current mode• Simple architecture does not require compensation• Seamless transition between light loads and heavy loads• Does not require an internal oscillator• Quasi-stable frequency during state-state operation• Integrated slope generator to keep the converter stable, even with low ESR | <ul style="list-style-type: none">• Must generate a slope on FB (e.g. using COUT_ESR)• The switching frequency (f_{sw}) is not constant due to variations in the off time• Output filter design is difficult and undesired in many sensitive systems |

Constant On-time Control - Operation

(w/ Offset Cancellation & Synthetic Ramp)

Legend
Fast Change: ↑
Slow change: ↑

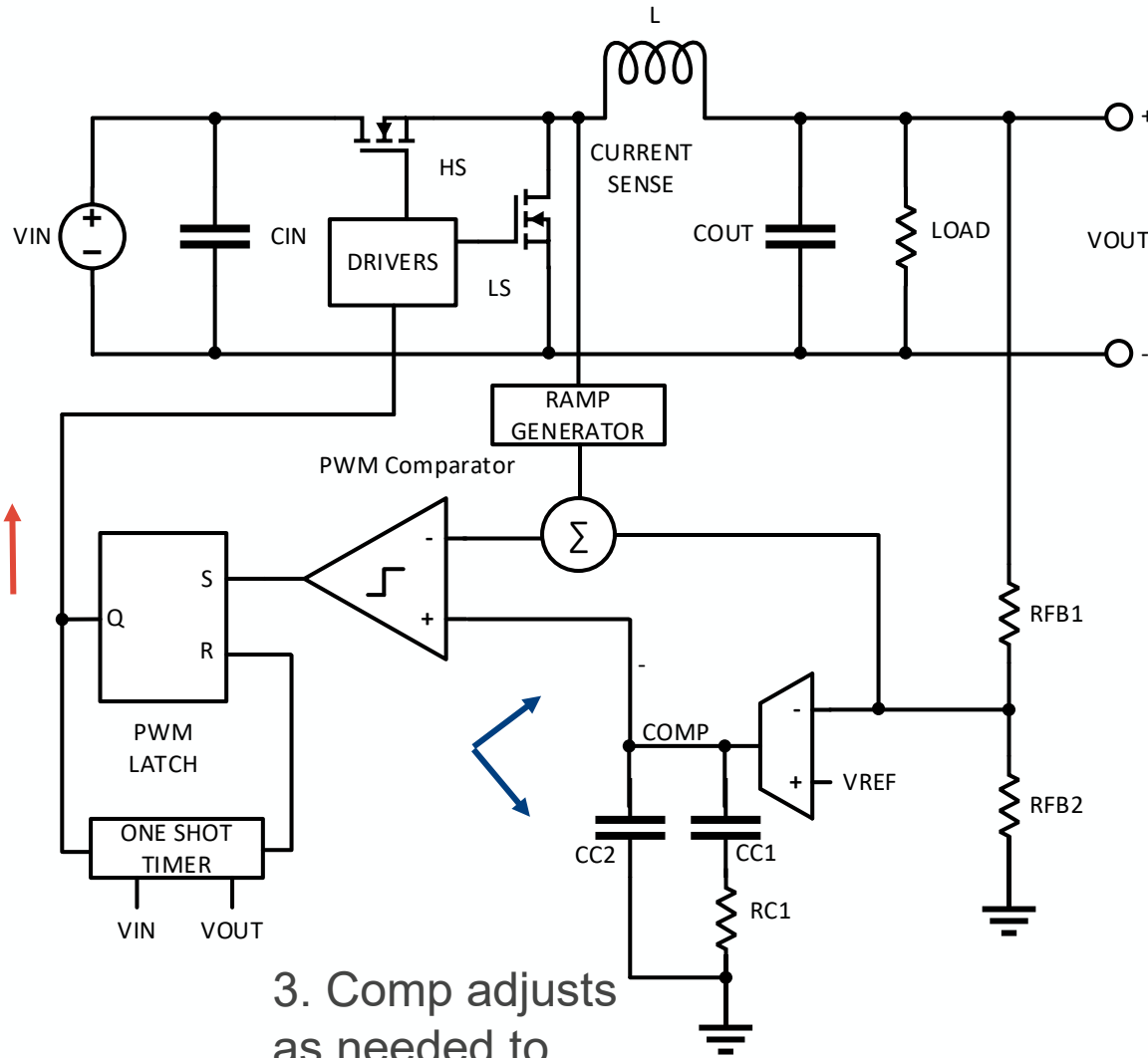


1. Sudden Current Increase causes output to drop

2. Vout dropping directly and immediately causes duty cycle to increase


3. Comp adjusts as needed to maintain DC regulation

COT Advantages: Fast Transient Response

Peak Current Mode

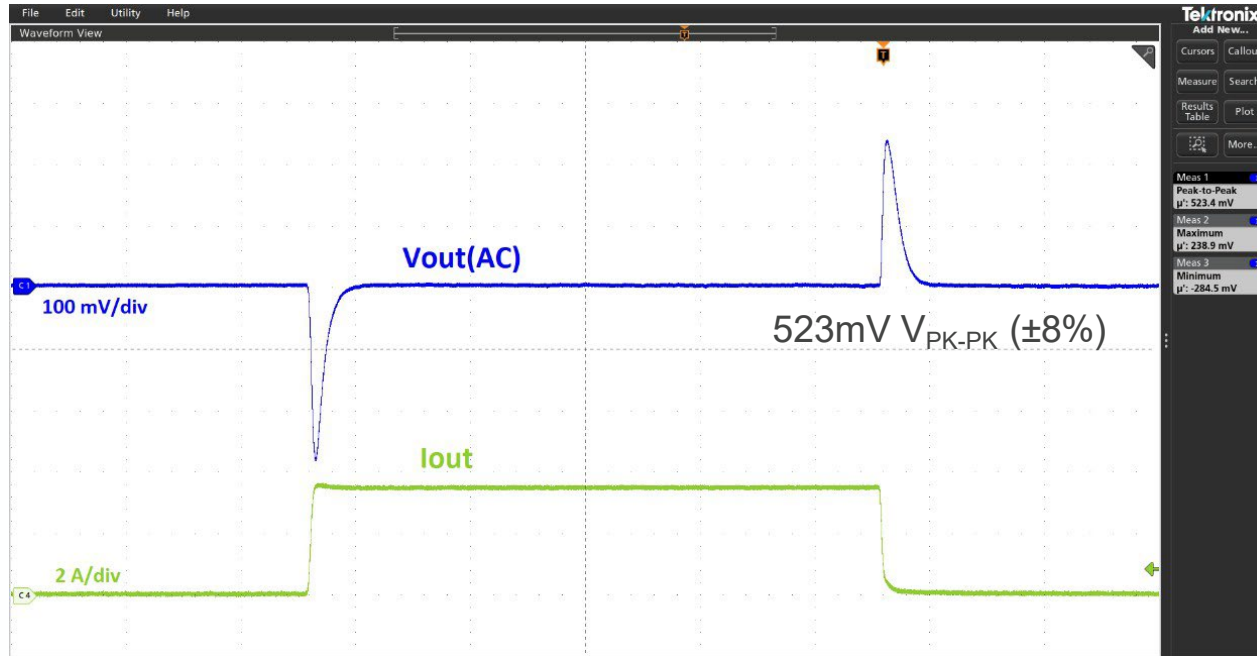


Constant-On-Time

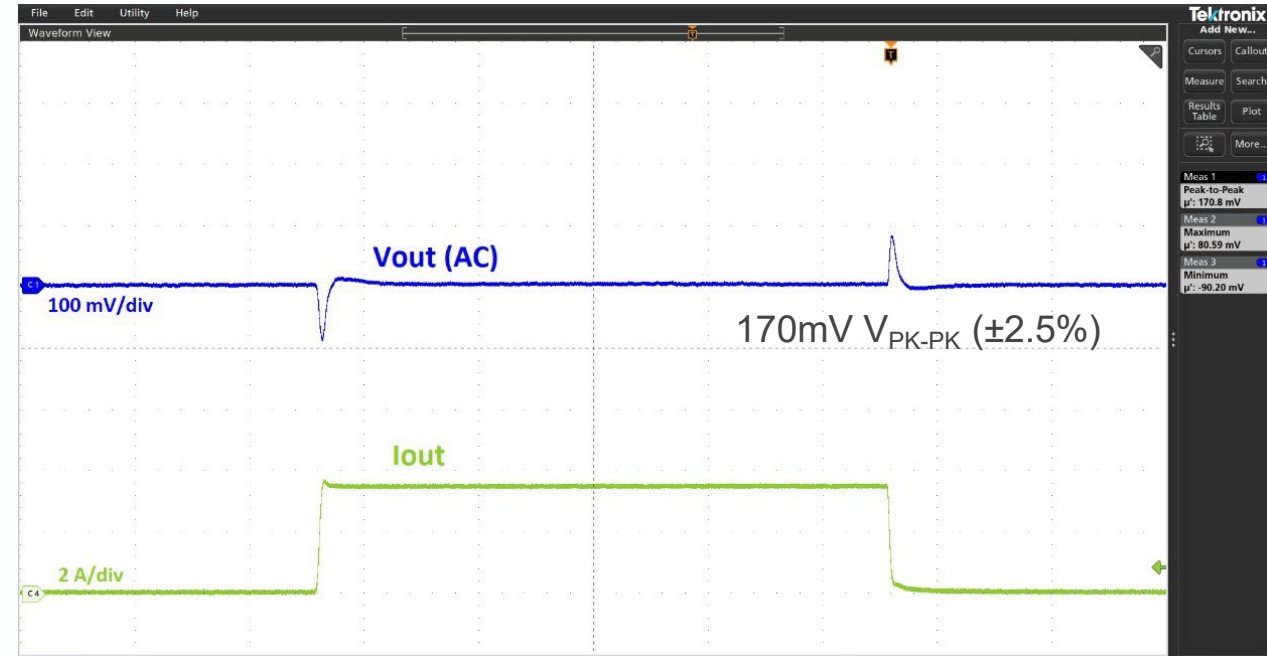


- 3x faster transient response compared to peak current mode with the same components and set-up:
 - 12V input, 3.3V output, 0A to 3.5A load step
 - $1\mu\text{H}$ L_{OUT} , $2 \times 22\mu\text{F}$ C_{OUT}

Fastest Fix Frequency Control – ZDP

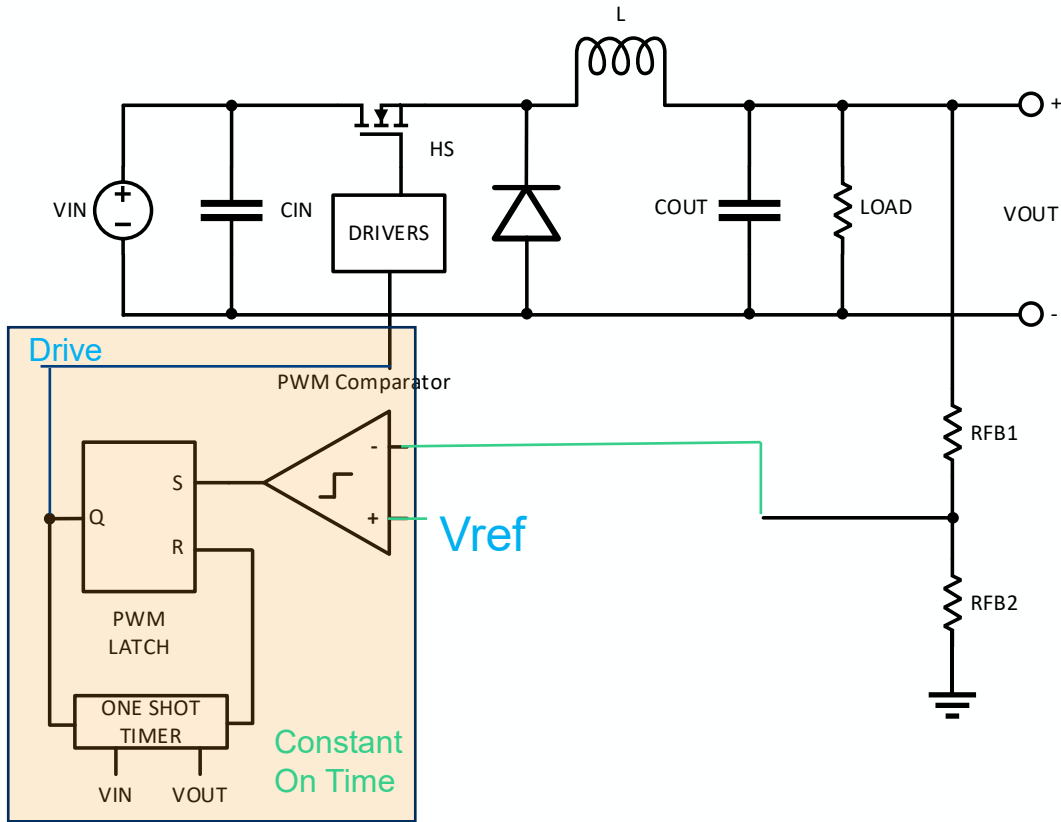



PWM Modulation Circuit

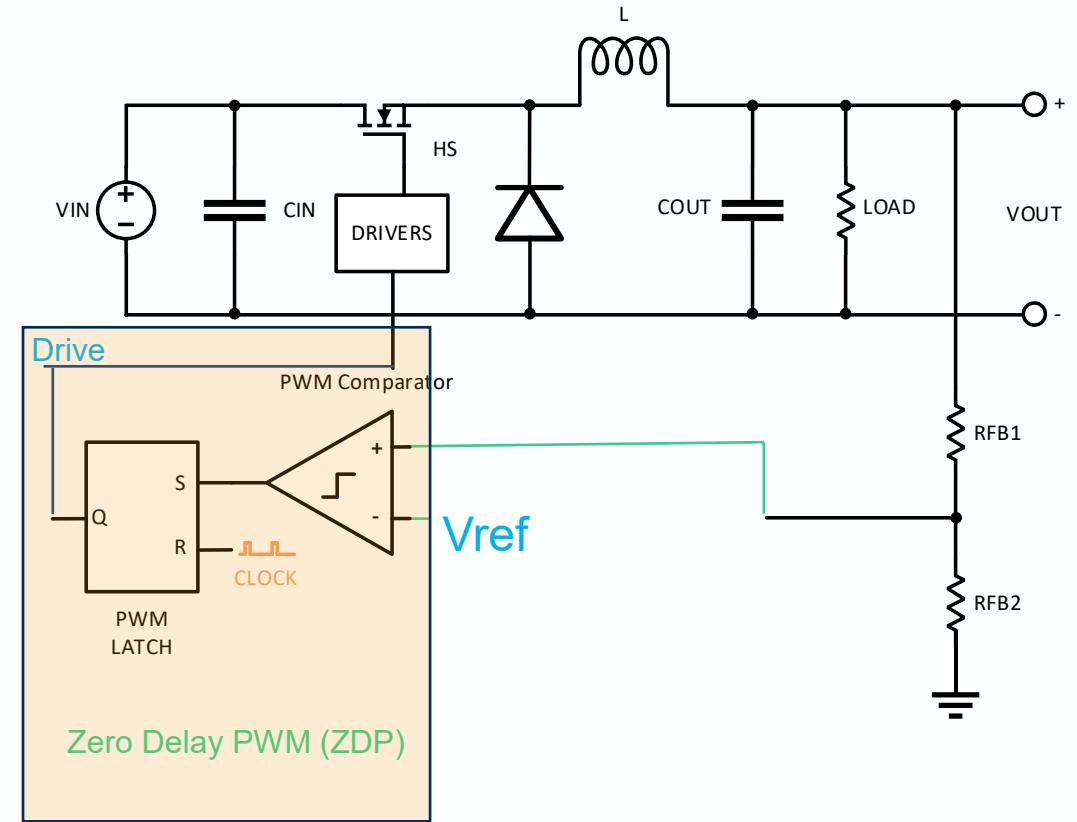- Use clock to set the fix frequency for turn off
- Turn on immediately when V_o is lower than V_{ref}
- As the result, duty cycle is changed instantly to response the transient



PWM Modulation Circuit



ZDP Control

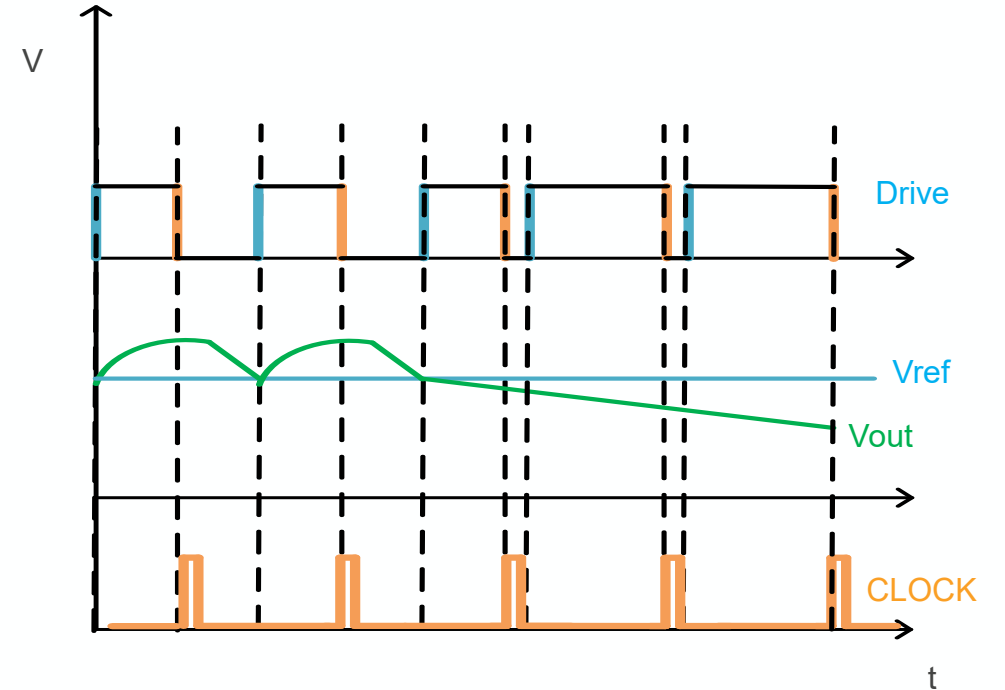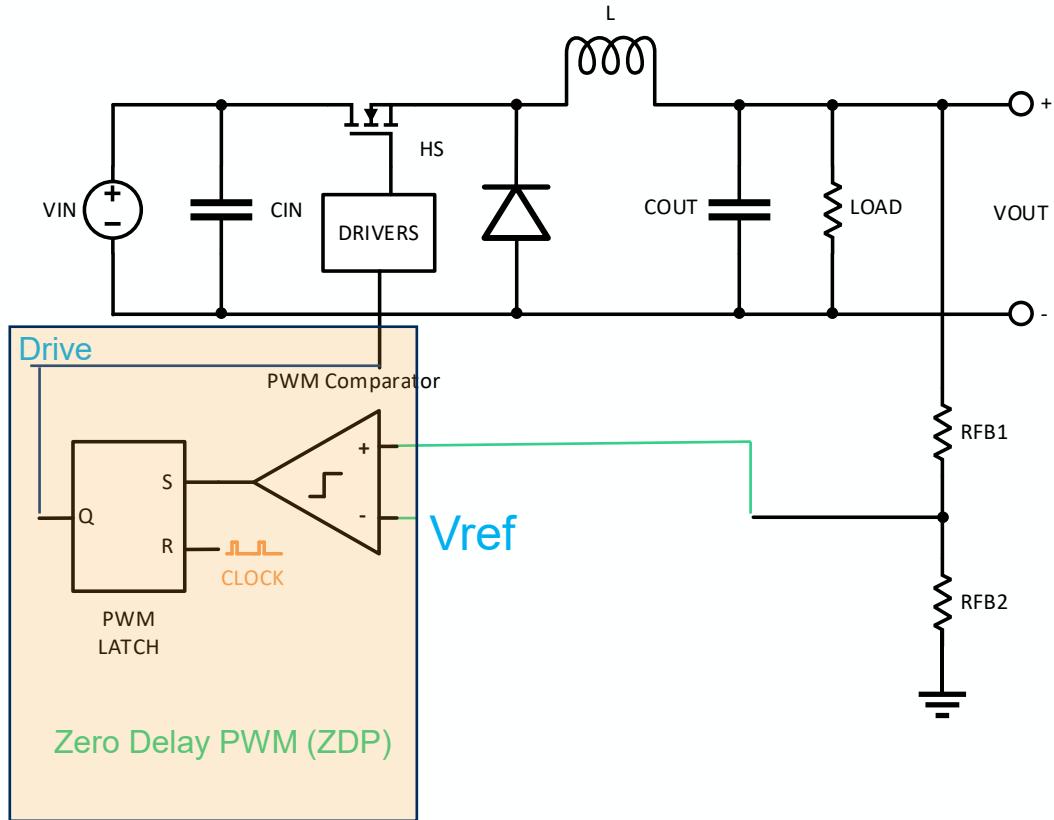

PWM Modulation Circuit



- Fastest Fixed Frequency Control because the duty cycle instantly change
- No linear control loop delay

Barebone ZDP in Frequency domain

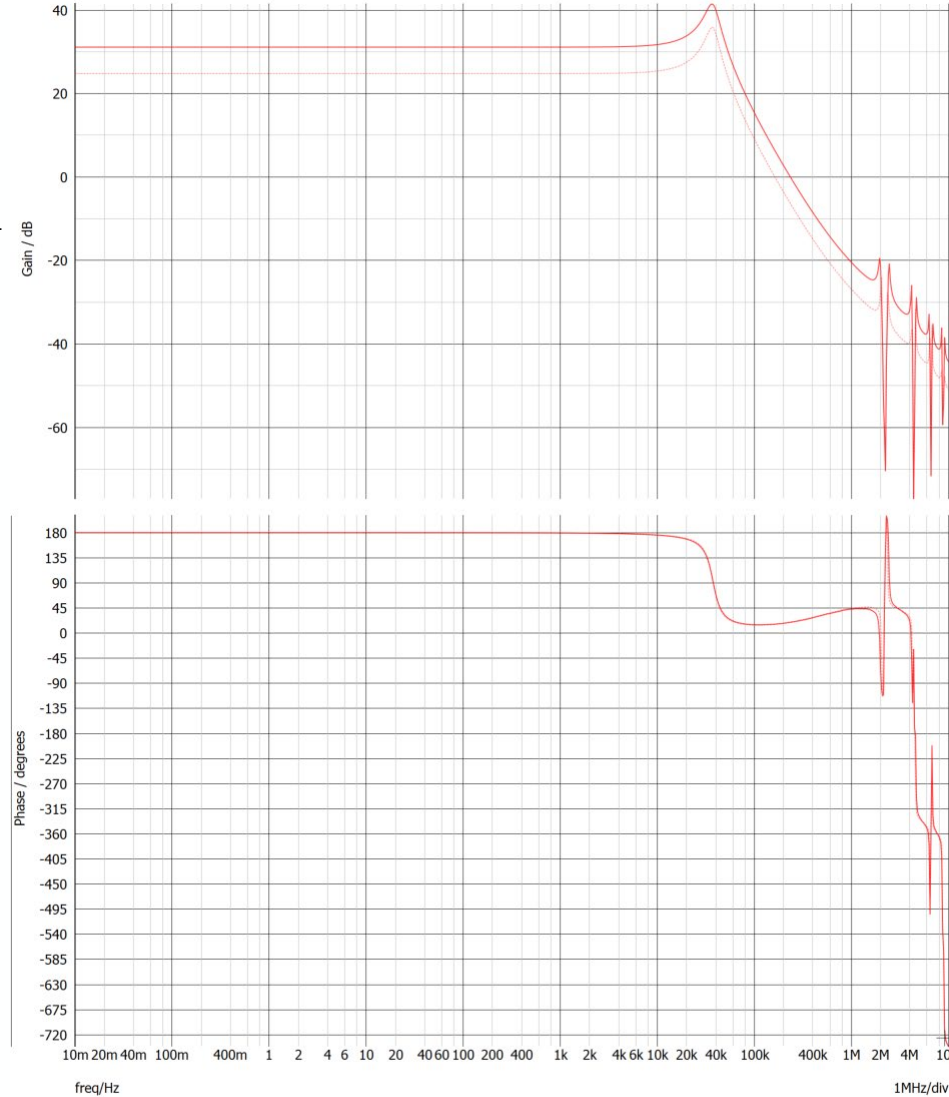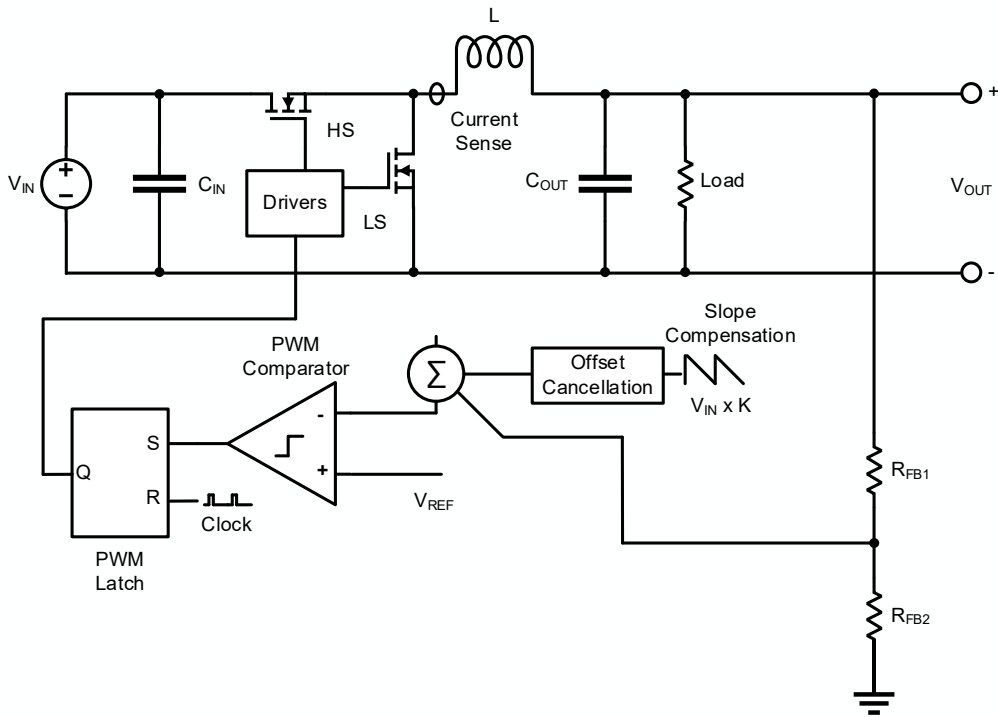

- 1x Ramp (K)
 - Crossover Frequency: 234kHz
 - Gain Margin: 20dB
 - Phase Margin: 19 degrees
- 2x Ramp (K)
 - Crossover Frequency: 163kHz
 - Gain Margin: 26dB
 - Phase Margin: 16 degrees

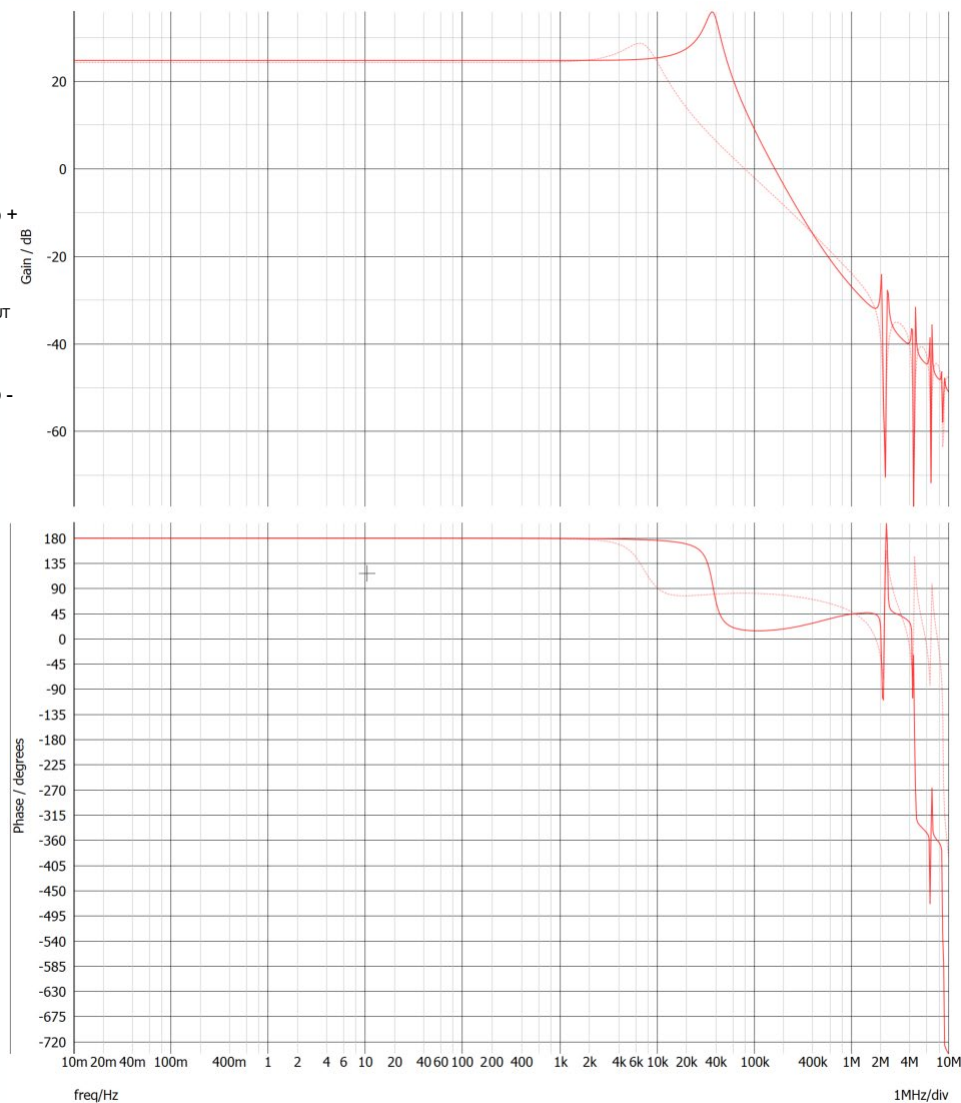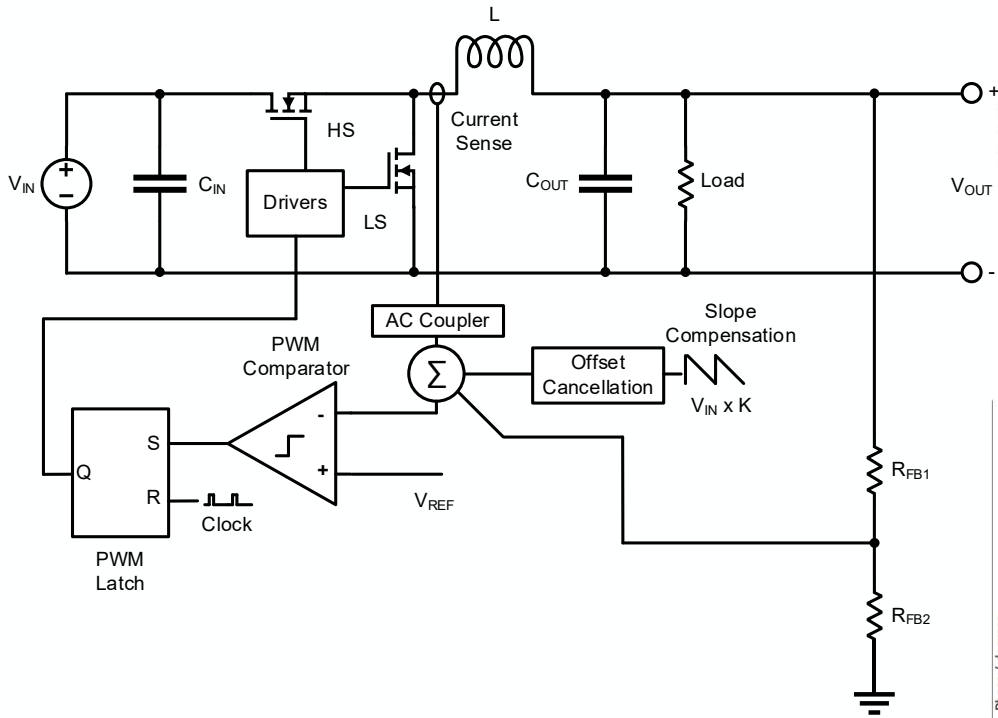Damp the Double Pole to Reduce the Phase Drop




- w/o AC coupler
 - Crossover Frequency: 163kHz
 - Gain Margin: 26dB
 - Phase Margin: 16 degrees
- - - with AC coupler
 - Crossover Frequency: 85kHz
 - Gain Margin: 32dB
 - Phase Margin: 81 degrees

Double pole is damped

| Curve label | Name | Value |
|-------------|--------------------------|------------------|
| Gai... | Gain Crossover Frequency | 162.58219kHz |
| Gai... | Gain Margin | 26.014644dB |
| Pha... | Phase Margin | 16.104432degrees |

Add Integrator to Reduce the DC Offset


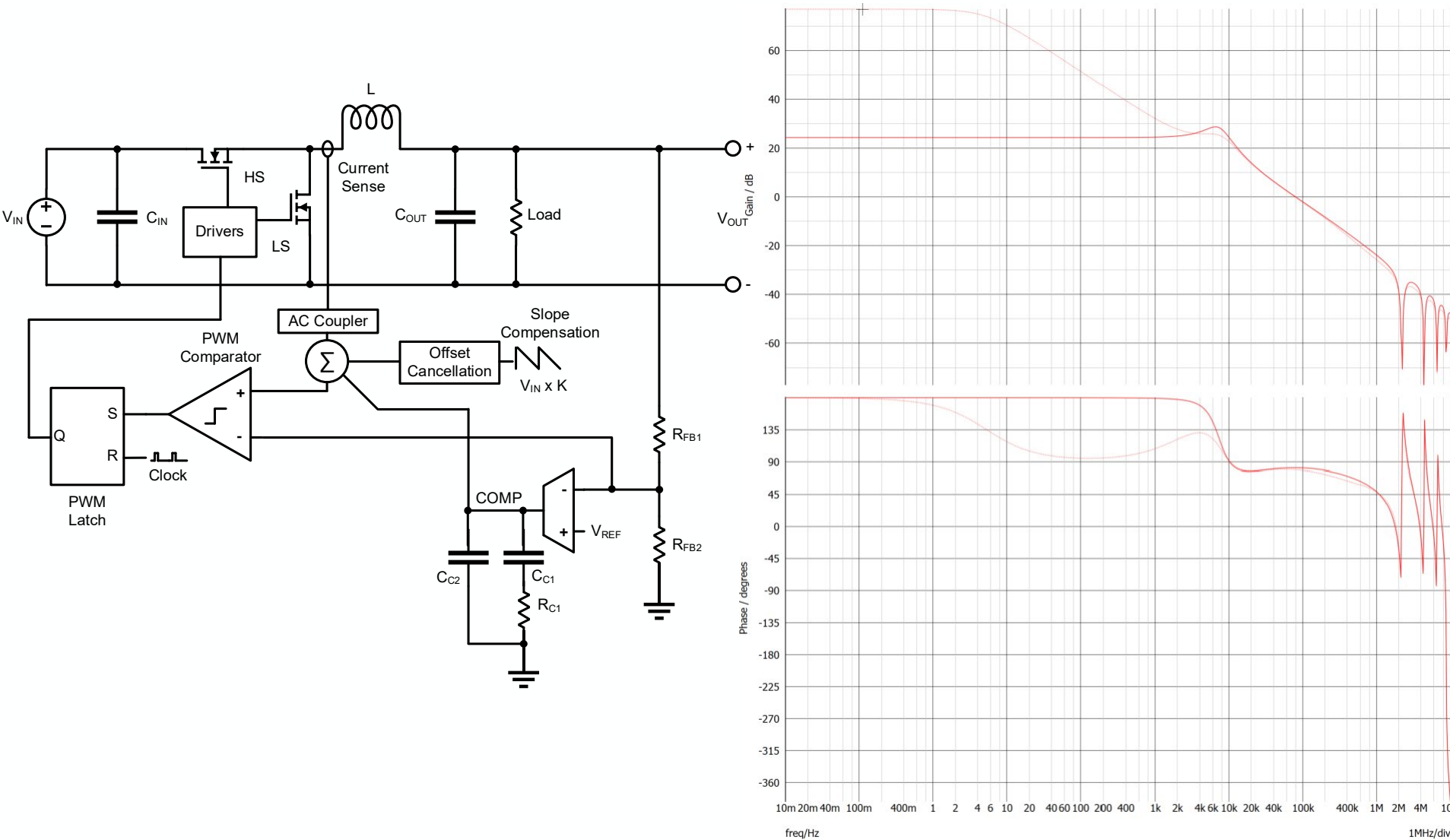


- w/o Integrator
 - Crossover Frequency: 85kHz
 - Gain Margin: 32dB
 - Phase Margin: 81 degrees
- - - with Integrator
 - Crossover Frequency: 80kHz
 - Gain Margin: 32dB
 - Phase Margin: 82 degrees

| Curve label | Name | Value |
|--------------|--------------------------|------------------|
| Gain (si...) | Gain Crossover Frequency | 79.70616kHz |
| Gain (si...) | Gain Margin | 32.437418dB |
| Phase (...) | Phase Margin | 81.730879degrees |



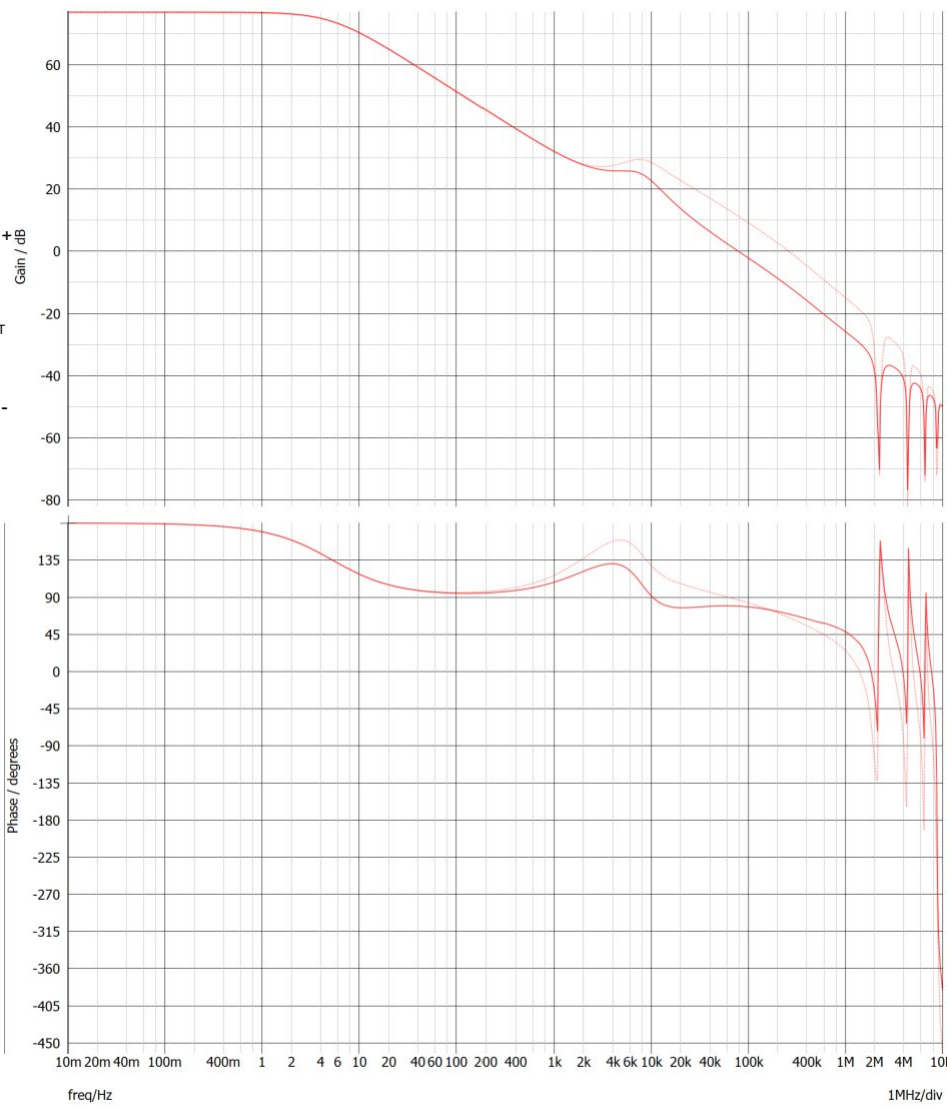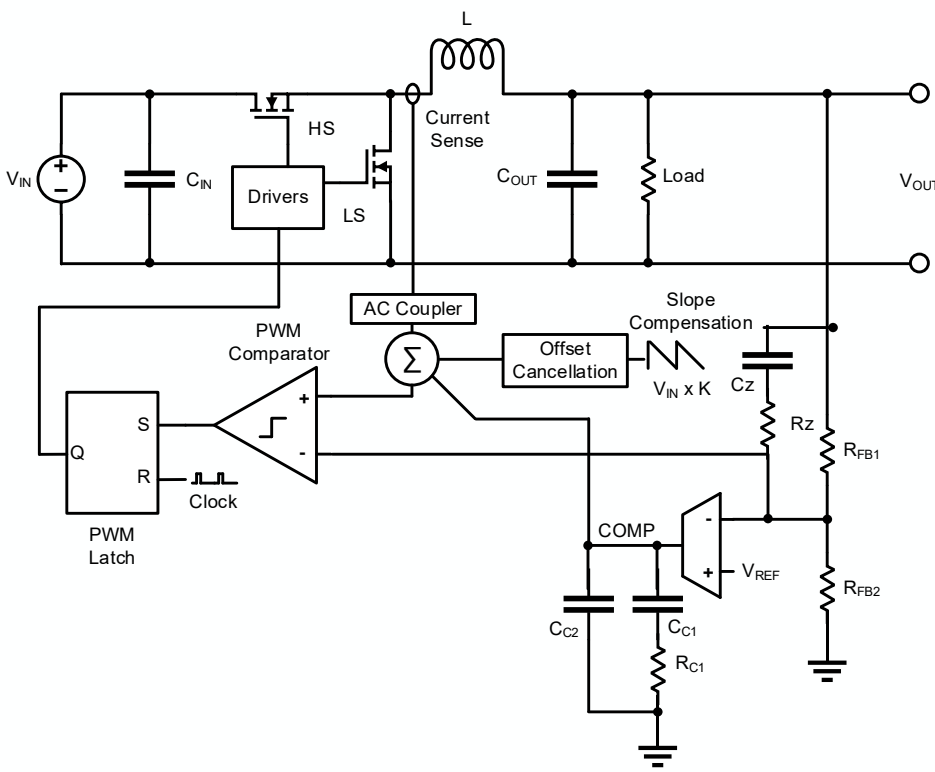Add Zero to Further Increase the Bandwidth





- w/o zero
- Crossover Frequency: 80kHz
- Gain Margin: 32dB
- Phase Margin: 82 degrees
- - - with zero
- Crossover Frequency: 245kHz
- Gain Margin: 19dB
- Phase Margin: 61 degrees

| Legend | Curve label | Name | Value |
|--------|-------------|--------------------------|------------------|
| Gain | Gai... | Gain Crossover Frequency | 78.75741kHz |
| Gain | Gai... | Gain Margin | 34.434187dB |
| Phase | Pha... | Phase Margin | 79.297673degrees |



ZDP Complete View in Frequency Domain

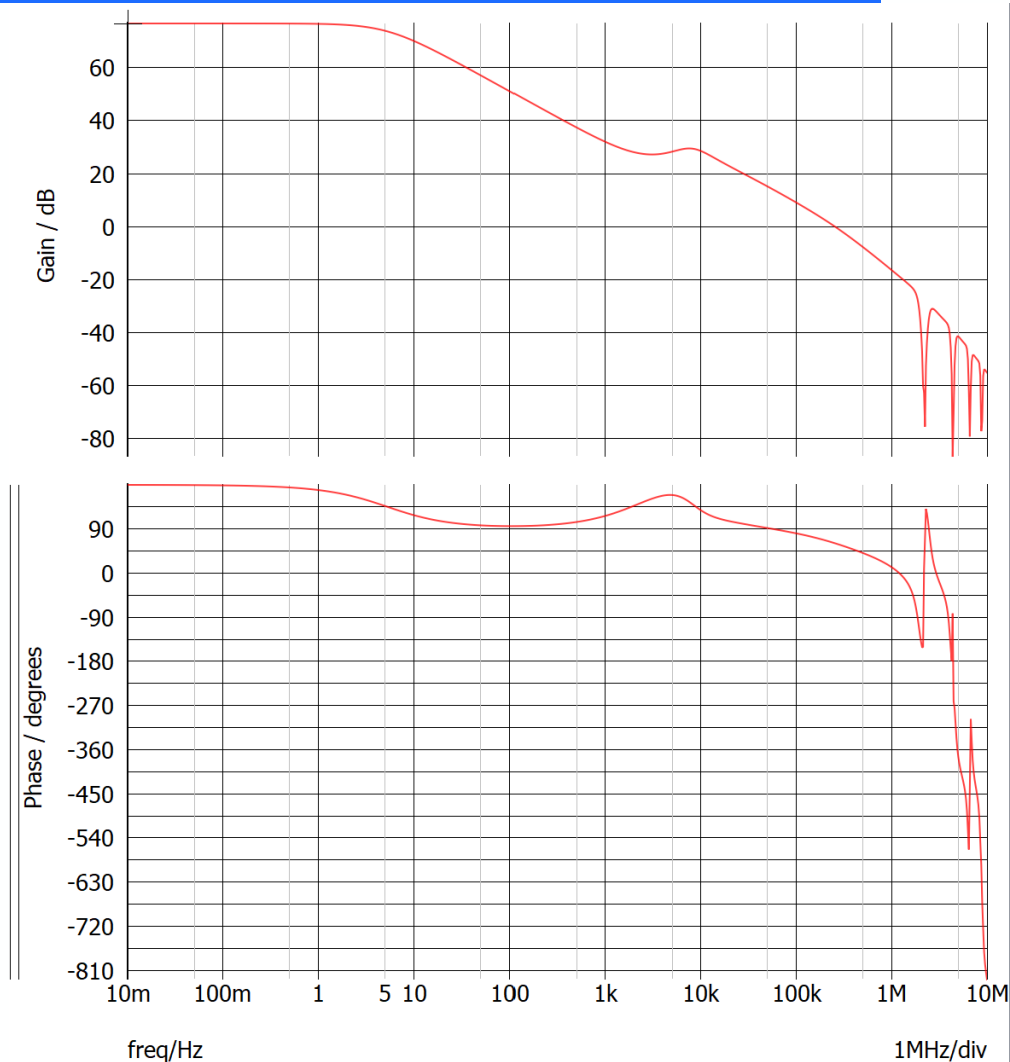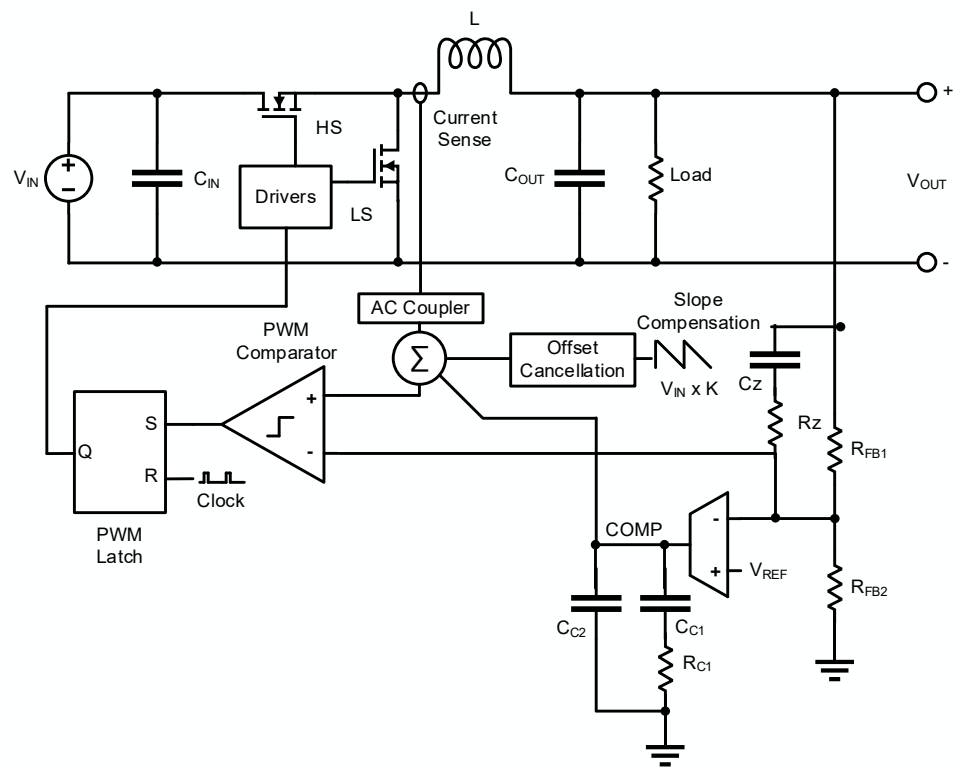



| .abel | Legend |
|-------|--------|
| Gain | — |
| Phase | — |

| Curve label | Name | Value |
|-------------|--------------------------|------------------|
| Gain | Gain Crossover Frequency | 254.45439kHz |
| Gain | Gain Margin | 18.791254dB |
| Phase | Phase Margin | 60.914817degrees |



With any possible control method, the highest bandwidth a switching converter can achieve is $\frac{1}{2}$ of switching frequency. This is limited by switcher.

How much ZDP can achieve?

Push the Bandwidth to the extreme

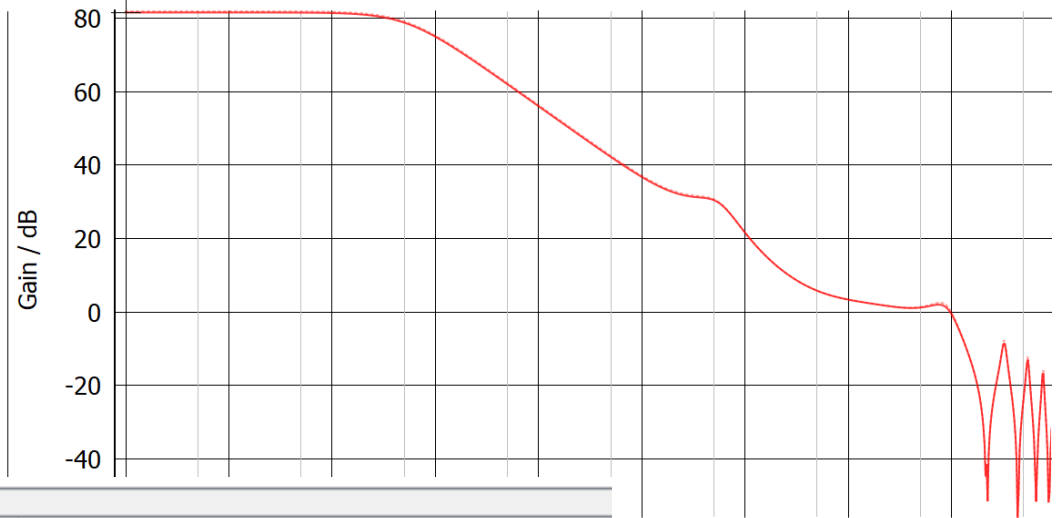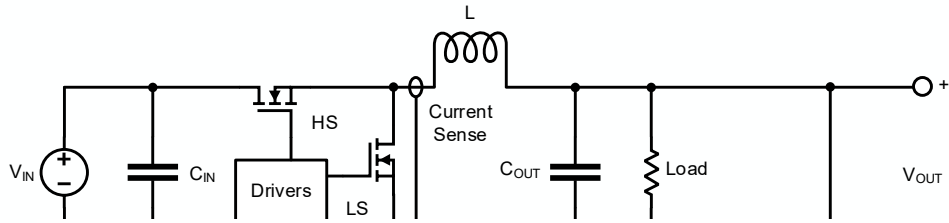

| Curve label | Name | Value |
|-------------|--------------------------|------------------|
| Gain (si... | Gain Crossover Frequency | 969.97022kHz |
| Gain (si... | Gain Margin | 9.2431529dB |
| Phase (... | Phase Margin | 46.486888degrees |

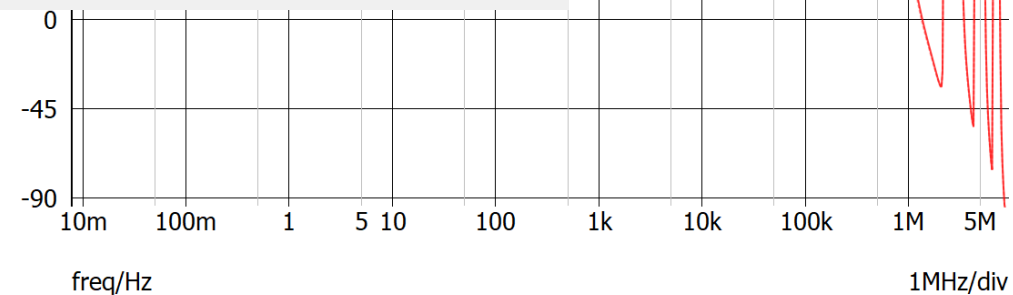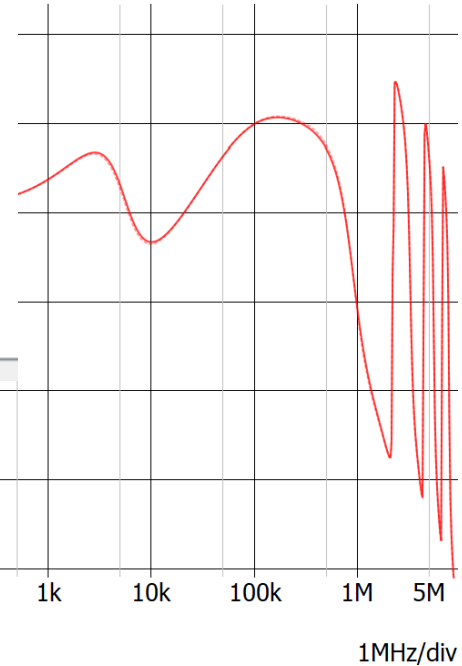

| Label | Legend |
|--------|--------|
| Gai... | — |
| Pha... | — |


| Curve label | Name | Value |
|-------------|--------------------------|------------------|
| Gain (si... | Gain Crossover Frequency | 969.97022kHz |
| Gain (si... | Gain Margin | 9.2431529dB |
| Phase (... | Phase Margin | 46.486888degrees |

COT Advantages: Fast Transient Response


- 12V input, 3.3V output, 0A to 3.5A load step

1 μ H L_{OUT}, 2x22 μ F C_{OUT}


Peak Current Mode

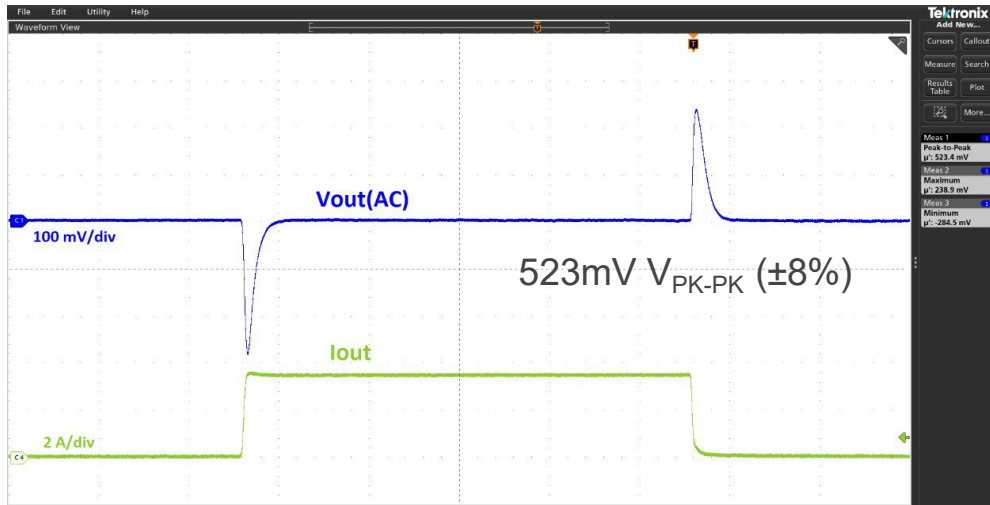


Constant-On-Time

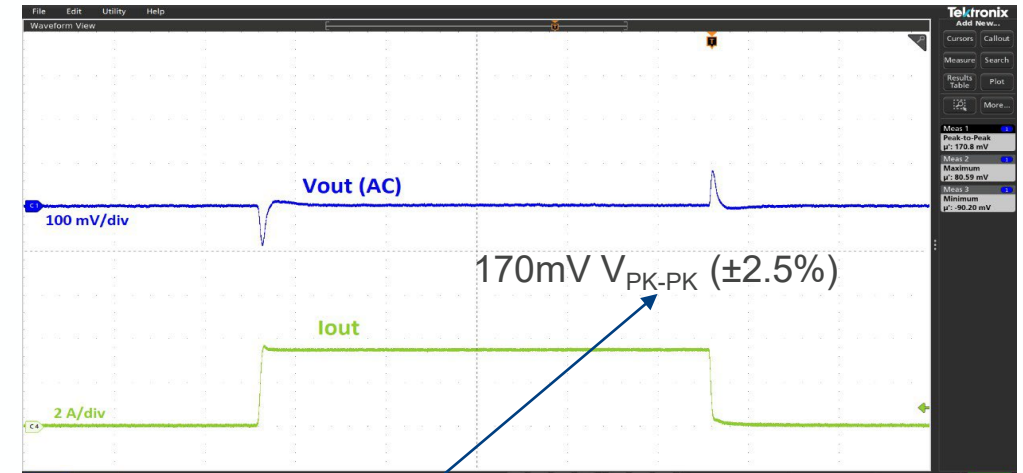


1 μ H L_{OUT}, 1x22 μ F C_{OUT}

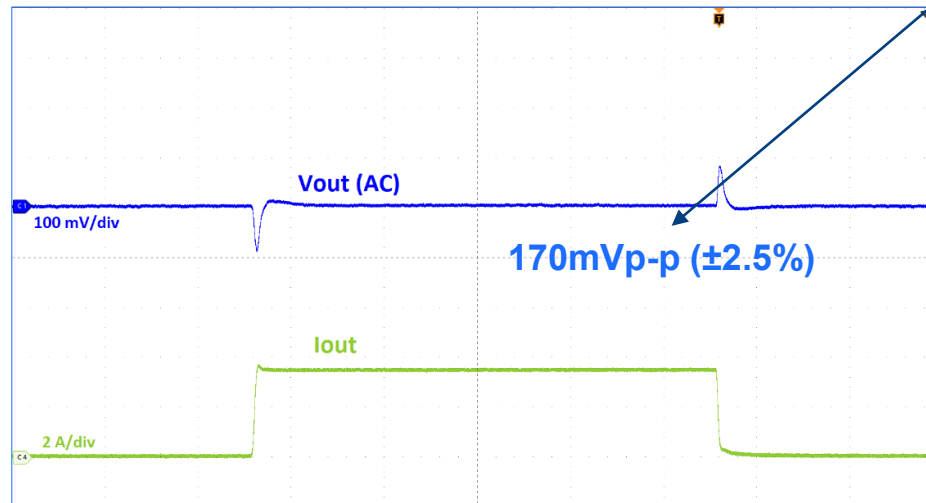


ZDP on a board

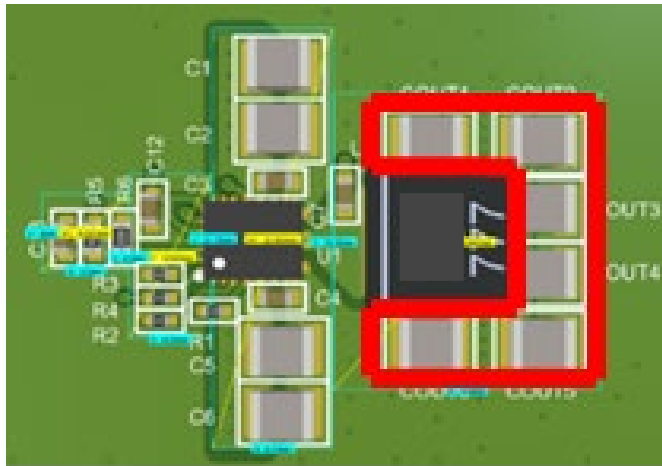

402mm²

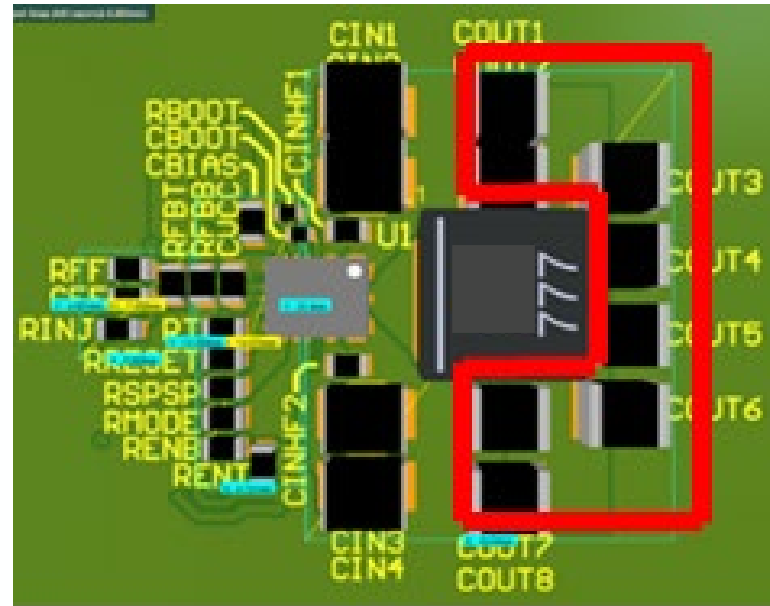

444mm²

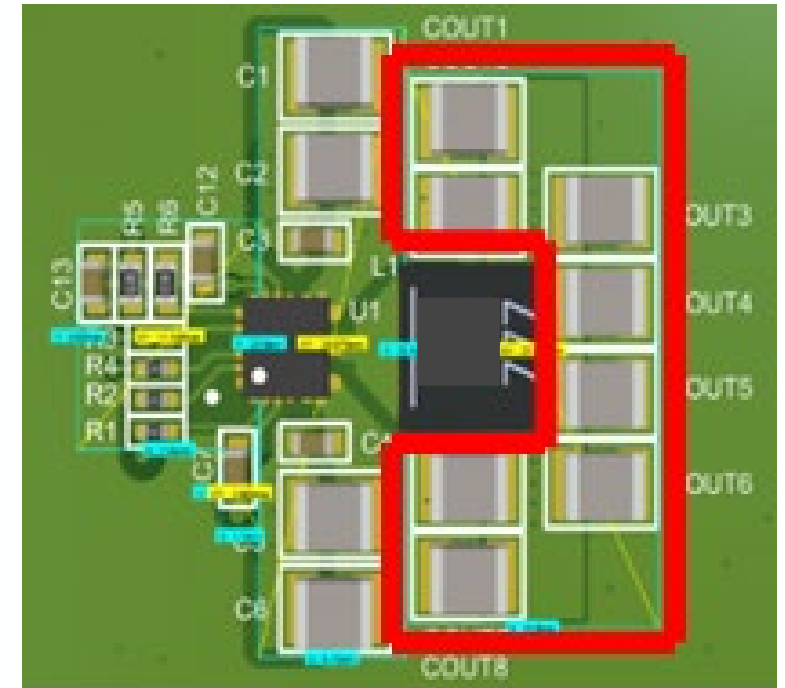

445mm²

Thank You